

Physics 321: HW 5

Do problems 4.6, 4.7, 4.13, and 4.16 in Sprott.

Hint for problem 4.13: try sliding R_2 to the left of C and replace the two resistors and V_{in} with a Thevenin equivalent circuit.