
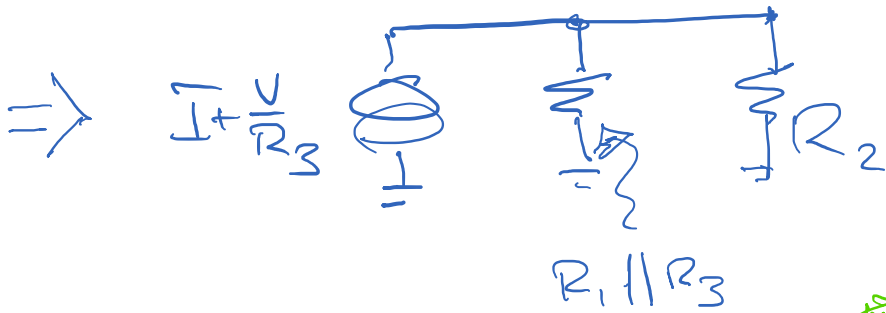


# MIDTERM SOLUTIONS

①

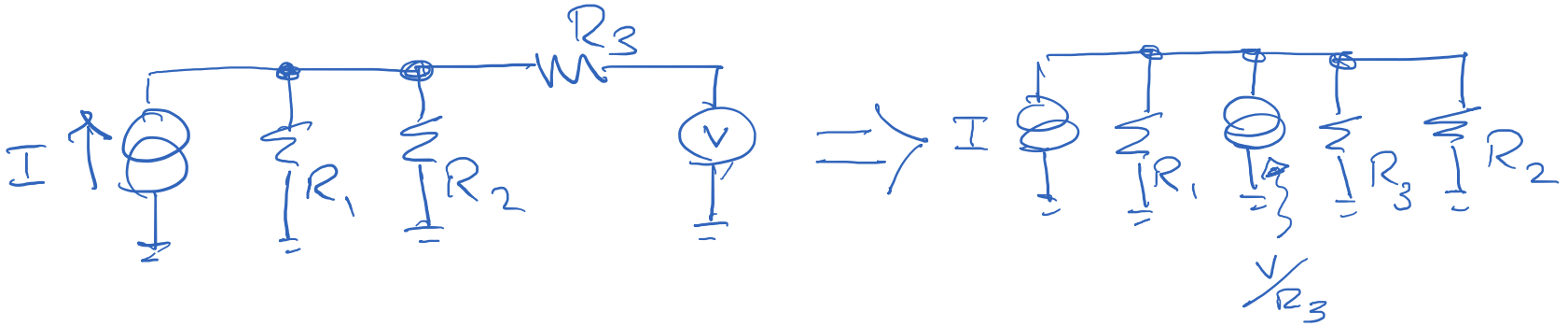


$$I(R_2) = \frac{R_1 \parallel R_3}{R_1 \parallel R_3 + R_2} \left[ I + \frac{V}{R_3} \right]$$

CURRENT DIVIDER  $\rightarrow$

$$= \frac{R_1}{R_1 R_2 + R_1 R_3 + R_2 R_3} \left[ I + \frac{V}{R_3} \right]$$

2

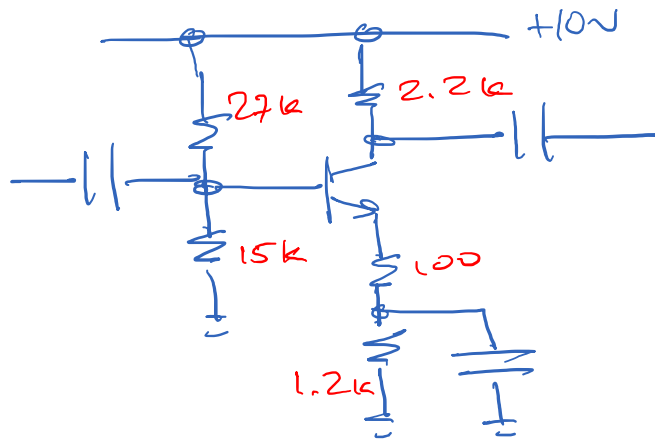

$$\underline{\underline{A}} \quad V_B \approx 10V \times \frac{15k}{15k + 27k} = 3.6V$$

[A MORE DETAILED CALCULATION THAT TAKES INTO ACCOUNT CURRENT DRAWN BY BASE YIELDS  $V_B = 3.4V$ ]

$$V_E = 3.6V - 0.6V = 3.0V \Rightarrow I_E \approx I_C = 2.3\mu A$$

$$V_C = 10V - (2.2k)(2.3\mu A) = 4.9V$$

B3  $R_{in} = 15k \parallel 27k \parallel R(\text{into base})$

$R(\text{into base})?$

@ SIGNAL FREQUENCIES,

HAVE  $R_{out} \approx \left(\frac{25}{2-3}\right) \Omega + 100\Omega \approx 110\Omega$

FROM EMITTER TO GROUND

$$R_{in} \approx 15k \parallel 27k \parallel 11k$$

$$\approx \underline{\underline{5.1k\Omega}}$$

C

$$R_{out} = R_c = 2.2k\Omega$$

D


For small signals,

RESISTANCE FROM EMITTER TO GROUND

IS  $\sim 110\Omega$

$$A_v = - \frac{R_c}{R_{E,eff}} = - \frac{2.2k}{110} = -20$$

3

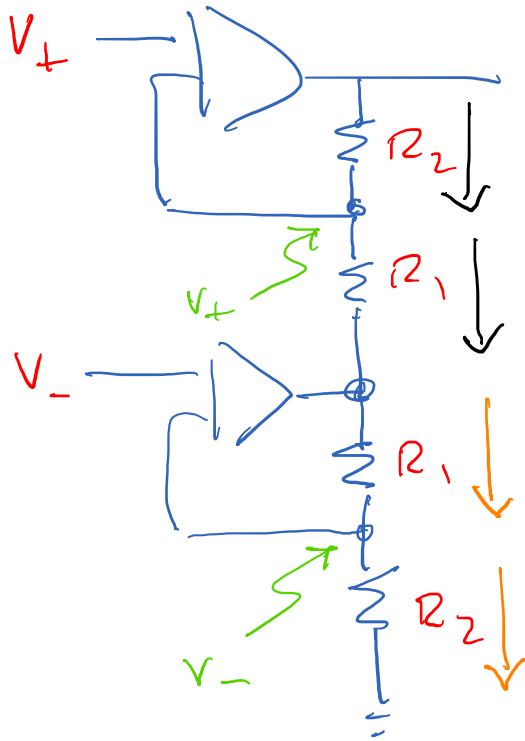

CURRENTS IN BLACK ARE EQUAL

CURRENTS IN ORANGE ARE EQUAL

[OP. AMP INPUTS DRAW NO CURRENT]

- CURRENT THRU  $R_2$  TO GROUND IS  $\frac{V_-}{R_2}$
- VOLTAGE @ OUTPUT OF LOWER OP. AMP IS THEREFORE  $V_- + \left(\frac{V_-}{R_2}\right)R_1$
- CURRENT THRU UPPER OP AMP IS  $\therefore \frac{1}{R_1} \left[ V_+ - \left(1 + \frac{R_1}{R_2}\right)V_- \right]$
- THIS SAME CURRENT FLOWS THRU UPPER RESISTOR  $R_2$ .

$\therefore$


$$V_{out} = V_+ + \frac{R_2}{R_1} \left[ V_+ - \left(1 + \frac{R_1}{R_2}\right)V_- \right]$$

$$= \left(1 + \frac{R_2}{R_1}\right) (V_+ - V_-)$$

$$A_{cm} = 0 ; A_D = 1 + \frac{R_2}{R_1}$$


4

A. VOLTAGE NOISE ?

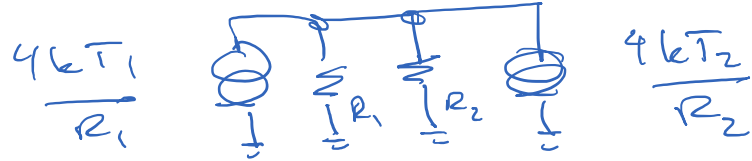

$$S_V = 4k \left[ \frac{T_1}{R_1} + \frac{T_2}{R_2} \right] (R_1 \parallel R_2)^2$$
$$= 4k [T_1 R_2 + T_2 R_1] \left[ \frac{R_1 R_2}{(R_1 + R_2)^2} \right]$$

B. CURRENT NOISE ?

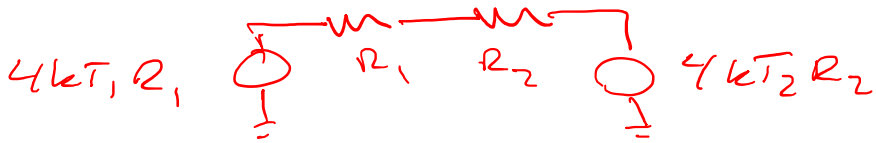

$$S_I = \frac{4k (T_1 R_1 + T_2 R_2)}{(R_1 + R_2)^2}$$