
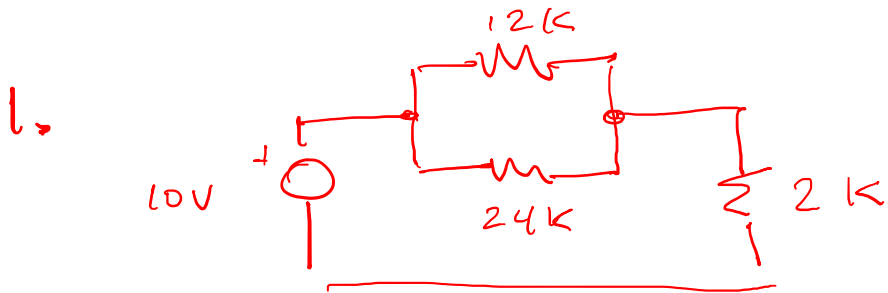



PS 1 SOLUTIONS

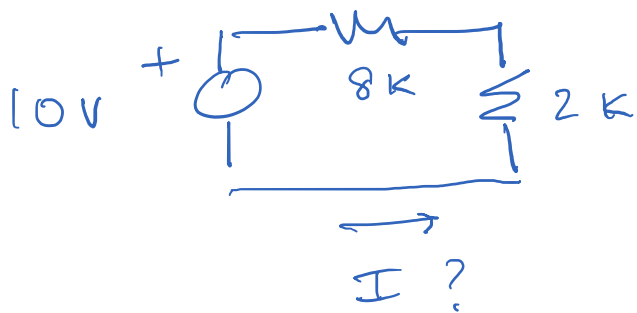

\rightarrow
 $I ?$



$$\underline{I = -1 \mu A}$$

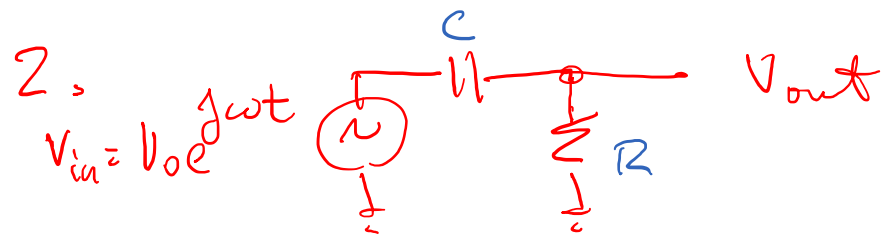

$$V_{out} = \frac{R}{R - j\frac{1}{\omega C}} V_{in} \quad ; \quad \text{DEFINE } \tau \equiv RC$$


$$\frac{V_o}{V_i} = \frac{1}{1 - j\frac{1}{\omega\tau}} = \omega\tau \frac{\omega\tau + j}{1 + (\omega\tau)^2}$$

A. $\left| \frac{V_o}{V_i} \right| = \frac{\omega\tau}{[1 + (\omega\tau)^2]^{1/2}}$


B. $\phi = \tan^{-1} \left[\frac{1}{\omega\tau} \right]$

3.


A.

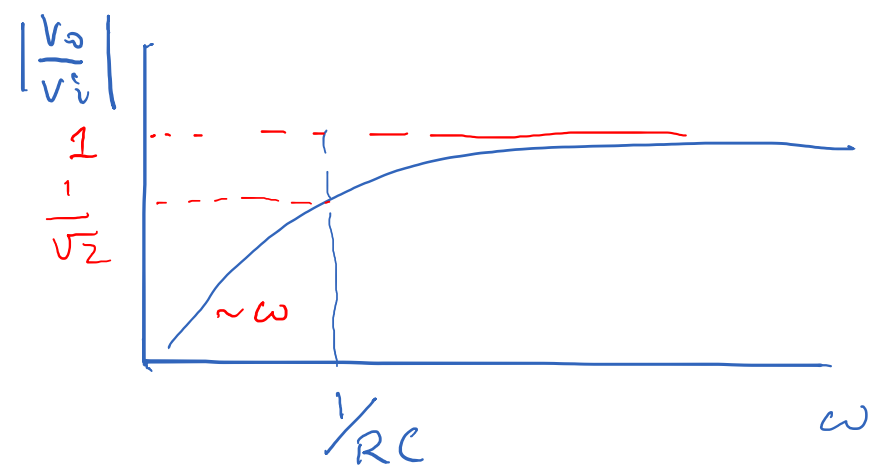

B.

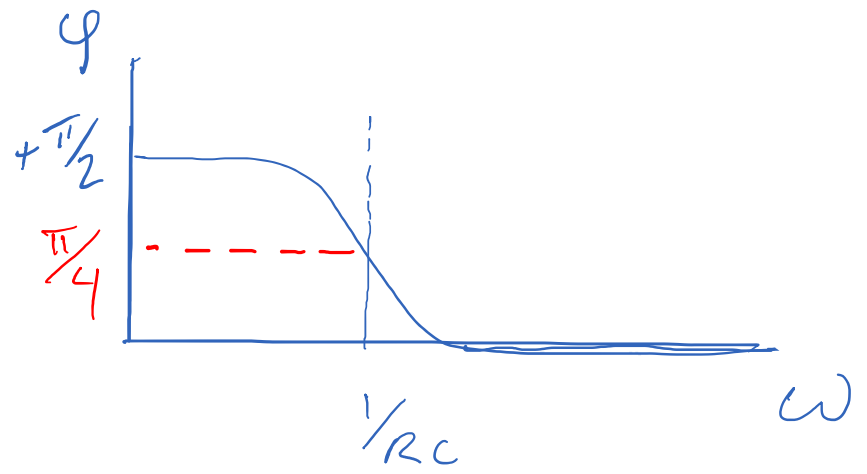


4.

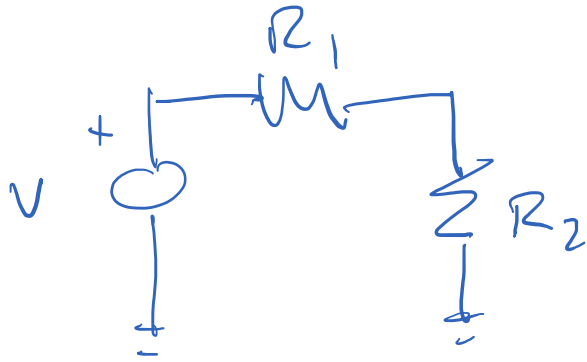

$$V_T = V_{oc} = \frac{R_2}{R_1 + R_2} V$$

$$R_T = V_{oc} / I_{sc}$$

I_{sc} ?

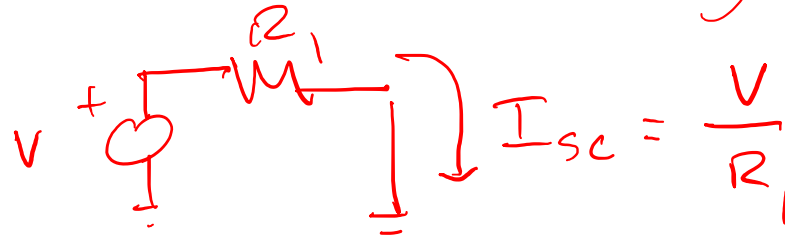



$$I_{sc} = \frac{V}{R_1}$$

$$\therefore R_T = \frac{\frac{R_2}{R_1 + R_2} V}{\left(\frac{V}{R_1}\right)}$$


$$R_T = \frac{R_1 R_2}{R_1 + R_2} = R_1 \parallel R_2$$

THEVENIN
EQUIVALENT

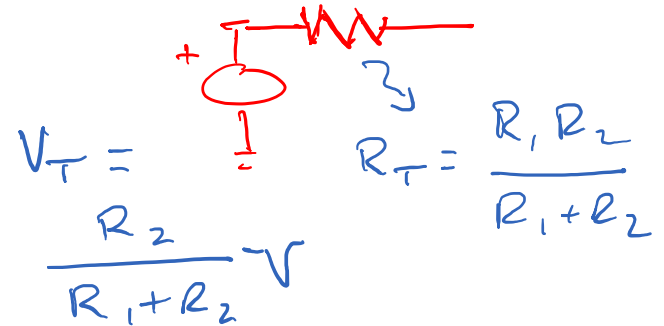

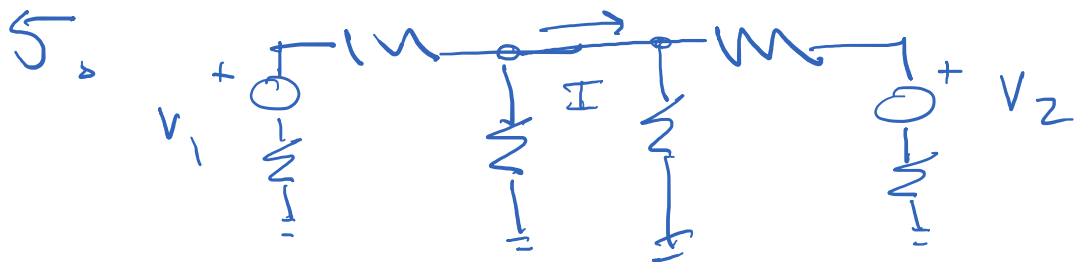

CONSIDER LEFT HALF

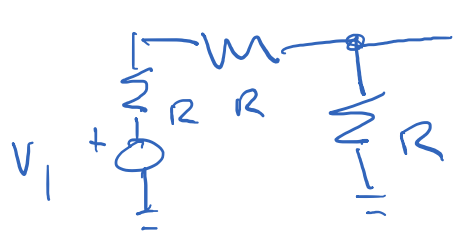


$$V_T = \frac{V_1}{3}$$

$$R_T = R \parallel 2R = \frac{2}{3} R$$

AND SIMILARLY FOR RIGHT HALF

OVER


SO CIRCUIT BECOMES

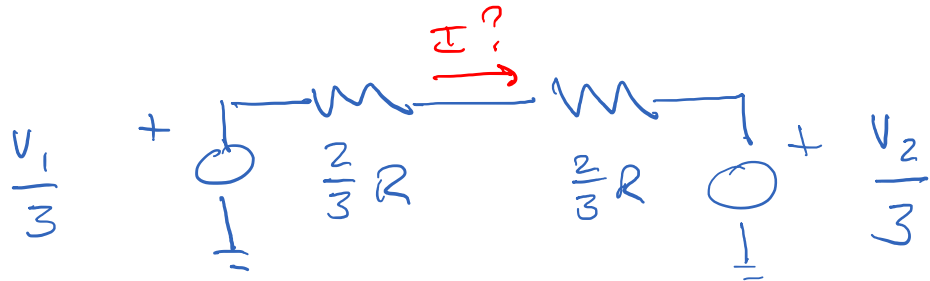

NOW, USE SUPERPOSITION TO CALCULATE PARTIAL CURRENTS


$$I_1 \neq I_2 ; I = I_1 + I_2$$

eg. , PARTIAL CIRCUIT # 1 :

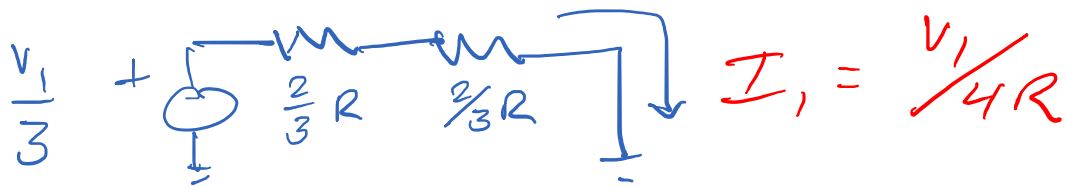

SIMILARLY, $I_2 = -\frac{V_2}{4R}$
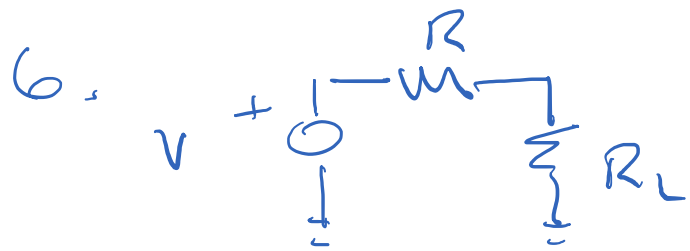
$$\begin{aligned} I &= I_1 + I_2 \\ &= \frac{1}{4R} [V_1 - V_2] \end{aligned}$$




$$P = \frac{V_L^2}{R_L} = \frac{1}{R_L} \left[\frac{R_L}{R + R_L} \right]^2 V^2$$

NEED TO MAXIMIZE $\frac{R_L}{(R + R_L)^2}$


SOLVE

$$\frac{dP}{dR_L} = 0$$
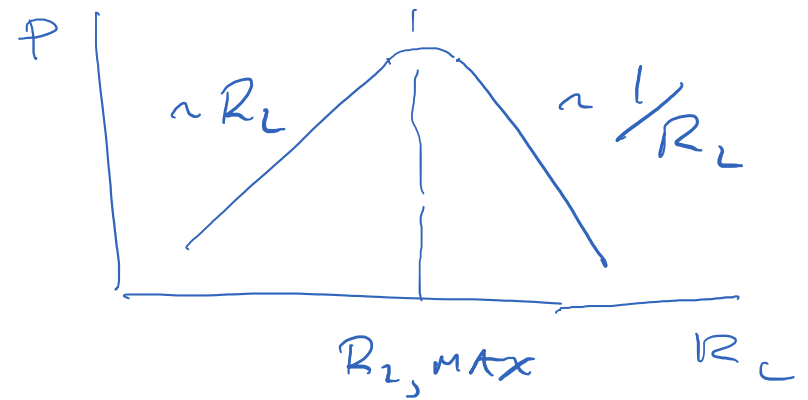
$$\frac{1}{(R + R_L)^2} - \frac{2R_L}{(R + R_L)^3} = 0 \Rightarrow \boxed{R = R_L}$$



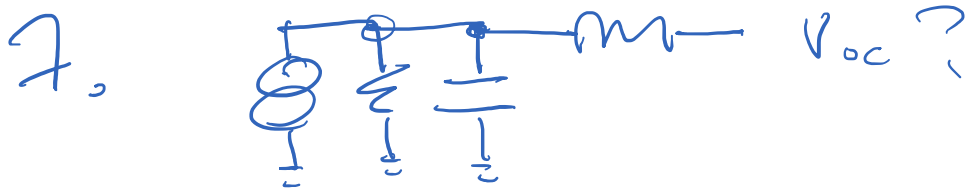
@ $R_L = R$, POWER TO LOAD IS $\frac{V^2}{4R}$ (1:1 VOLTAGE DIVIDER)



∥ (NO CURRENT THROUGH L)

$$V_{oc} = I \left(\frac{-j}{\omega_0 C} \right) = -j \frac{R}{Q} I$$

NEXT, WANT I_{sc}

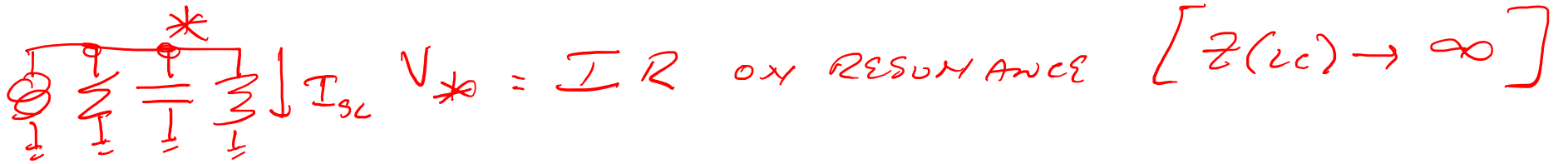

$$\therefore I_{sc} = \frac{I R}{j\omega_0 L} = -j Q I$$

NORTON EQUIVALENT: $-j Q I$ $\frac{R}{Q^2}$

NOTE
CONSERVATION
OF POWER