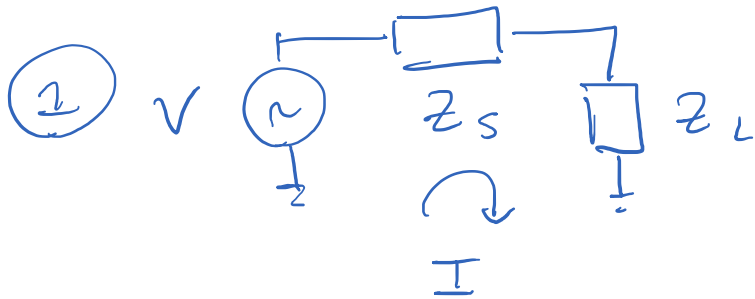


## PS 2 SOLUTIONS



WRITE  $Z_s = R_s + jX_s$

$$Z_L = R_L + jX_L$$

INSTANTANEOUS POWER TO LOAD =  $I^2 R_L$


$$I = \frac{V}{Z_s + Z_L} = \frac{V}{R_s + R_L + j(X_s + X_L)}$$

CLARLY, IMAGINARY PART OF  $Z_s + Z_L$  ONLY REDUCES CURRENT WITHOUT CONTRIBUTING TO POWER DISSIPATION IN LOAD.

CURRENT IS MAXIMIZED FOR  $X_s = -X_L$ . WITH THIS CONDITION, PROBLEM REDUCES TO USUAL POWER MATCHING WITH RESISTIVE SOURCE + LOAD. DESIRED POWER MATCH CONDITION IS A

CONJUGATE MATCH  $Z_L = Z_s^*$ .

②

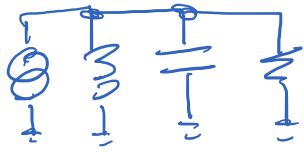

$$Y = \frac{1}{j\omega L} + j\omega C + \frac{1}{R} \equiv \frac{1}{R} + jX$$

$$V = \frac{I}{Y} = \frac{\frac{1}{R} - jX}{\frac{1}{R^2} + X^2} I$$


TAKE  $Q \gg 1 \rightarrow X \equiv \omega C - \frac{1}{\omega L} \approx \frac{2}{Z_0} \frac{\Delta}{\omega_0}$

A.  $V = \left[ \frac{1 - j2Q \frac{\Delta}{\omega_0}}{1 + 4Q^2 \left(\frac{\Delta}{\omega_0}\right)^2} \right] Q Z_0 I_0 e^{j\omega t}$


B-C. ON RESONANCE,  $I_L = -jQ I_0 e^{j\omega_0 t} = -I_C$

3

CONSIDER

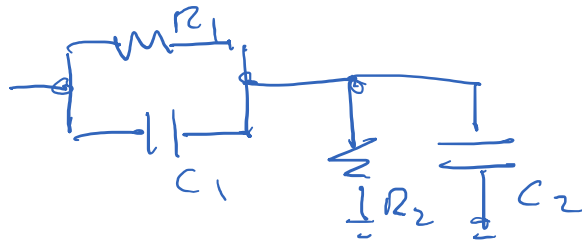

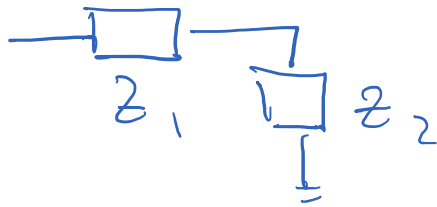THIS IS SIMPLE VOLTAGE DIVIDER  
w/ COMPLEX IMPEDANCES



PROVIDED  $Z_1 = \text{CONST} \times Z_2$ ,

WILL GET SAME VOLTAGE DIVISION @ ALL  
FREQUENCIES

$$\text{For } R \parallel C, Z = \frac{-j \frac{R}{\omega C}}{R - j\omega C} = \frac{R}{1 + j\omega RC} \quad \tau = RC \quad \xrightarrow{\text{over}}$$

CLEARLY, WE WANT  $R_1 C_1 = R_2 C_2$   
IN ORDER TO GET VOLTAGE DIVISION THAT IS  
INDEPENDENT OF FREQUENCY.

TO HAVE 10x DIVISION, REQUIRE

$$R_1 = 9 R_2$$

$$C_1 = \frac{1}{9} C_2$$

$$\therefore R_1 = 9 \text{ M}\Omega, C_1 = 13 \text{ pF}$$

$$Z_{in} = Z_1 + Z_2 = (R_1 + R_2) \frac{1}{1 + j\omega\tau} ; \tau = 1 \mu\Omega \cdot 120 \text{ pF}$$

$$= 10 \text{ M}\Omega \frac{1}{1 + j\omega\tau} \quad \text{LOOKS LIKE } 10 \text{ M}\Omega \parallel \frac{1}{j\omega} 12 \text{ pF}$$