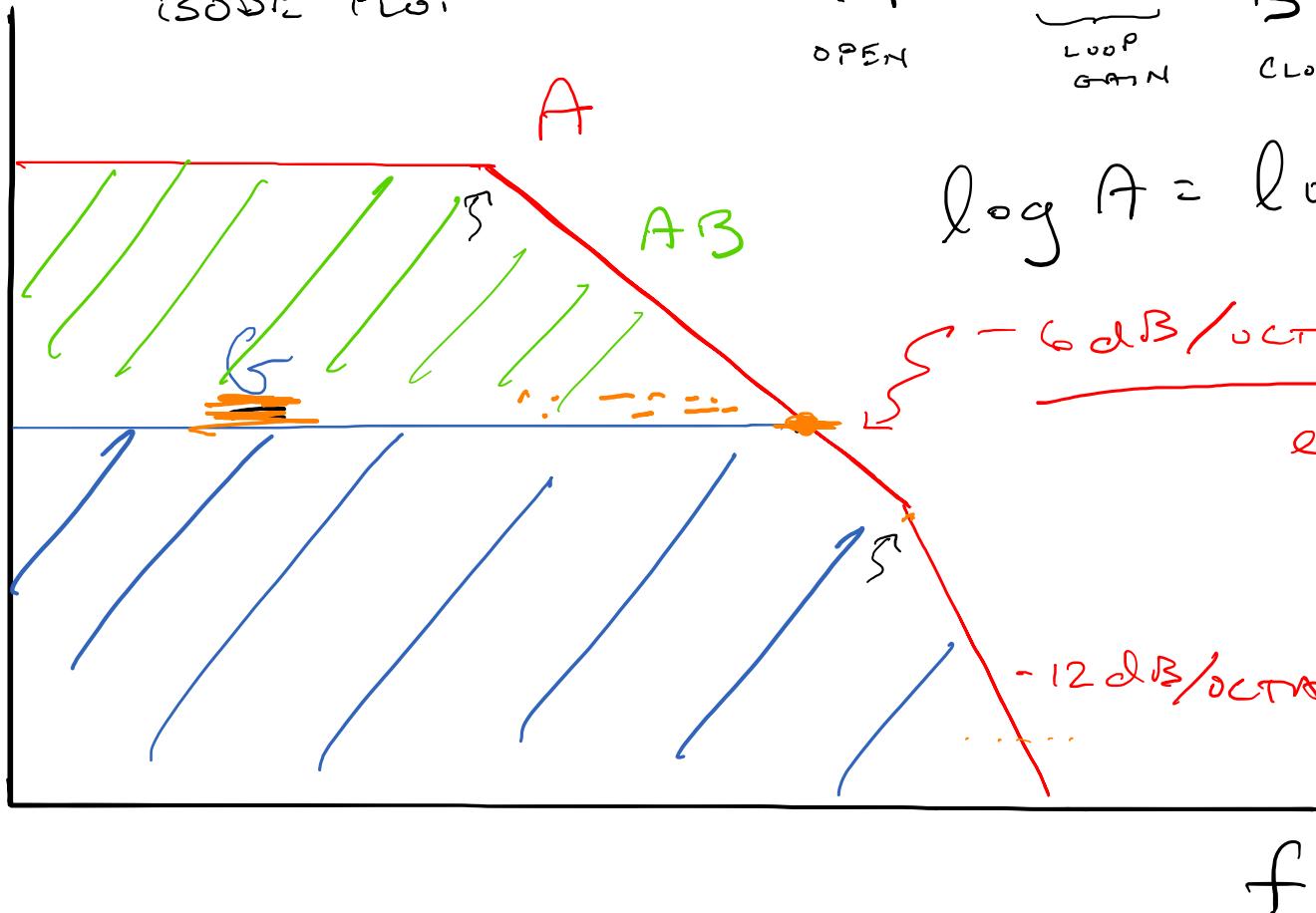


## OP AMP STABILITY

"BODE PLOT"

GAIN.  
e.g.  
 $10\log_{10}|A|^2$



$$A = \underbrace{(AB)}_{\substack{\text{OPEN} \\ \text{LOOP} \\ \text{GAIN}}} \frac{1}{\underbrace{B}_{\substack{\text{CLOSED}}}} = (AB) G$$

$$\log A = \log (AB) + \log G$$


$-6 \text{ dB/octave}$

e.g.  $\frac{1}{f^2}$

SINGLE-POLE  
LOW-PASS


$-12 \text{ dB/octave}$ .

## OP AMP STABILITY

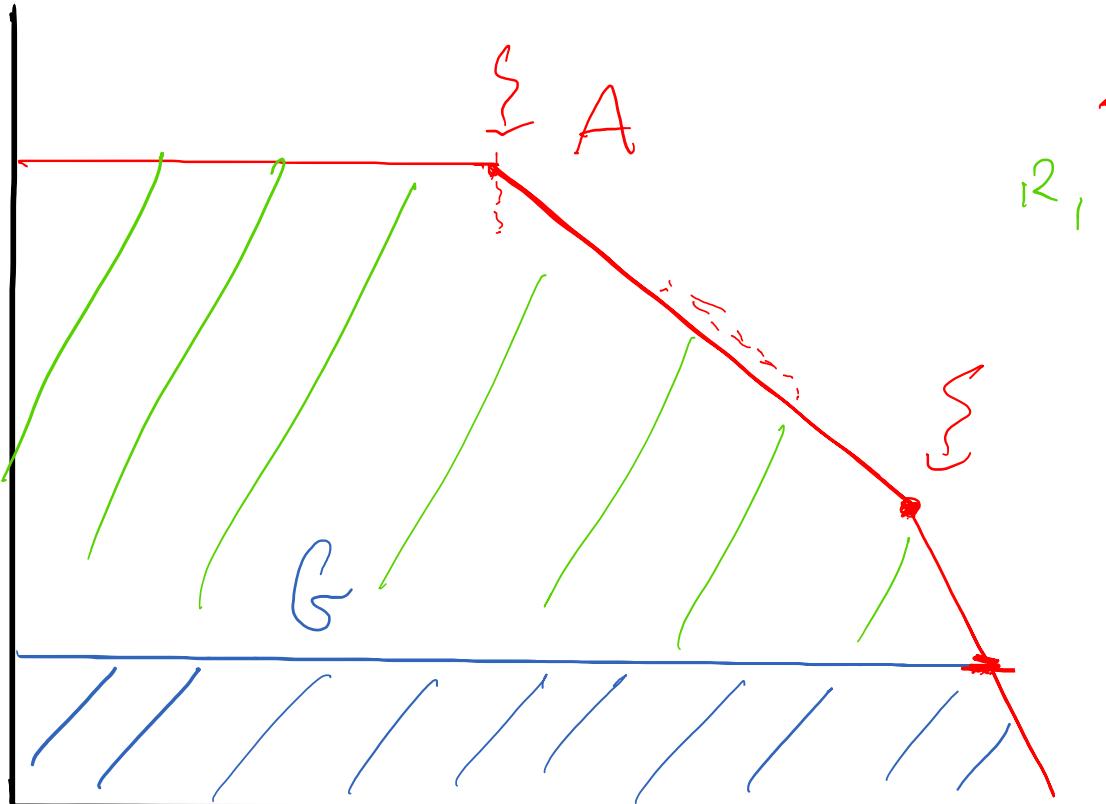

WORST CASE:

FOLLOWER:  $G = 1$

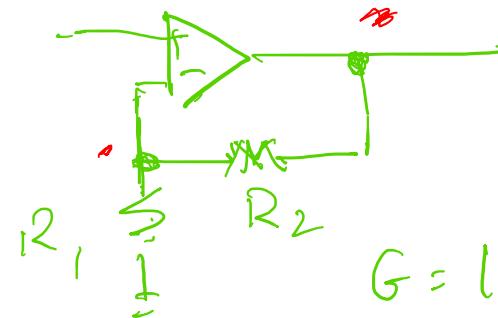

$R_1$

$R_2$

$$G = 1 + \frac{R_2}{R_1}$$


"PHASE MARGIN"

HOW FAR ACCUM. PHASE  
IN FB LOOP IS FROM  
 $-180^\circ$  @ POINT  
WHERE LOOP GAIN


$f$

= 1.


## OP AMP STABILITY

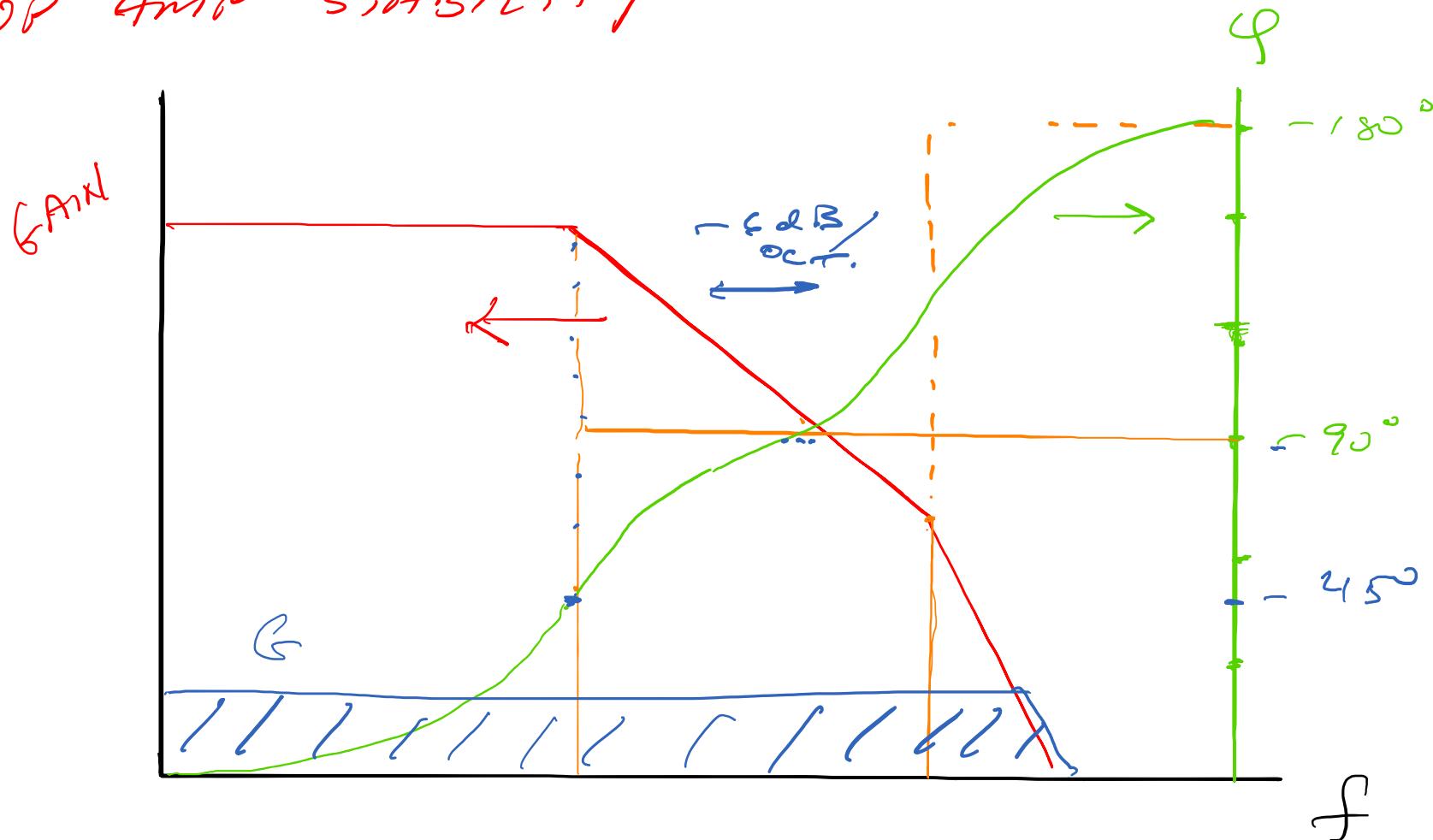



## OP AMP STABILITY

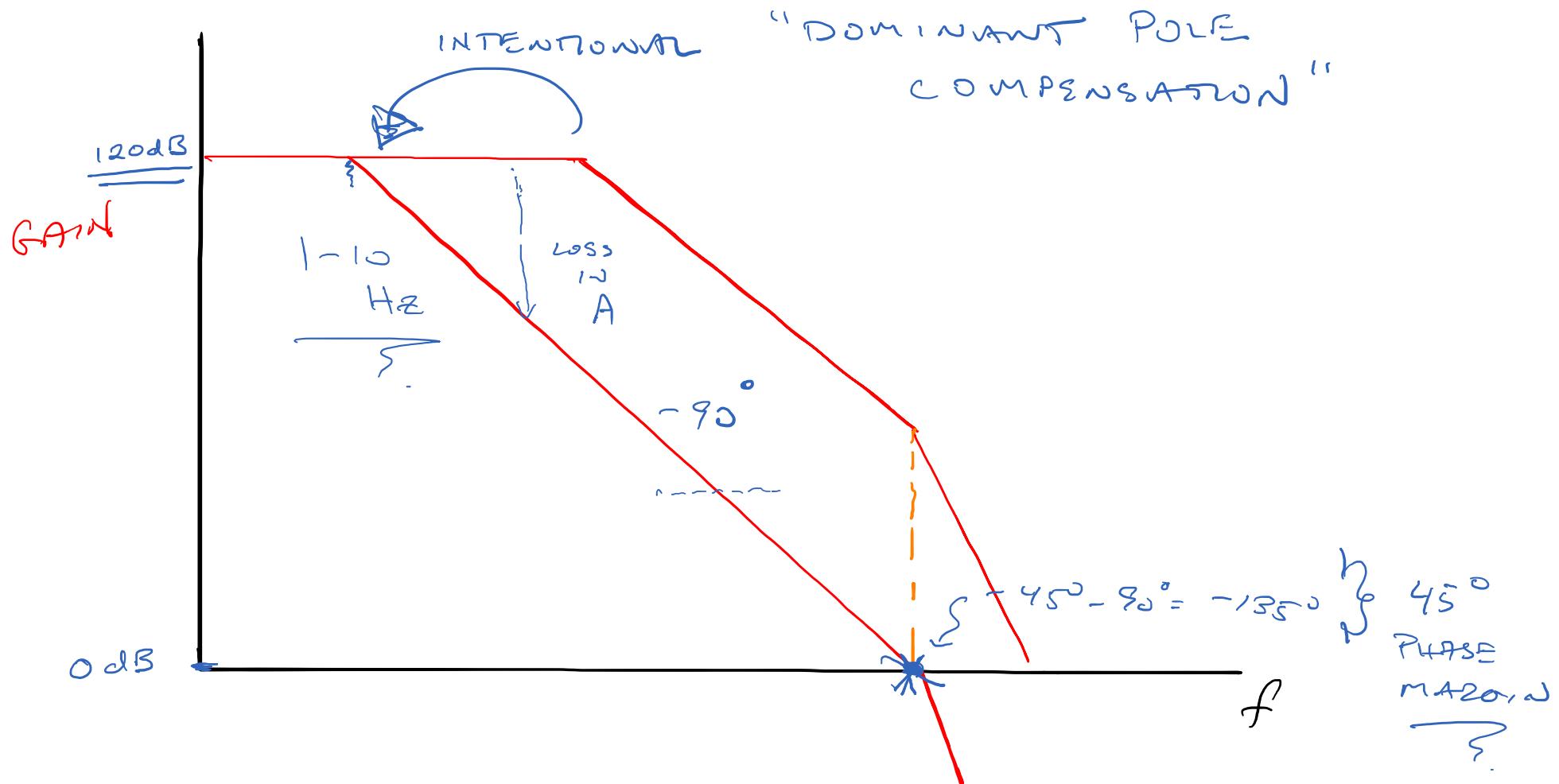

## OP AMP STABILITY

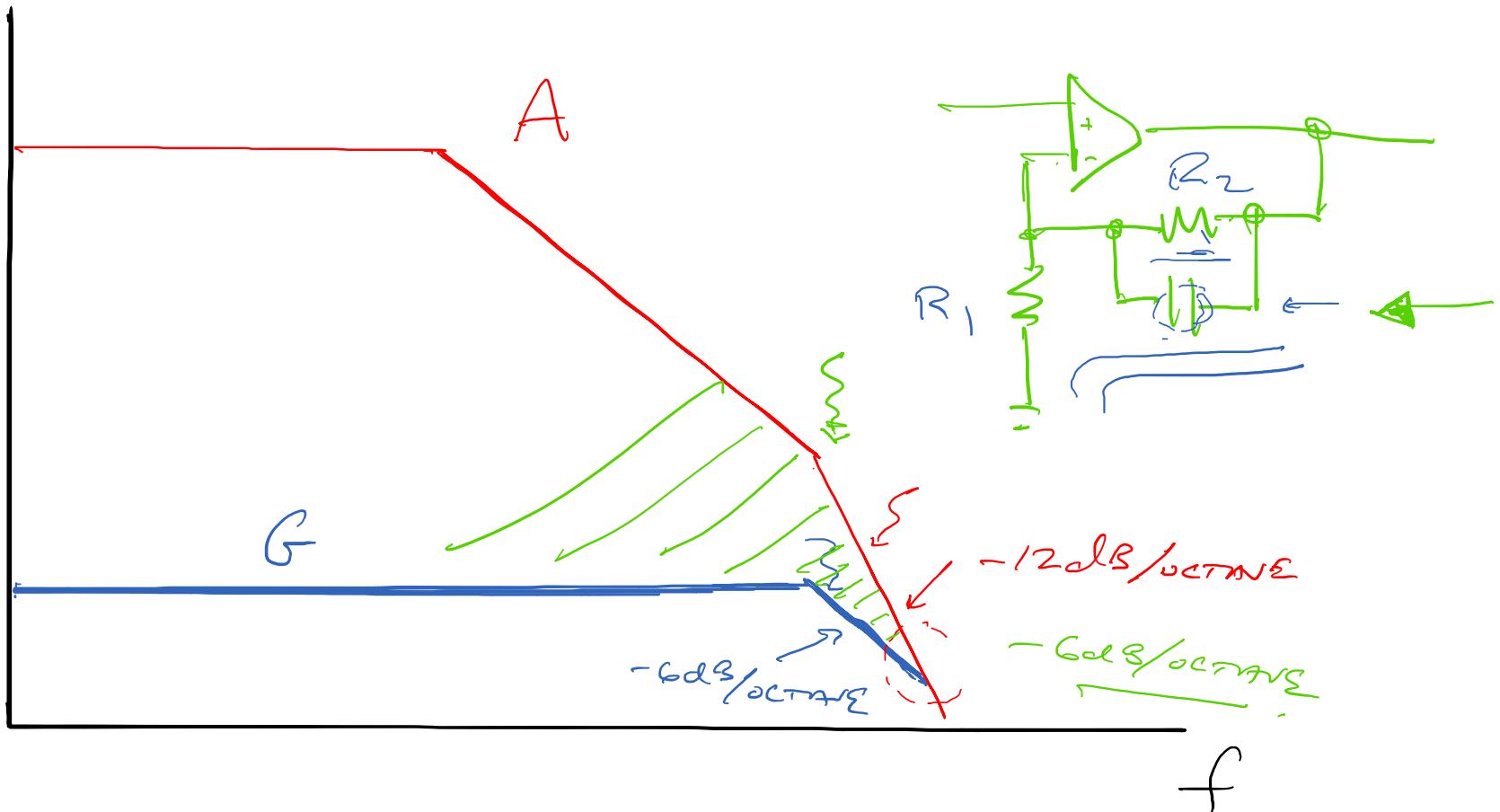

## OP AMP STABILITY

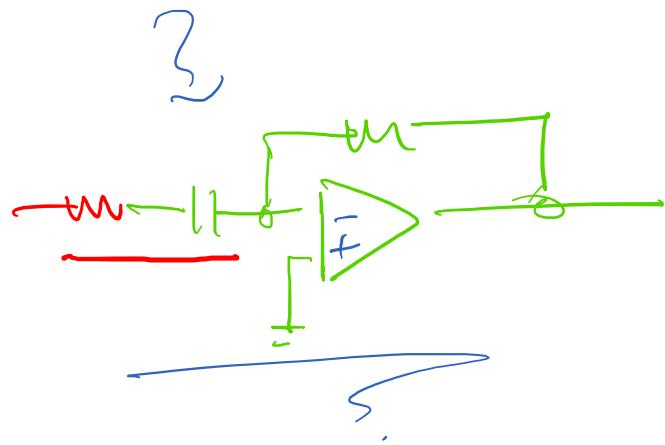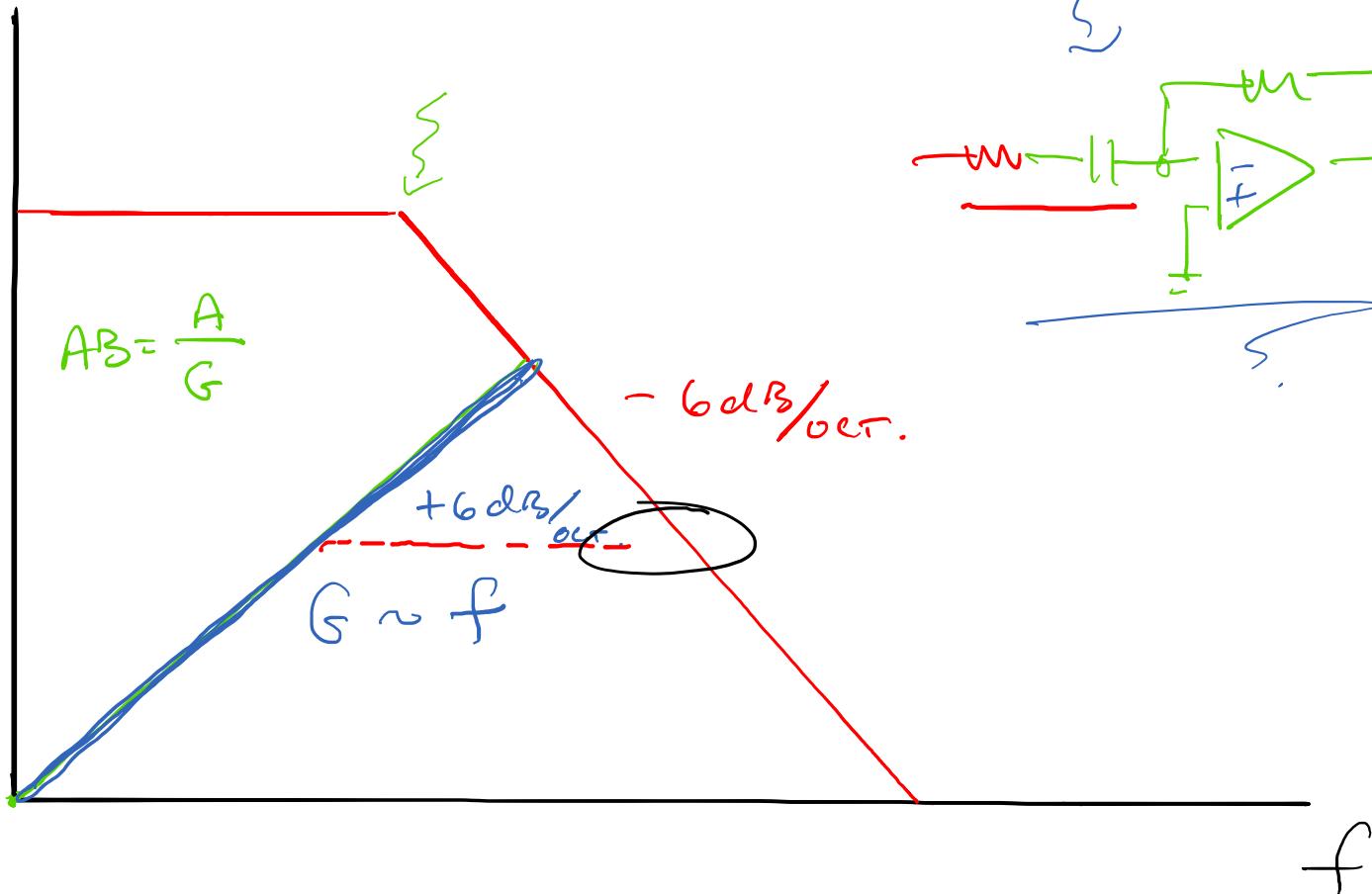

## Fourier Theory

Consider periodic signal

$$V(t \pm T) = V(t)$$

Fundamental (Angular) Frequency  $\omega_0 = \frac{2\pi}{T}$

$$\underline{V(t)} = \frac{a_0}{2} + \sum_{n=1}^{\infty} \left[ \underbrace{a_n}_{?} \cos n\omega_0 t + \underbrace{b_n}_{?} \sin n\omega_0 t \right] \dots$$

use orthogonality of sin/cos to solve

for  $a_n, b_n$

$$\int_{-\frac{T}{2}}^{\frac{T}{2}} \cos n\omega_0 t \cos m\omega_0 t dt = \frac{T}{2} \delta_{nm}$$

$$\int_{-\frac{T}{2}}^{\frac{T}{2}} \sin n\omega_0 t \sin m\omega_0 t dt = \frac{T}{2} \delta_{nm}$$

$$\int_{-\frac{T}{2}}^{\frac{T}{2}} \sin n\omega_0 t \cos m\omega_0 t dt = 0$$

$$a_n = \frac{2}{T} \int_{-T/2}^{T/2} v(t) \cos nw_0 t \, dt$$

$$b_n = \frac{2}{T} \int_{-T/2}^{T/2} v(t) \sin nw_0 t \, dt$$

Consider odd/even symmetry of waveform

ODD: only sin components

EVEN: only cos components

or// use complex notation

$$\underline{v(t)} = \sum_{n=-\infty}^{\infty} \underline{c_n e^{jn\omega_0 t}} \dots$$

$$c_{-n} = c_n^*$$

Ensures  $v(t)$  real

ORTHOGONALITY:

$$\int_{-\frac{T}{2}}^{\frac{T}{2}} e^{j(n-m)\omega_0 t} dt = T \delta_{nm}$$

$$\Rightarrow c_n = \frac{1}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} v(t) e^{-jn\omega_0 t} dt$$

Example




$$c_n = \frac{2}{T} \int_0^{T/2} V_0 e^{-jn\omega_0 t} dt$$

$$c_n = \frac{2}{T} V_0 \left( \frac{-1}{jn\omega_0} \right) \left( e^{-jn\omega_0 \frac{T}{2}} - 1 \right) = \frac{2 V_0}{\pi j} \frac{1}{n}$$

$$\boxed{v(t) = \frac{2 V_0}{\pi j} \sum_{n \text{ odd}} \frac{1}{n} e^{jn\omega_0 t}}$$
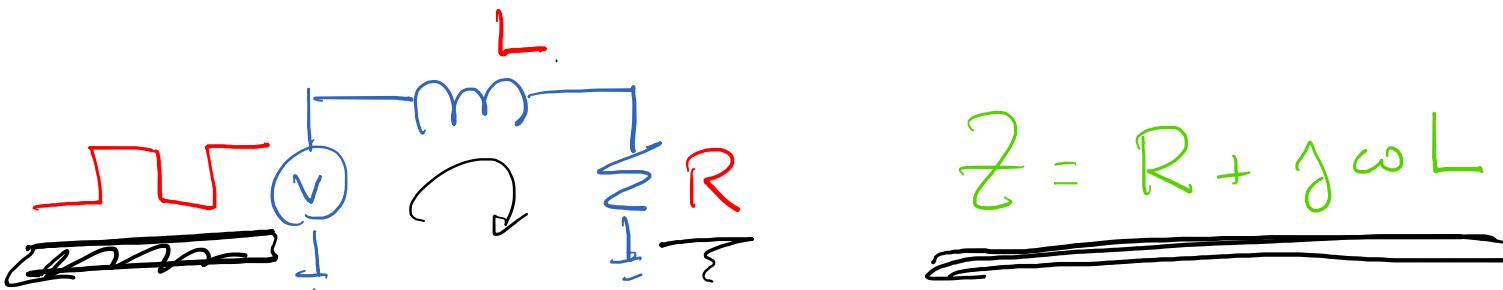
$$e^{jx} = \cos x + j \overline{\sin x}$$




Solve for  $V_R$

$$I = \frac{V}{Z} = \frac{2V_0}{\pi j} \left\{ \frac{1}{n[R+jn\omega_0 L]} e^{jn\omega_0 t} \right\}$$

$$V_R = \frac{2V_0}{\pi} \left\{ \frac{1}{-n^2\omega_0^2 + jn} e^{jn\omega_0 t} \right\} ; \tau = \frac{1}{R}$$

TAKE  $\omega_0 \tau \gg 1$
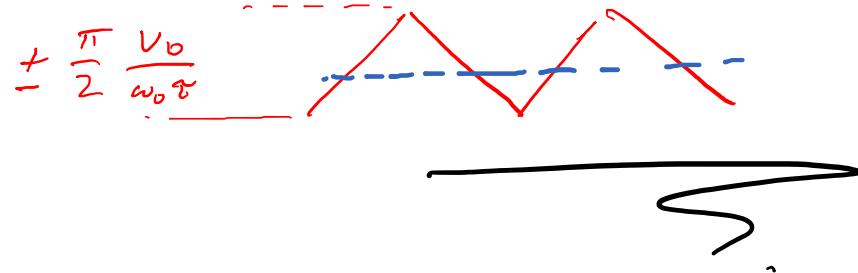
$$V_R \approx \frac{2 V_0}{\pi} \sum_{n \text{ odd}} \left( -\frac{1}{n^2 \omega_0 \tau} \right) e^{j n \omega_0 t}$$



$$\pm \frac{\pi}{2} \frac{V_0}{\omega_0 \tau}$$

$$V_R \approx \frac{1}{T} \int v_{in} dt$$

## Fourier Transform

$$v(t) = \sum c_n e^{j n \omega_0 t} \quad \text{let } \omega = n \omega_0 ;$$

TAKING  $\omega_0 \rightarrow 0$  with

$$v(t) = \sum c_n e^{j \omega t} \frac{T}{2\pi} \Delta \omega \quad \frac{T \Delta \omega}{2\pi} = 1$$

$$\underbrace{v(t)}_{\tilde{v}} = \frac{1}{2\pi} \int_{-\infty}^{\infty} \tilde{c}_n T e^{j \omega t} d\omega$$

$c_n \cdot T \leftrightarrow \tilde{v}(\omega)$

Fourier Transform

$$v(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} \tilde{v}(\omega) e^{j\omega t} d\omega$$

Fourier  
X'form


$$\tilde{v}(\omega) = \int_{-\infty}^{\infty} v(t) e^{-j\omega t} dt$$

INVERSE  
F.T.

$$v(t) = V_0 e^{-t^2/\tau^2}$$

Gauss, A&D

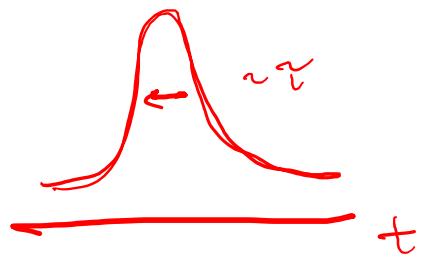


$$v(t) = V_0 e^{-|t|/\tau}$$

Exp. Decay


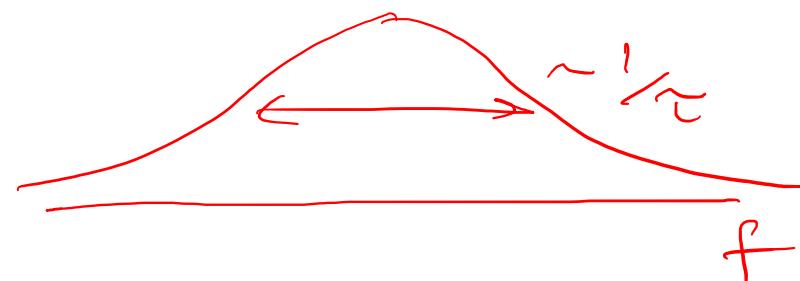
$$\tilde{v}(\omega) = \sqrt{\pi} V_0 \tau e^{-(\omega/\tau)^2}$$




$$\tilde{v}(\omega) = \frac{2 V_0 \tau}{1 + j \omega \tau}$$

Lorentzian  
 $\tau?$

## EXAMPLE

ARBITRARY

$$\underline{I}(t)$$

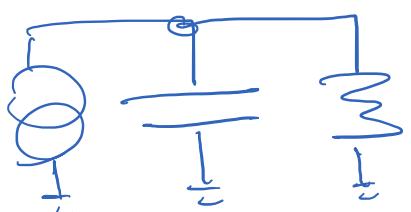

$$h \quad \text{mode @ } \omega_0 = \frac{1}{\sqrt{LC}}$$

ENERGY coupled to mode ?

FIRST  
TAKE

$$\underline{I}(t) = \sum Q \delta(t), \quad \text{LINEAR RESPONSE THEORY.}$$

$$\underline{V}(t) = \frac{Q}{C} \cos \omega_0 t, \quad \text{FREEx's function / IMPULSE RESPONSE.}$$

For ARBITRARY  $\underline{I}(t)$ ,

$$\underline{V}(t) = \frac{1}{C} \int_{-\infty}^t \underline{\underline{I}}(t') \cos [\omega_0 (t - t')] dt'.$$

$$\underline{V}(t) = \frac{1}{C} \operatorname{Re} \left\{ e^{j\omega_0 t} \int_{-\infty}^t I(t') e^{-j\omega_0 t'} dt' \right\}$$

Take  $t \rightarrow \infty$ . looks like current goes to zero  $I(t) \rightarrow 0$

→ ENERGY STORED IN MODE?

$$\underline{E} = \frac{1}{2} C V_{\max}^2 = \frac{1}{2C} | \tilde{I}(\omega_0) |^2$$

looks like  
current energy  
 $\sim \frac{Q^2}{2C}$ .

DIMENSIONALITY,

$$\tilde{I}(\omega_0) \rightarrow Q$$