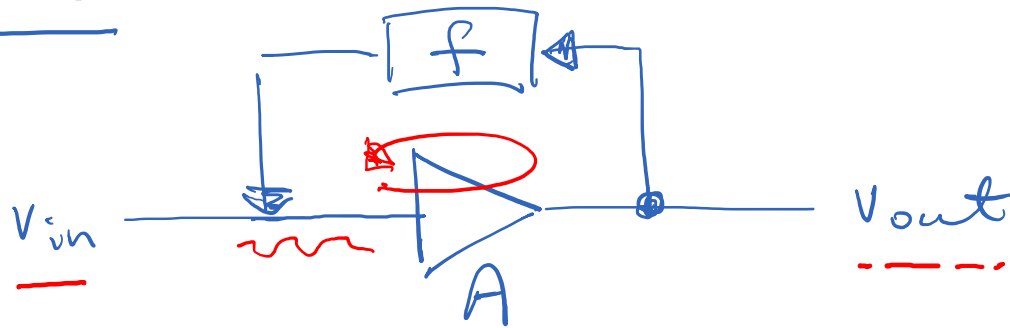


# OSCILLATORS




→ OPEN LOOP GAIN  $A$

CLOSED LOOP GAIN  $\frac{A}{1+Af} \approx \frac{1}{f}$


→ LOOP GAIN  $Af$

→ STABLE, SELF-SUSTAINING OSCILLATION FOR  $Af = 1$   
 $|Af| = 1$   $\nabla$  PHASE SHIFT  $\rightarrow 0^\circ$



# WIEN BRIDGE OSCILLATOR

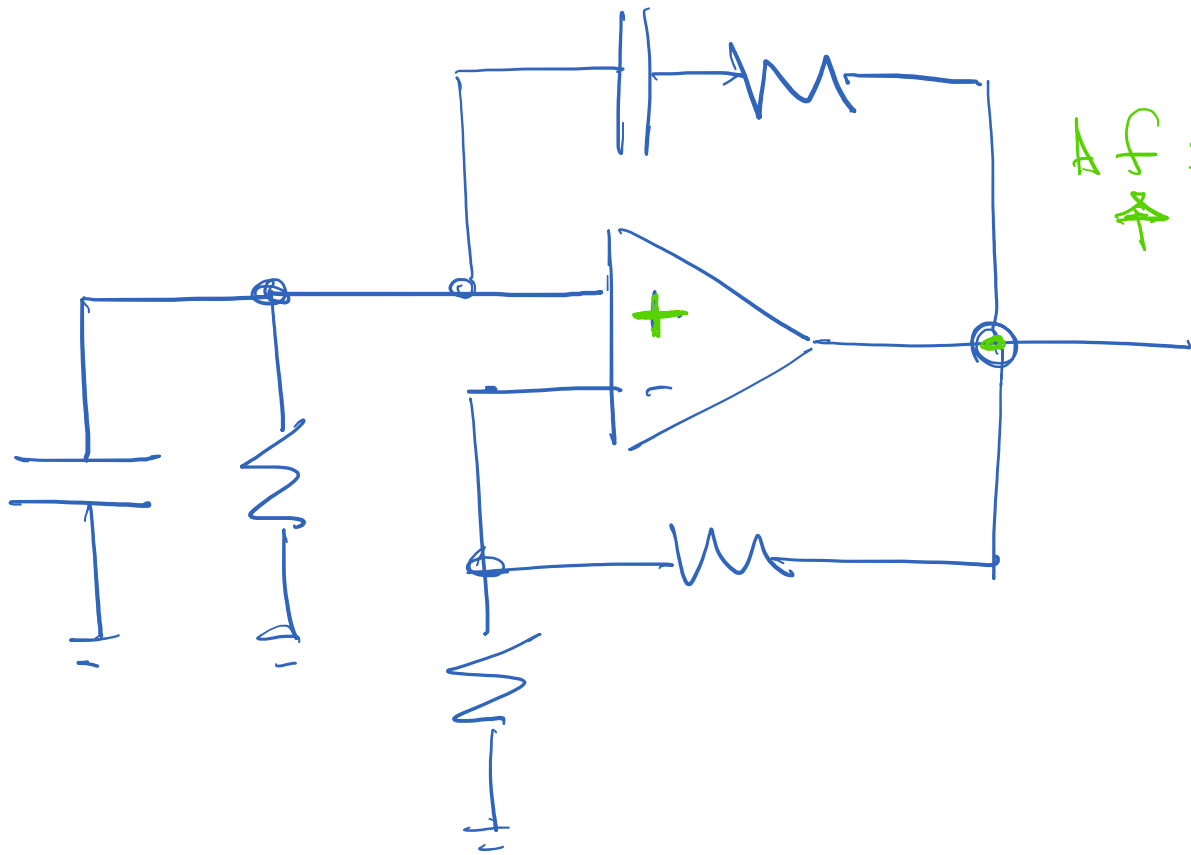

AF  
→  
||  
↑  
.

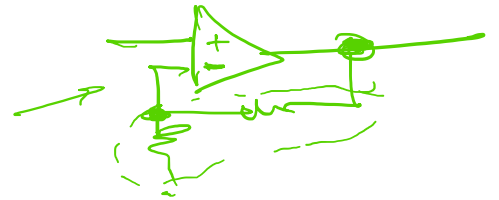


# WIEN BRIDGE OSCILLATOR

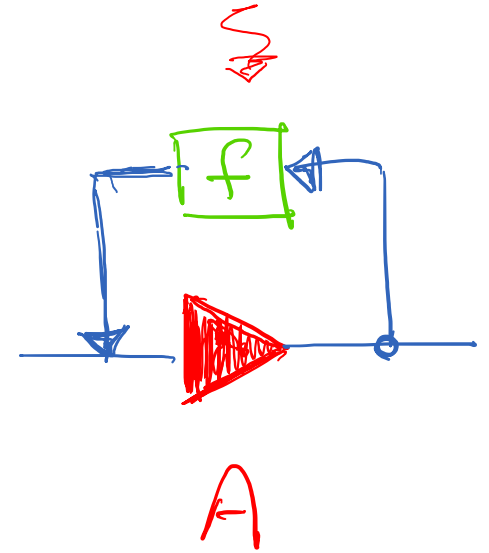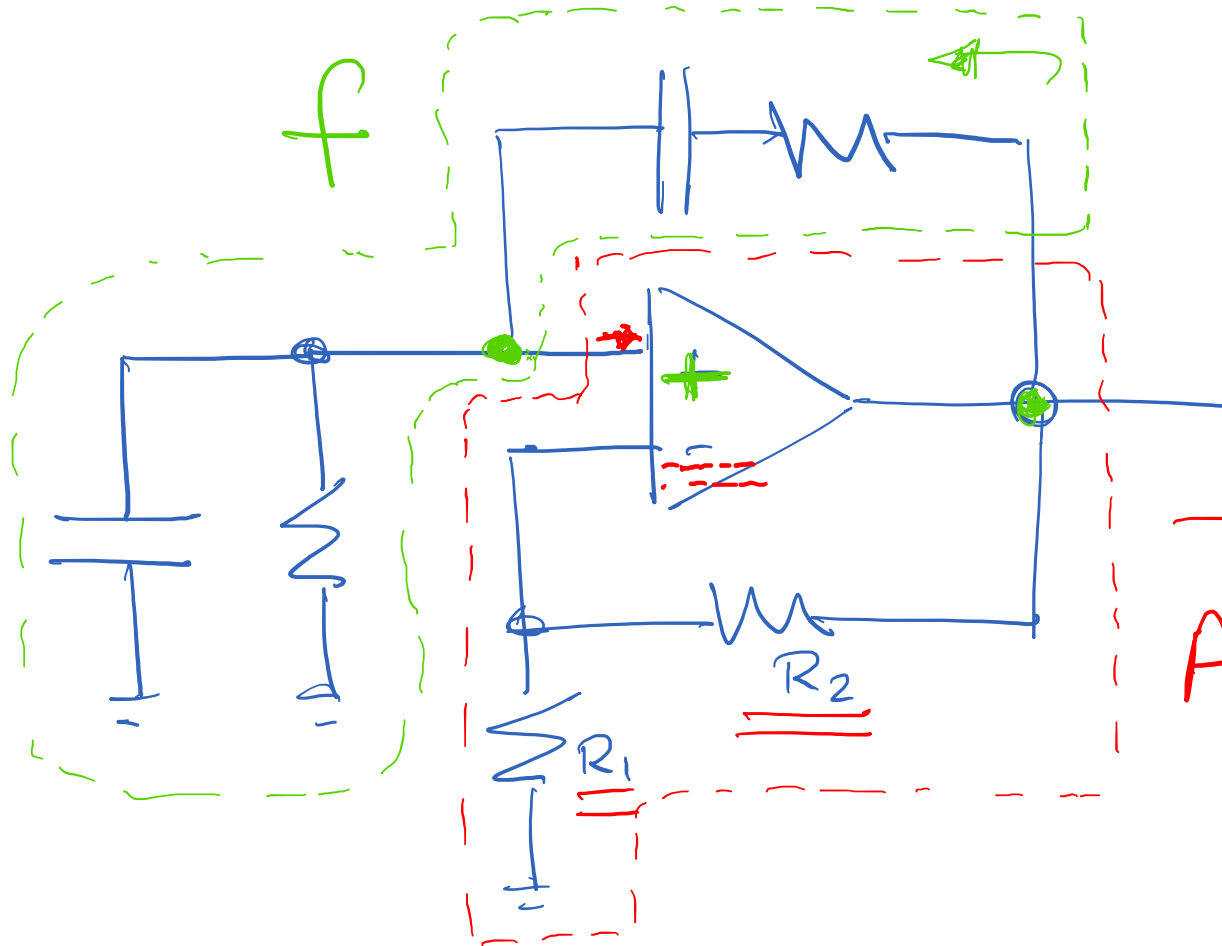

$$A = 1 + \frac{R_2}{R_1}$$


# FEEDBACK NETWORK

$\mu = RC$

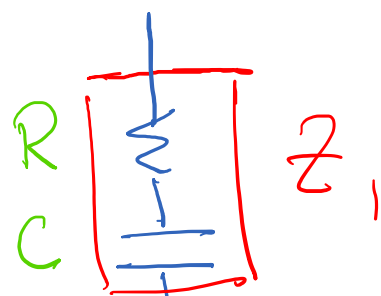

$$f = \frac{z_2}{z_1 + z_2}$$
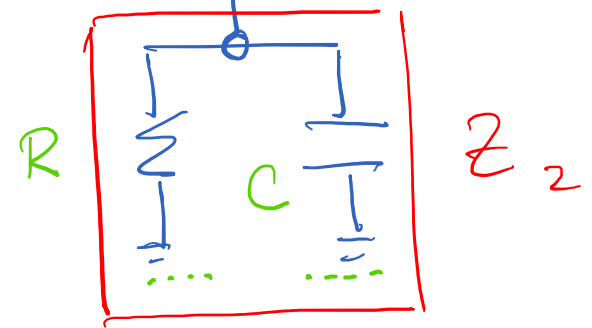
$$z_1 = R - \frac{\delta}{\omega C} = R \left[ 1 - \frac{\delta}{\omega RC} \right]$$




$$z_2 = \left[ \frac{1}{R} + j\omega C \right]^{-1} = \frac{R}{1 + j\omega RC}$$

$$f = \frac{1}{3 + j(\omega RC - \frac{1}{\omega RC})}$$

at  $\omega RC = 1$

$$f = \frac{1}{3}$$


# WIEN BRIDGE OSCILLATOR

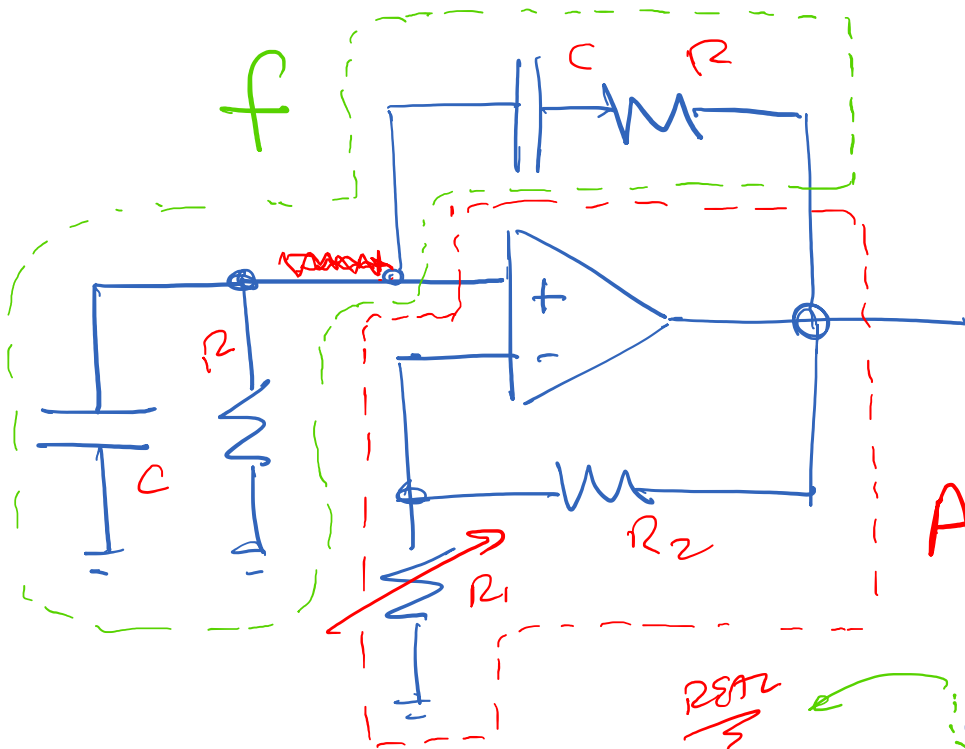

$A = 1 + \frac{R_2}{R_1}$   
 NEED

$A \cdot f = 1$

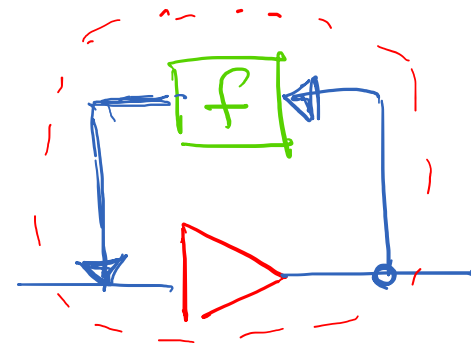How to ARRANGE?  
 REAL @  $\omega = 1/RC$




A

WEE

A=3

# ELECTROTHERMAL FEEDBACK

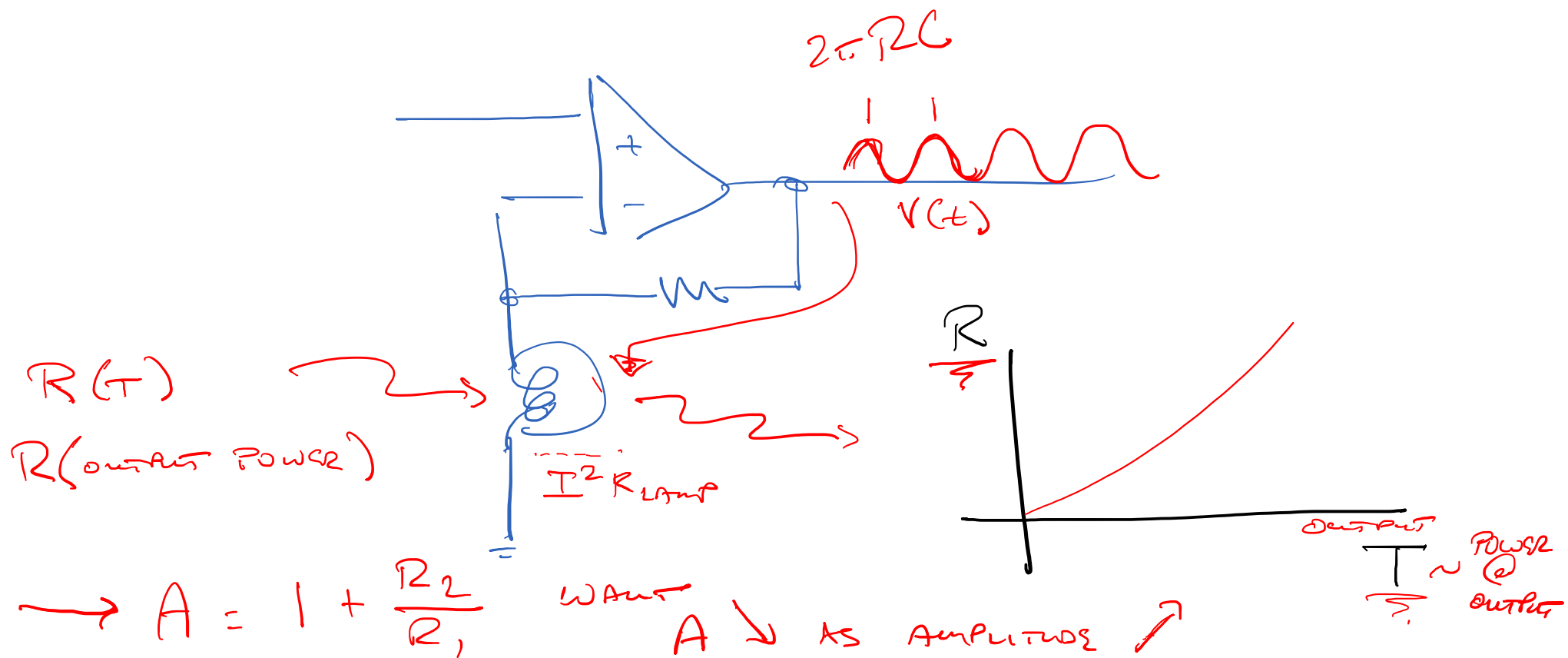

# ALTERNATIVE WAY TO STABILIZE GAIN



$R_2$   
CONTROL  
AMPLITUDE  
@ OUTPUT


$$A = 1 + \frac{R_2}{R_1}$$

SS

$$A = 3$$

P → n


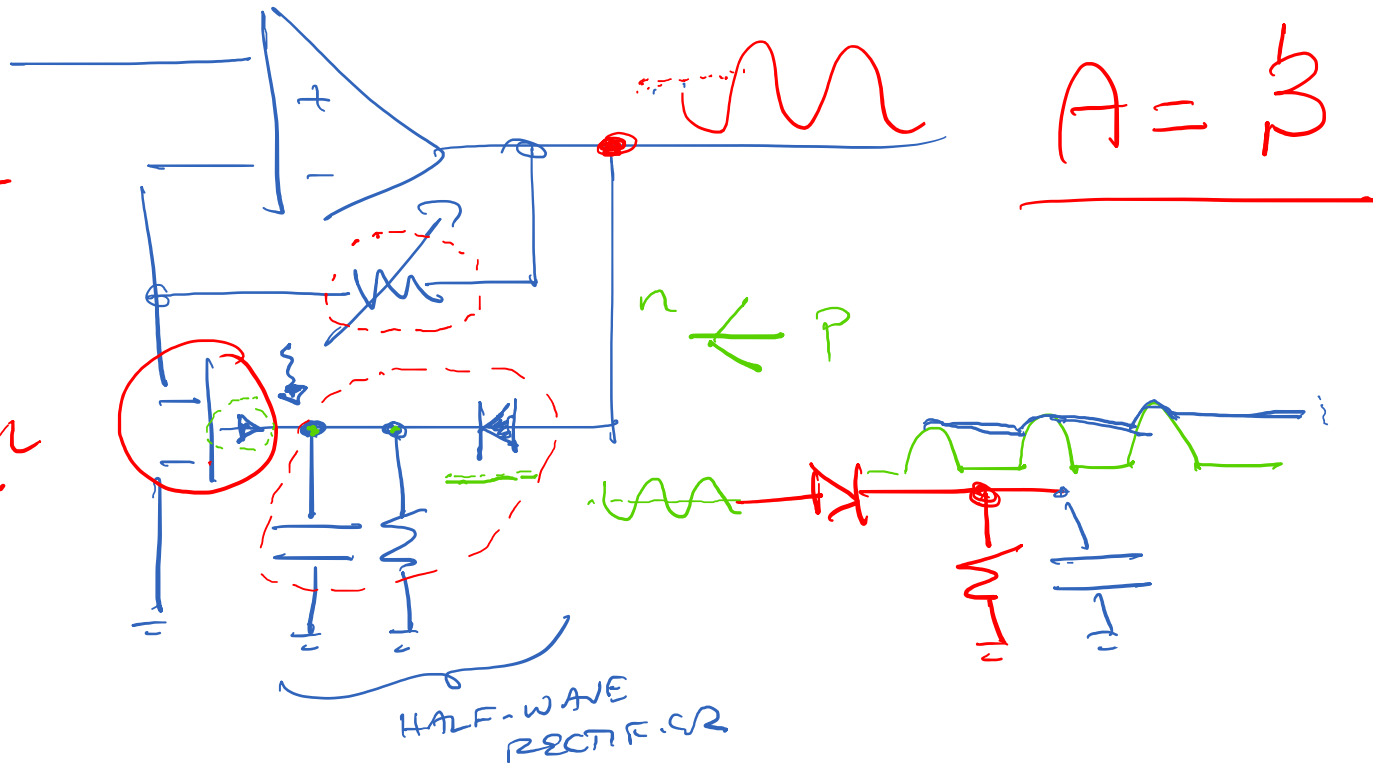
P-CHANNEL  
JFET  
AS  
VARIABLE  
RESISTOR





HALF-WAVE  
RECTIFIER

# P-channel JFET

BIAS  
NEGATIVE  
D WRT S

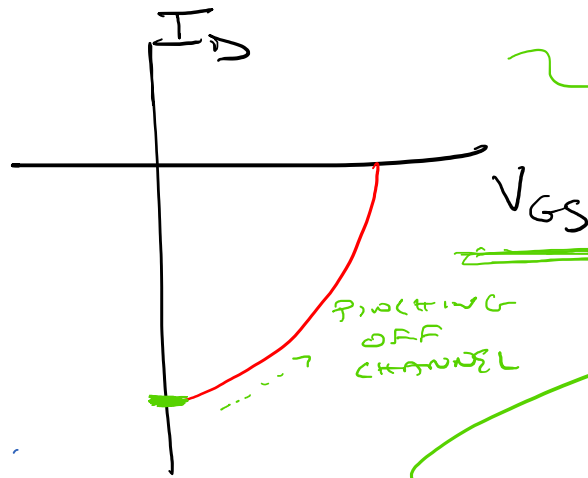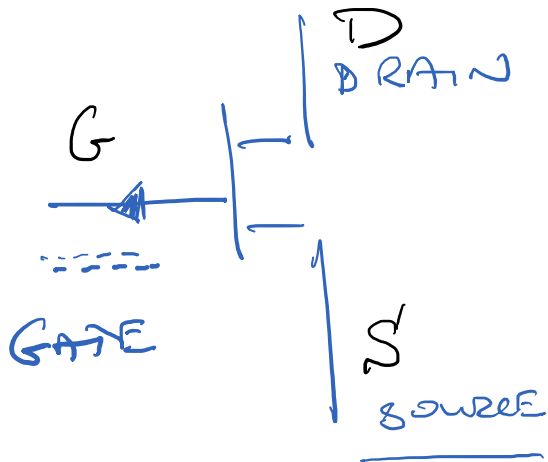

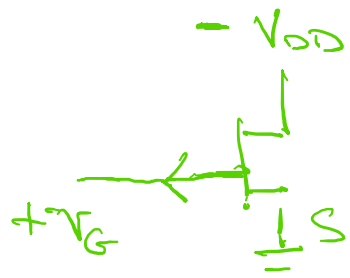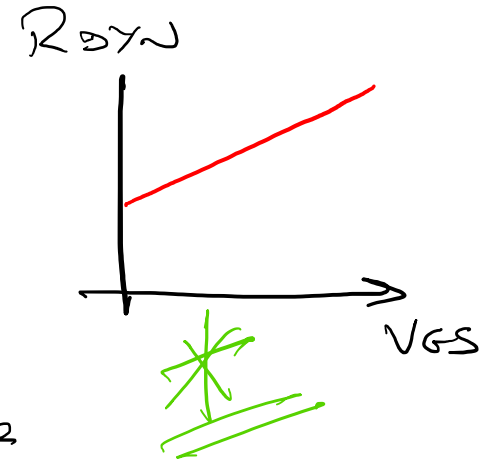
$$g_f = \frac{\partial I_D}{\partial V_{GS}}$$






# ALTERNATIVE WAY TO STABILIZE GAIN

---

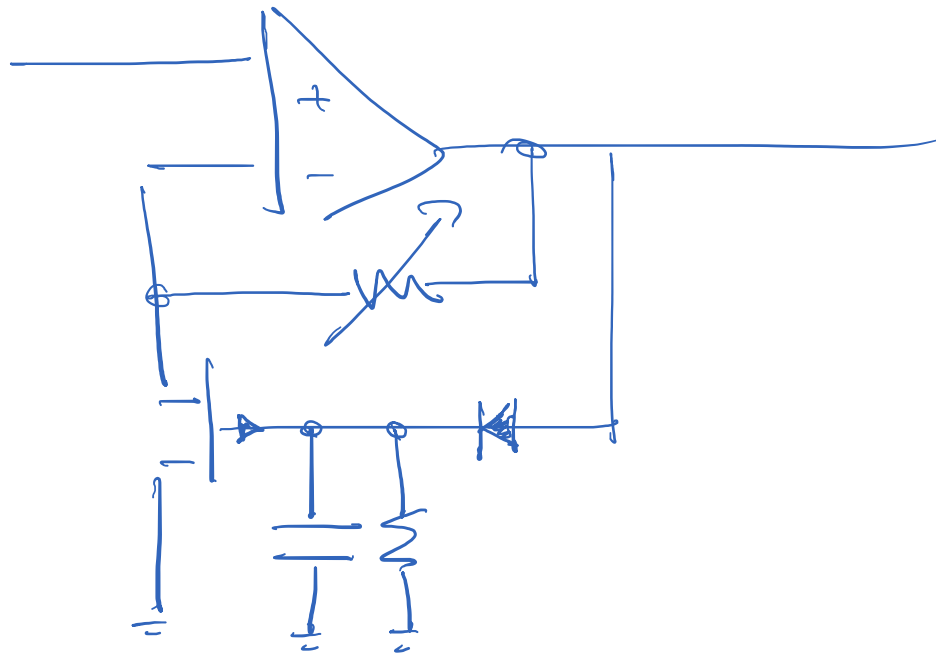

# Сомпаратюр / 2 АТЧ

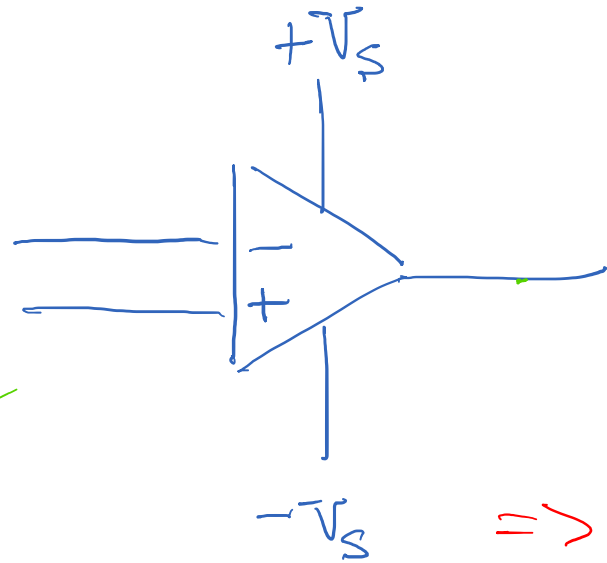


$$v_{out} = A[v_+ - v_-]$$

$A \gg 1$



$\Rightarrow$  output either @

$$+V_s \quad [F_{02} \quad \underline{v_+ > v_-}]$$
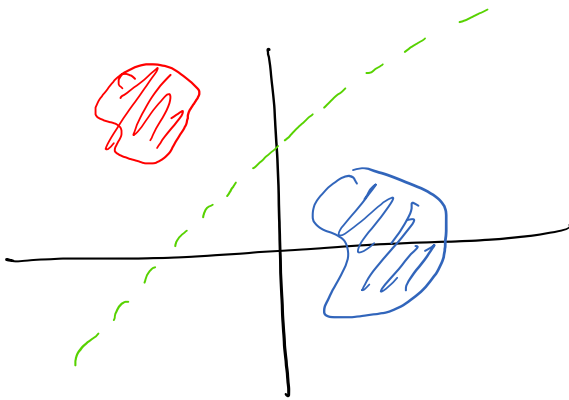
$$-V_s \quad [F_{02} \quad \underline{v_+ < v_-}]$$




NAIVE APPROACH.

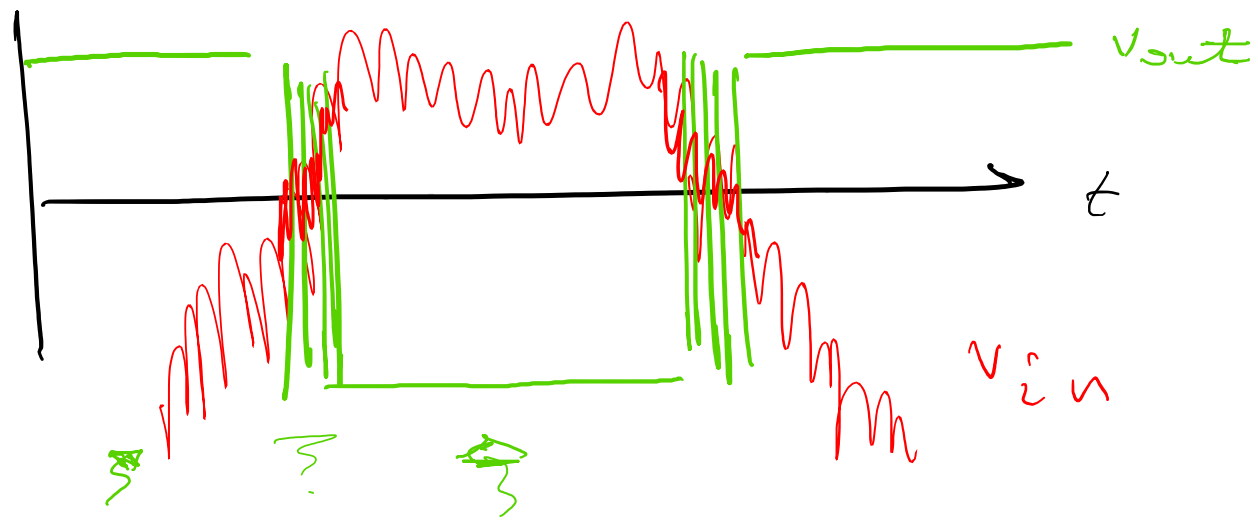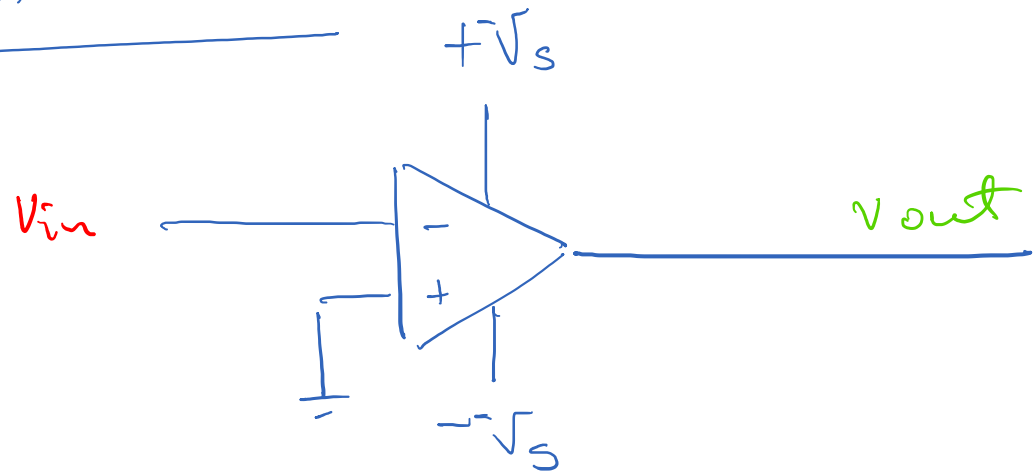

# BETTER APPROACH

LOOKS LIKE NON-INVERTING AMP.

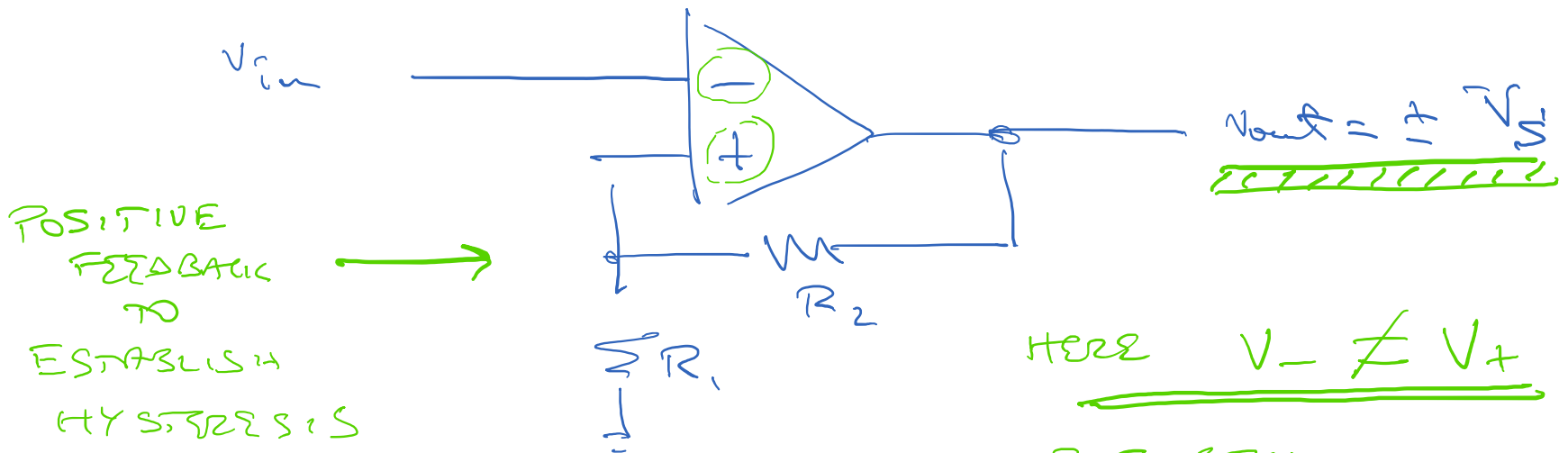


BUT. STILL,  
 INPUTS DONT  
 NO CURRENT.


THRESH. DETECTOR.


$$V_{TH} = \pm V_s \cdot \frac{R_1}{R_1 + R_2}$$

$V_+$

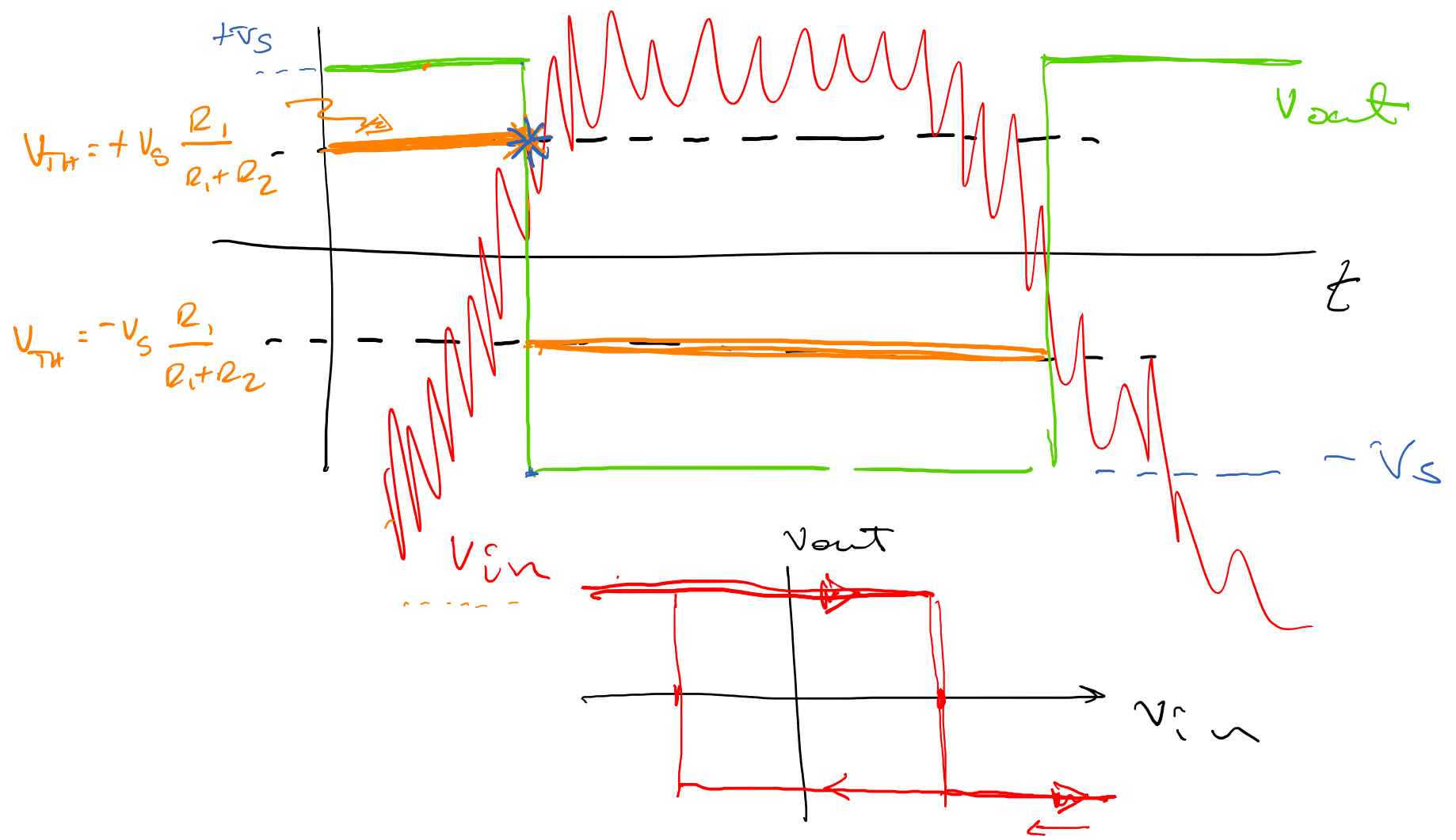

# RELAXATION OSCILLATOR

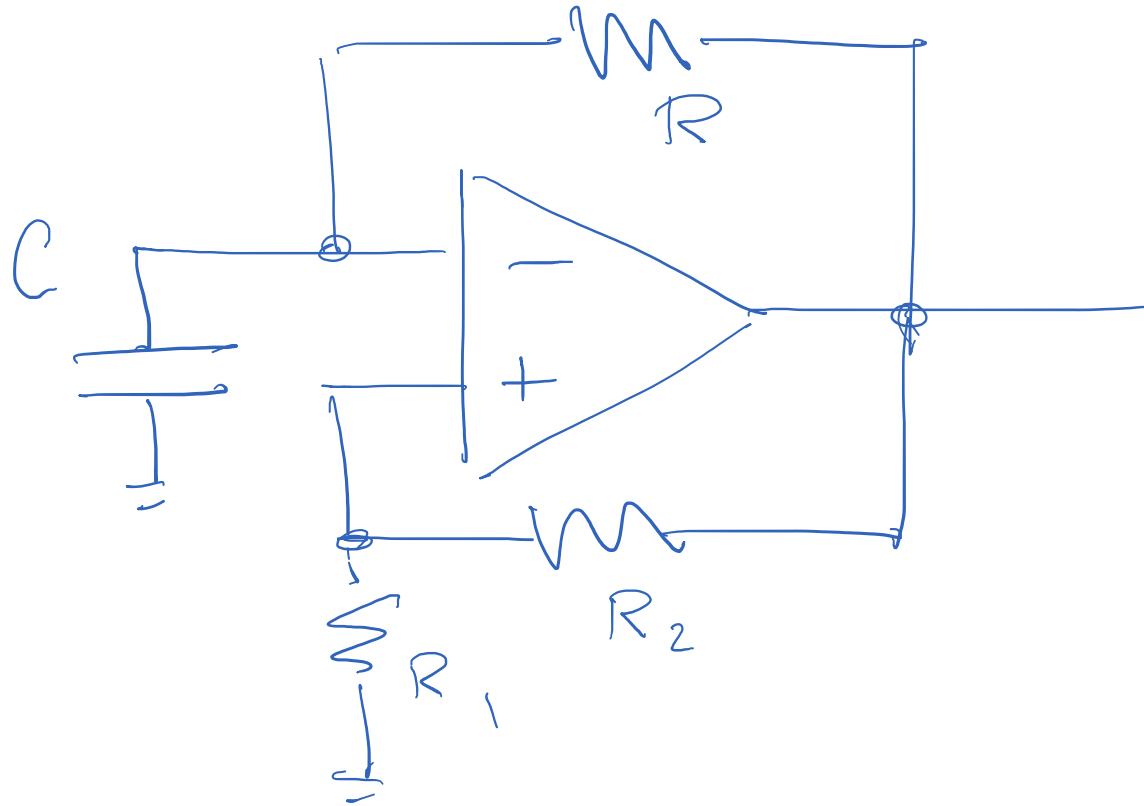

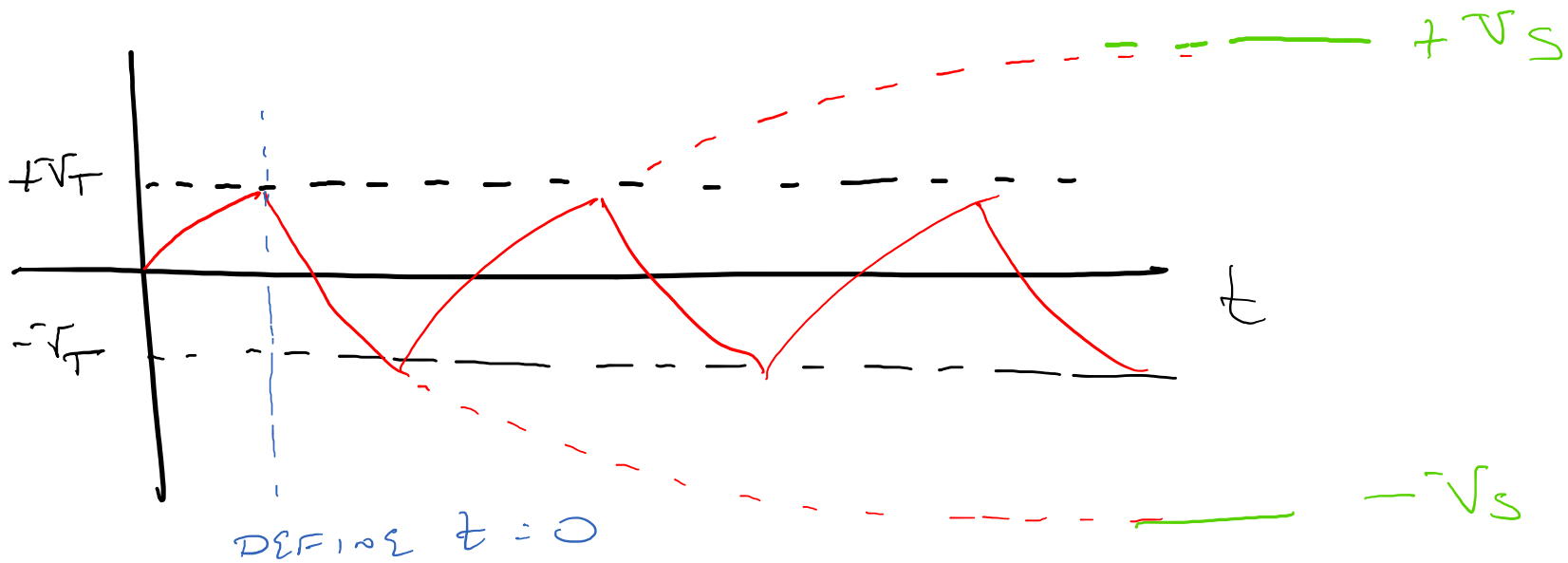

$$V_{out}(t) = A e^{-t/\tau} + B \quad ; \quad \begin{aligned} V_{out}(t=0) &= +V_T \\ V_{out}(t \rightarrow \infty) &= -V_S \end{aligned}$$

$$\Rightarrow \underline{V_{out}(t) = (V_T + V_S) e^{-t/\tau} - V_S}$$

PERIOD?

$$-V_T = (V_T + V_S) e^{-\frac{T}{2\tau}} - V_S$$


$$\Rightarrow T = 2\tau \ln \left( \frac{V_S + V_T}{V_S - V_T} \right)$$

$$\text{e.g. } V_T = \frac{V_S}{2} \Rightarrow \underline{\underline{T = 2\tau \ln 3}}$$



# COMPARATOR

---

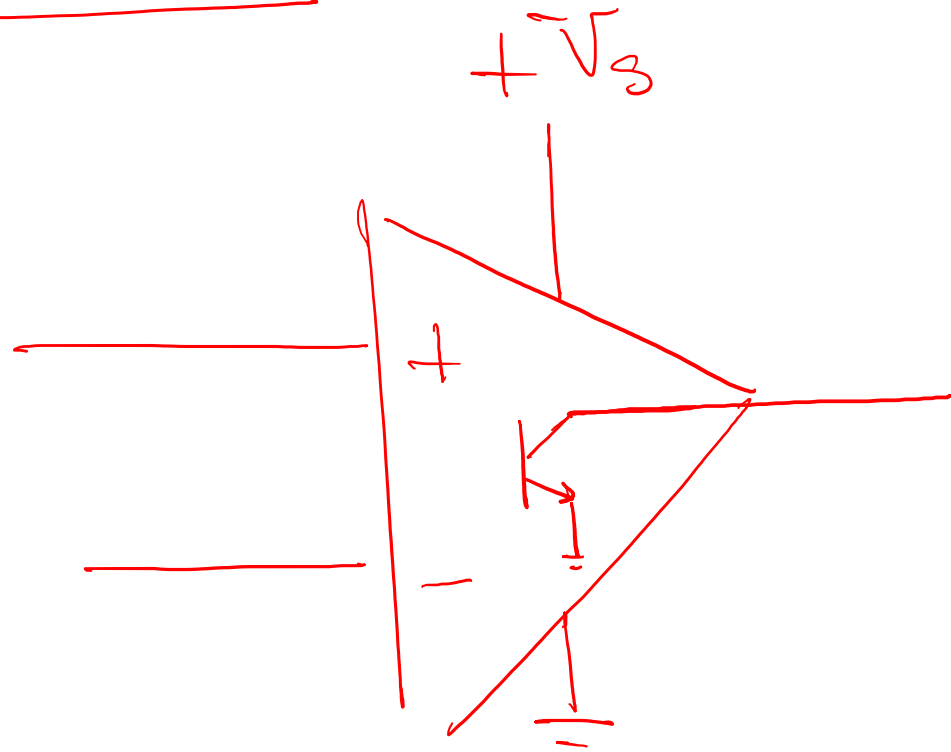

# COLPITTS OSCILLATOR

---

