 


Сомпаратор / 2 АТЧ




$$v_{out} = A[v_+ - v_-]$$

$A \gg 1$



\Rightarrow OUTPUT EITHER @

$$+V_s \quad [F_{02} \quad \underline{v_+ > v_-}]$$
 
$$-V_s \quad [F_{02} \quad \underline{v_+ < v_-}]$$




NAIVE APPROACH.

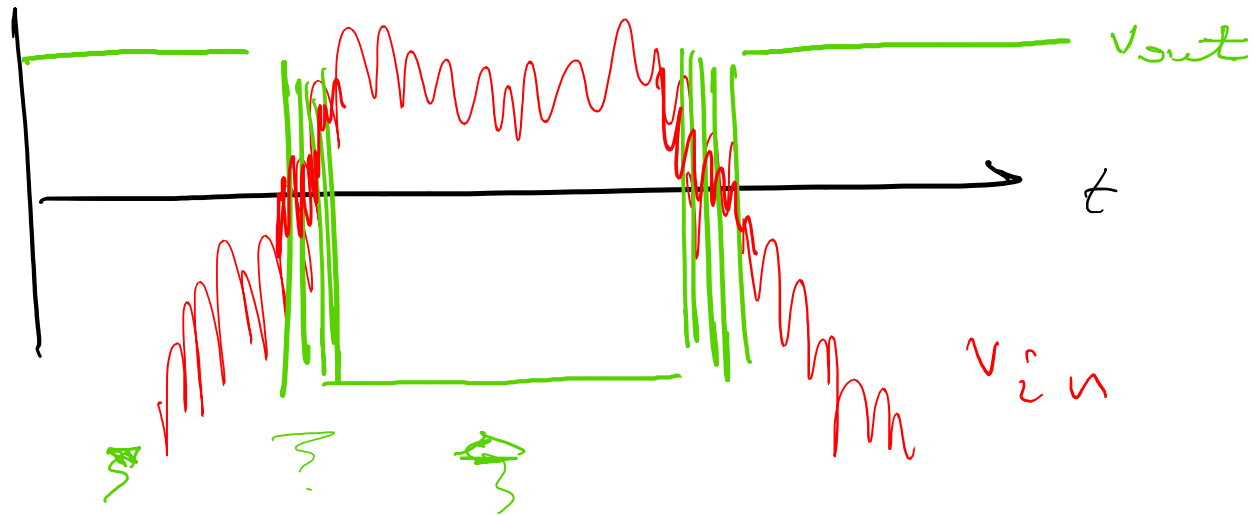 

BETTER APPROACH

LOOKS LIKE NON-INVERTING AMP.

 


BUT STILL, INPUTS DONT NO CURRENT.


THRESH. DETECTOR.

$$V_{TH} = \pm V_s \cdot \frac{R_1}{R_1 + R_2}$$

V_+ // V_{TH}

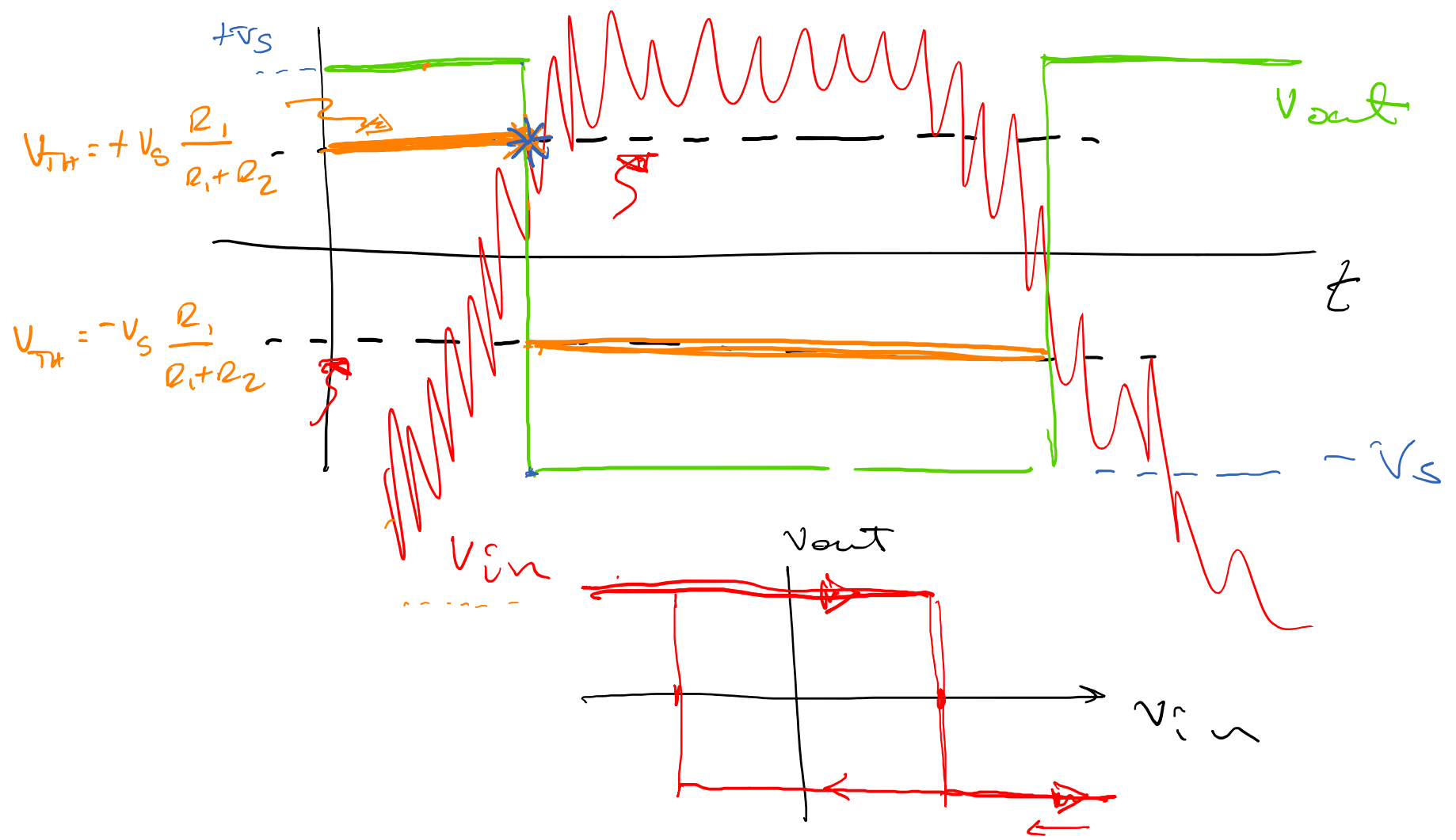

RELAXATION OSCILLATOR

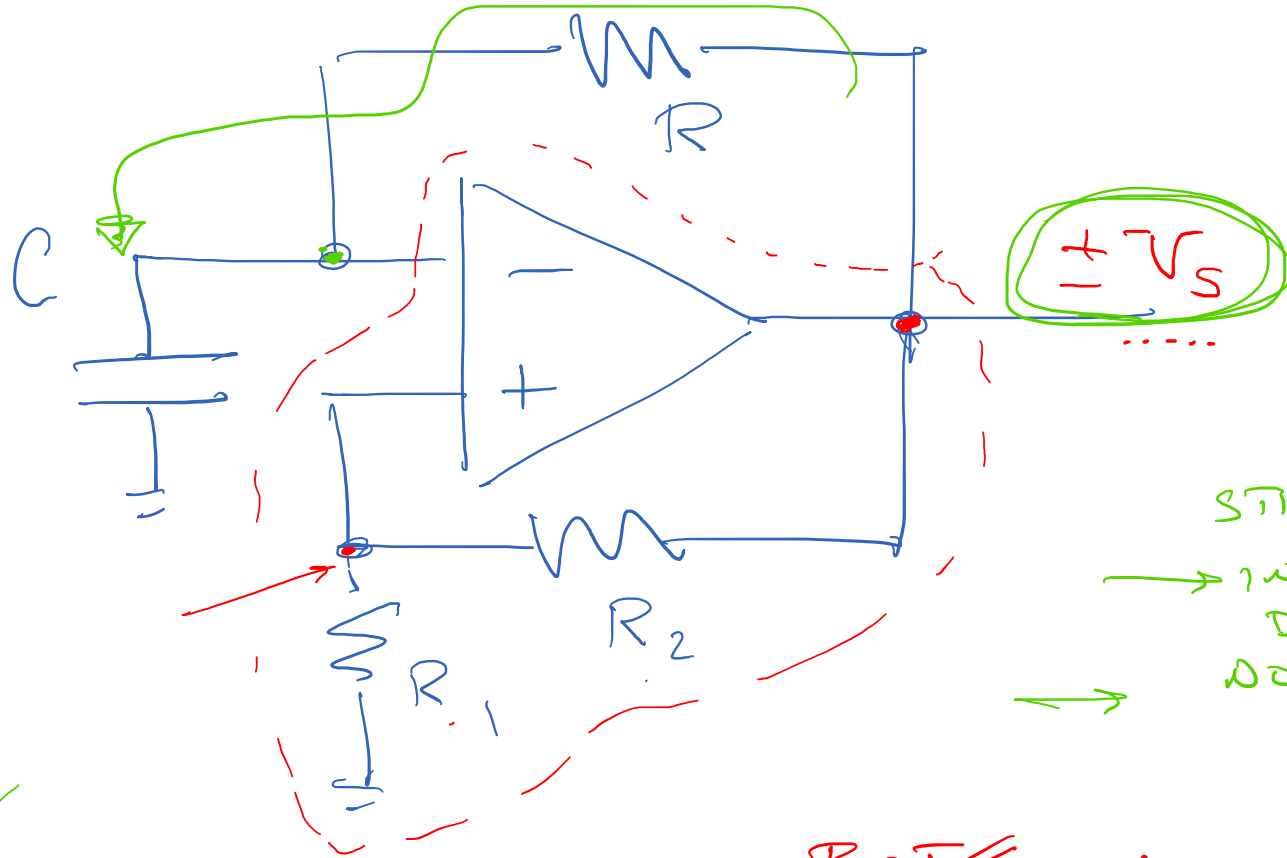

OLD FAITHFUL


STILL TRUE

→ INPUTS
DRAW
NO [NEGLECTIBLE]
CURRENT

~~But~~

$$V_+ \neq V_-$$



 

$\tau = RC$

$\Rightarrow V_{CAP}(t) = A e^{-t/\tau} + B$; $V_{CAP}(t=0) = +V_T$
 $V_{CAP}(t \rightarrow \infty) = -V_S$

$\Rightarrow V_{CAP}(t) = (V_T + V_S) e^{-t/\tau} - V_S$

PERIOD?

$$V_T = V_S \frac{R_1}{R_1 + R_2}$$

PERIOD T

$$-V_T = (V_T + V_S) e^{-\frac{T}{2\tau}} - V_S$$

$$\Rightarrow T = 2\tau \ln \left(\frac{V_S + V_T}{V_S - V_T} \right)$$

e.g. $V_T = V_S/2 \Rightarrow$

$$T = 2\tau \ln 3$$

$R_1 = R_2$

BOOLEAN ALGEBRA

LOGICAL 0 & 1 ["FALSE" & "TRUE"]


BITS A AND B

SINGLE BIT OPERATION

NOT A \bar{A}

TRUTH TABLE


INPUTS		OUTPUTS	
A	\bar{A}		
0	1		
1	0		

 

TWO-BIT OPERATIONS

A AND B

A · B

 


A	B	A · B
0	0	0
0	1	0
1	0	0
1	1	1



A OR B

A + B

 

A	B	A + B
0	0	0
0	1	1
1	0	1
1	1	1



NOR 


NAND 

→ EXCLUSIVE OR [XOR]

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

"A OR B
BUT
NOT
BOTH"


A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

 

~~AND~~

3-BIT OPERATIONS

e.g. 3-BIT AND

 

ETC.

THEOREMS OF BOOLEAN ALGEBRA

- $A + 1 = 1$
- $A + 0 = A$
- $A \cdot 1 = A$
- $A \cdot 0 = 0$
- $A + A = A$
- $A \cdot A = A$
- $A + \bar{A} = 1$
- $A \cdot \bar{A} = 0$

DISTRIBUTION

$$A \cdot (B + C) = \underline{AB + AC}$$

COMMUTATION

$$A + B = B + A$$

$$AB = BA$$

EXAMPLES

$$\underline{A + BC = (A + B)(A + C)} \quad \leftarrow$$

$$A + BC = \underline{A \cdot 1} + BC$$

$$= A \cdot (1 + B) + BC$$

$$= \underline{A \cdot 1} + \underline{AB} + \underline{BC}$$

$$= A \cdot (1 + C) + B(A + C)$$

$$= A \cdot (A + C) + B(A + C)$$


$$\Rightarrow \underline{\underline{(A + B)(A + C)}}$$

$$A \cdot 1 = A \cdot A$$

[DISTRIBUTION]

De Morgan's Theorem

 I. $\overline{A \cdot B} = \bar{A} + \bar{B}$
 NOT (A AND B) = NOT A OR NOT B



II. $\overline{A + B} = \bar{A} \cdot \bar{B}$
 NOT (A OR B) = NOT A AND NOT B



eg

A	B	$\overline{A \cdot B}$	$\bar{A} + \bar{B}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

↔

EXAMPLE

~~XXXXXXXXXX~~






$$= \overline{A \bar{B} + (\bar{B} + C)}$$

$$= \underline{A \bar{B} + B \bar{C}}$$

W

ANOTHER: XOR FROM NAND

$$A \cdot \bar{B} + \bar{A} \cdot B$$

   


XOR


$$A \oplus B = \bar{A} \cdot \bar{B} + A \cdot B$$

$$= \overline{A \cdot \bar{B} + \bar{A} \cdot B}$$

 
$$= \overline{(A \cdot \bar{B}) \cdot (\bar{A} \cdot B)}$$



DIGITAL LATCH

 

A	B	A+B
0	0	1
0	1	0
1	0	0
1	1	0

 

TRUTH TABLE

	INPUTS			
	X	Y		
SR	00	01	10	11
→ 00	11	01	10	00
→ 01	10	00	10	00
10	01	01	00	00
11	00	00	00	00


(NOT USED)



MEMORY


output bits XY

REDUCED TRUTH TABLE

 


S	R	Q _{NEXT}
0	0	Q
0	1	0
1	0	1
1	1	X

GATED D-LATCH

 


D FLIP FLOP

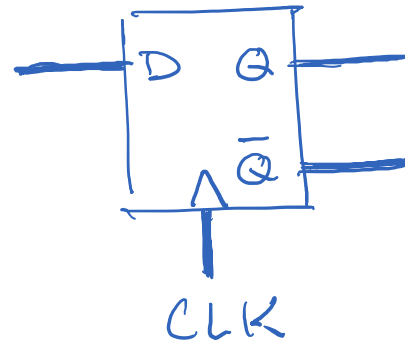


CLK	D	Q
RISING EDGE	0	0
RISING EDGE	1	1
NON RISING	X	Q

$$Q_{next} = D$$

SHIFT REGISTER

 

ASYNCHRONOUS COUNTER

 

Q_3	Q_2	Q_1	Q_0
0	0	0	0
0	0	0	1