
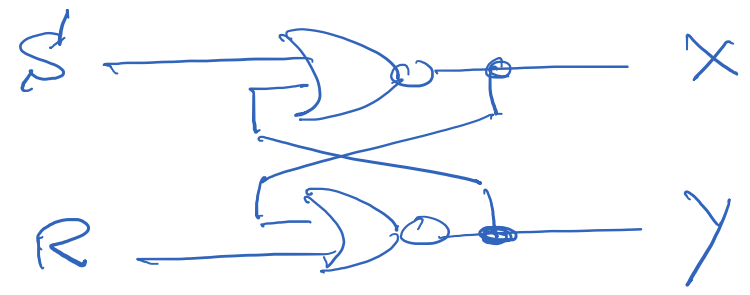


DIGITAL LATCH

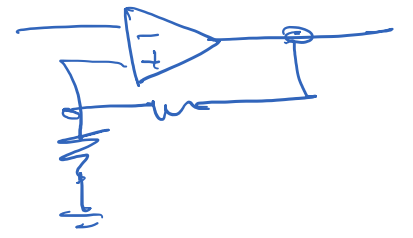

| A | B | A+B |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |



TRUTH TABLE


| S | R |
|-----|---|
| → 0 | 0 |
| → 0 | 1 |
| 1 | 0 |
| → 1 | 1 |

| INPUTS XY | ↓ | ↓ | |
|--------------|----|----|----|
| 00 | 01 | 10 | 11 |
| 11 | 01 | 10 | 00 |
| 10 | 00 | 10 | 00 |
| 01 | 01 | 00 | 00 |
| 00 | 00 | 00 | 00 |


(NOT USED)



MEMORY

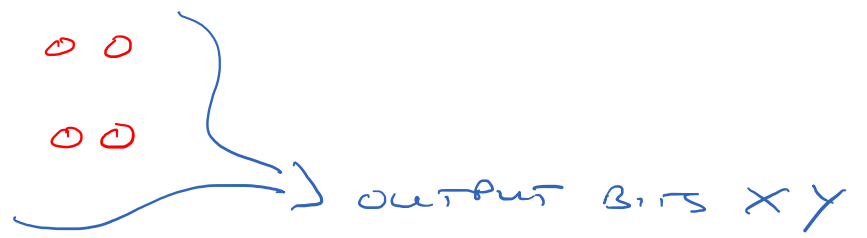


REDUCED TRUTH TABLE

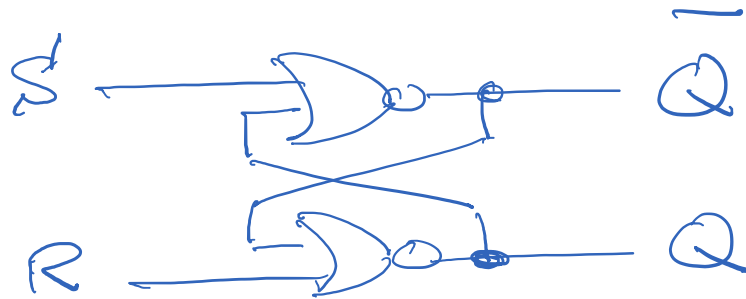

| S | R | Q |
|---|---|---------------|
| 0 | 0 | (HOLD) |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | (NOT ALLOWED) |

A red arrow points to the first row (S=0, R=0). A blue arrow points to the last two rows (S=1, R=0 and S=1, R=1).

GATED D-LATCH

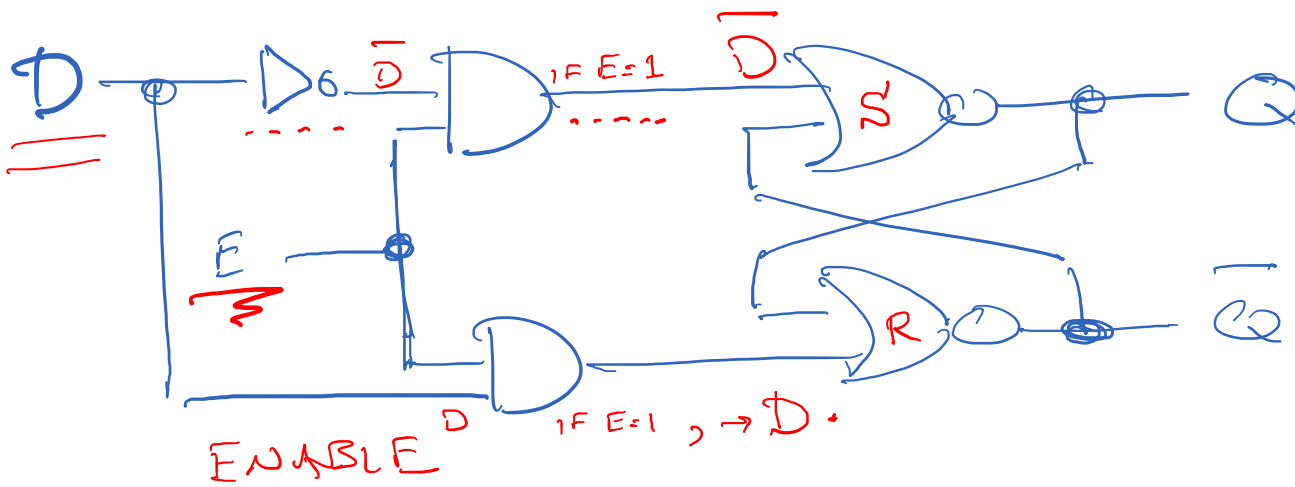


| D | E | Q |
|---|---|--------|
| X | 0 | (HOLD) |
| 0 | 1 | 0 |
| 1 | 1 | 1 |


$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$


EDGE-TRIGGERED D. FLOP FWP

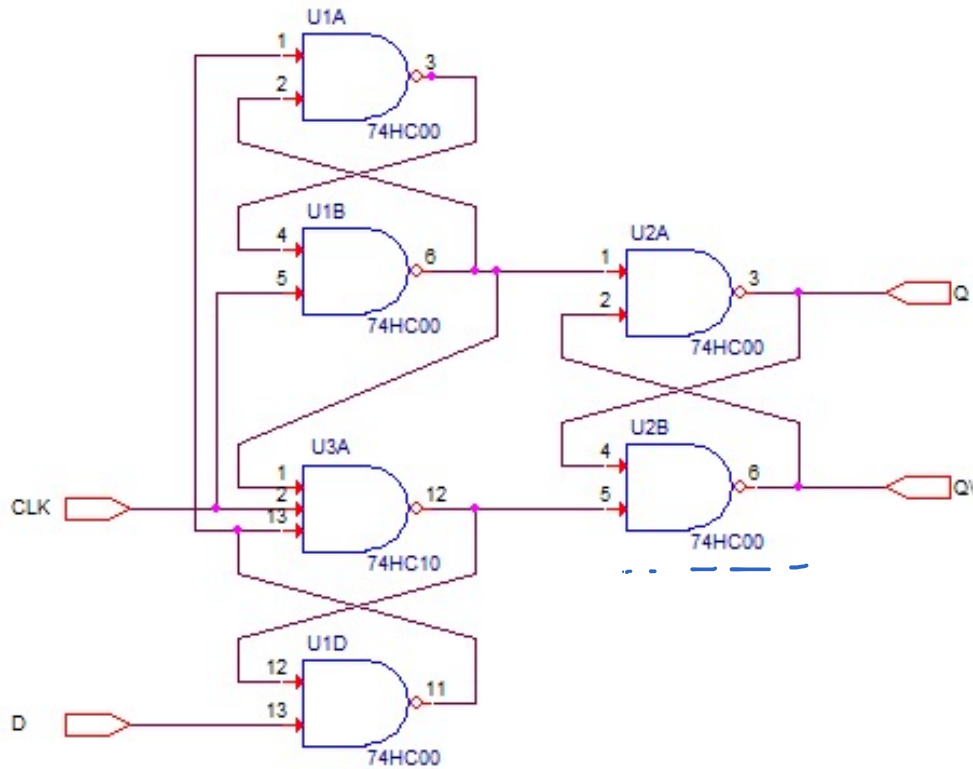

SR w/ NAND

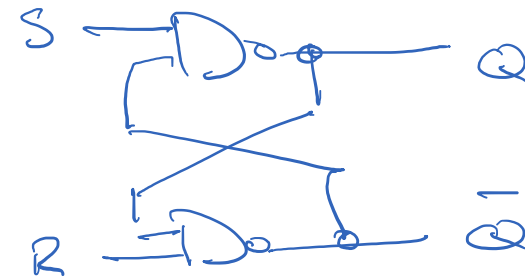

| S | R | Q |
|---|---|-------------|
| 0 | 0 | NOT ALLOWED |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | HOLD |

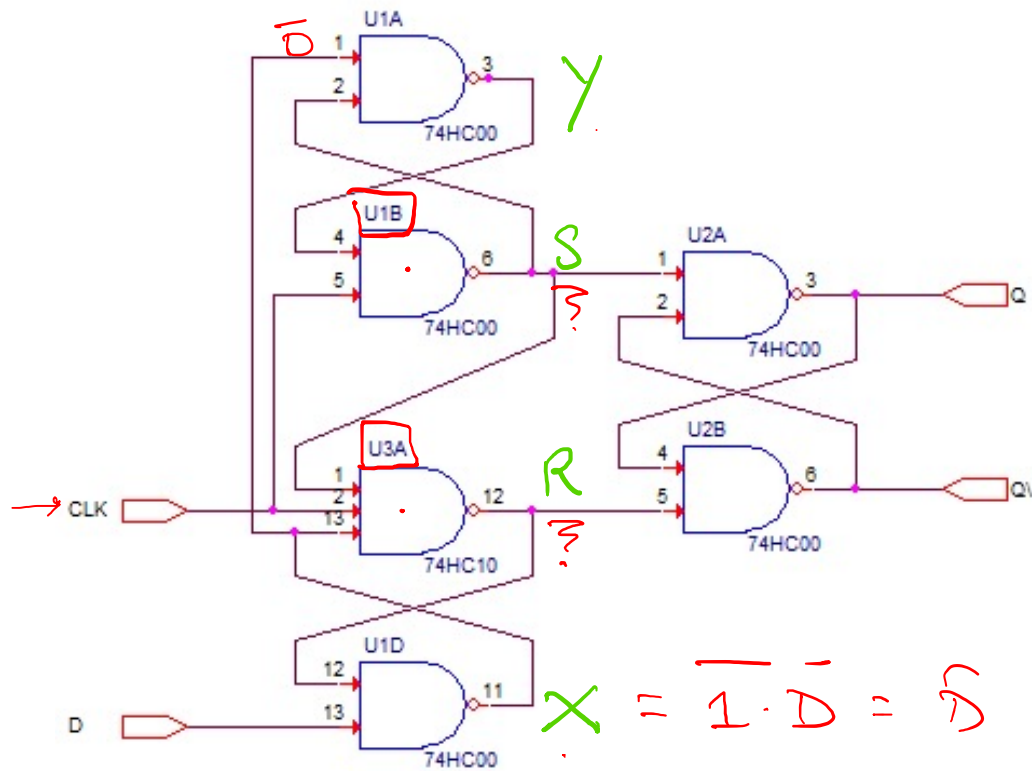

| A | B | $\overline{A \cdot B}$ |
|---|---|------------------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

| S | R | Q | \overline{Q} |
|---|---|------|----------------|
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | HOLD | |

CLK = 0


$\Rightarrow R = 1$

$S = 1$

OUTPUTS HOLD

$X = \overline{D}$

$Y = D$

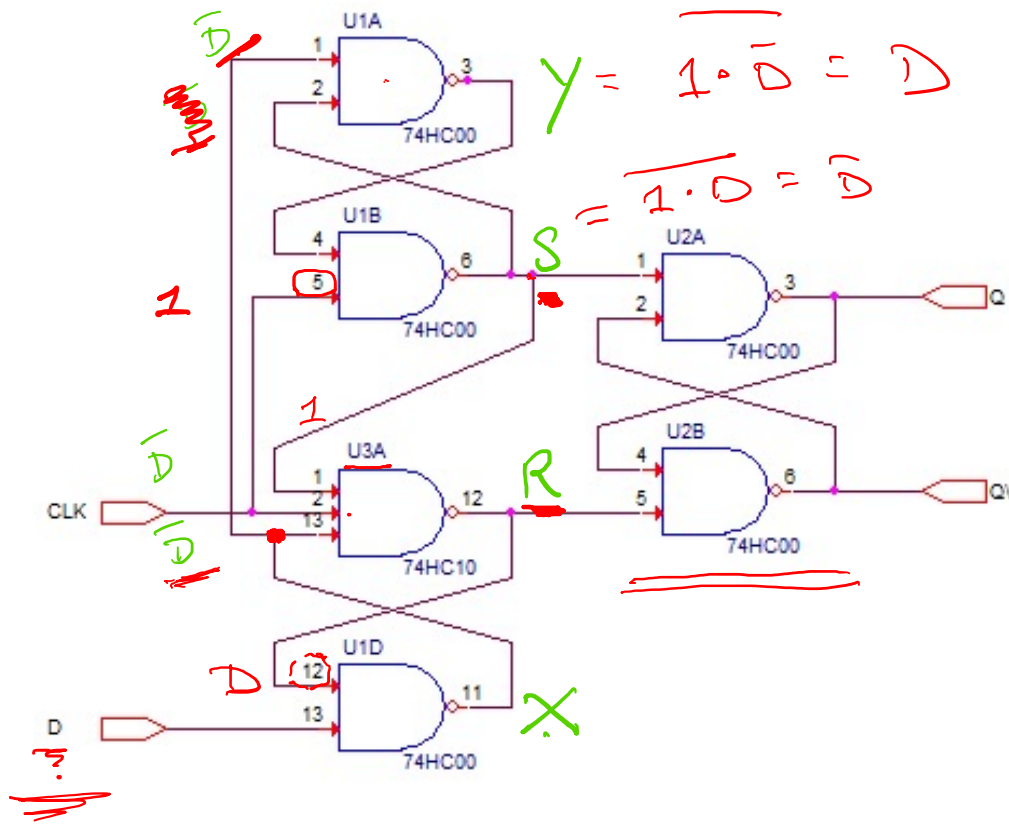

| A | B | $\overline{A \cdot B}$ |
|---|---|------------------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

| S | R | Q | \bar{Q} |
|---|---|------|-----------|
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | Hold | |


$\rightarrow CLK = 1$
 \Rightarrow

$\Rightarrow R = \bar{D}$
 $\rightarrow X = \bar{D}$
 $\rightarrow Y = D$
 $\rightarrow S = \bar{D}$

$Q = D$

$\Rightarrow \bar{Q} = \bar{D}$

~~_____~~

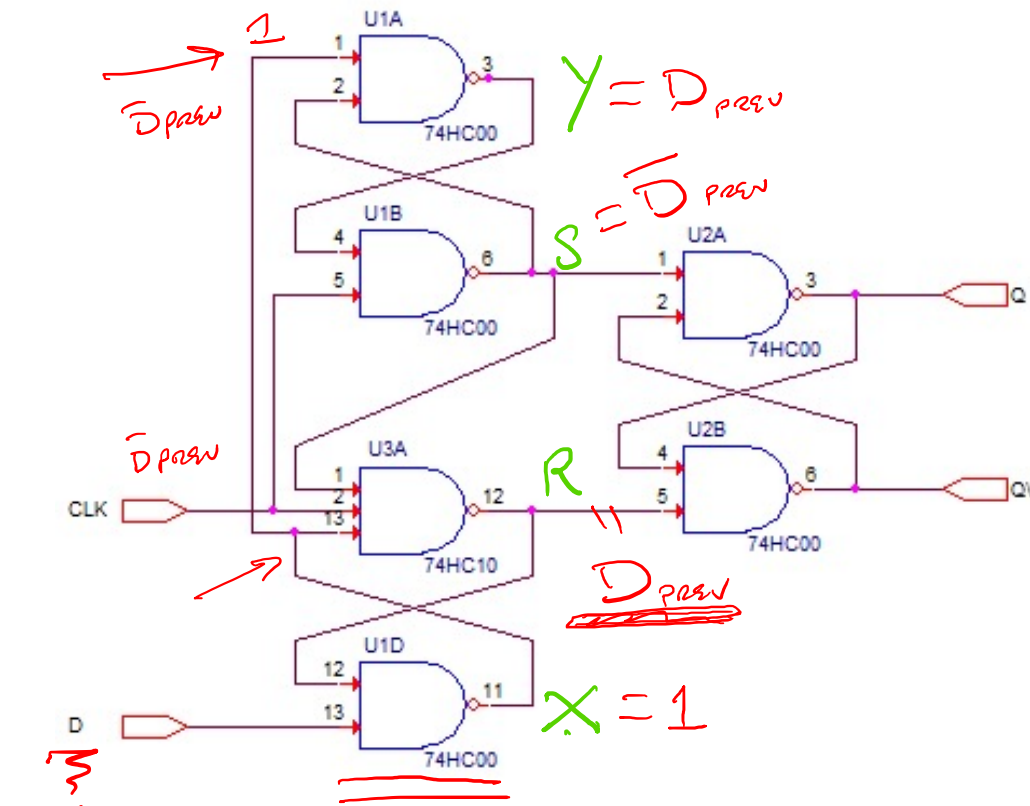

| A | B | $\overline{A}B$ |
|---|---|-----------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

| S | R | Q | \overline{Q} |
|---|---|------|----------------|
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | HOLD | |

CLK = 1

\Rightarrow

now D changes

$X \rightarrow 1$


$\Rightarrow Y, S, R$ all

maintain output

$\overline{A} \cdot \overline{A} = 1$

| A | B | $\overline{A}B$ |
|---|---|-----------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

| S | R | Q | \overline{Q} |
|---|---|------|----------------|
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | HOLD | |

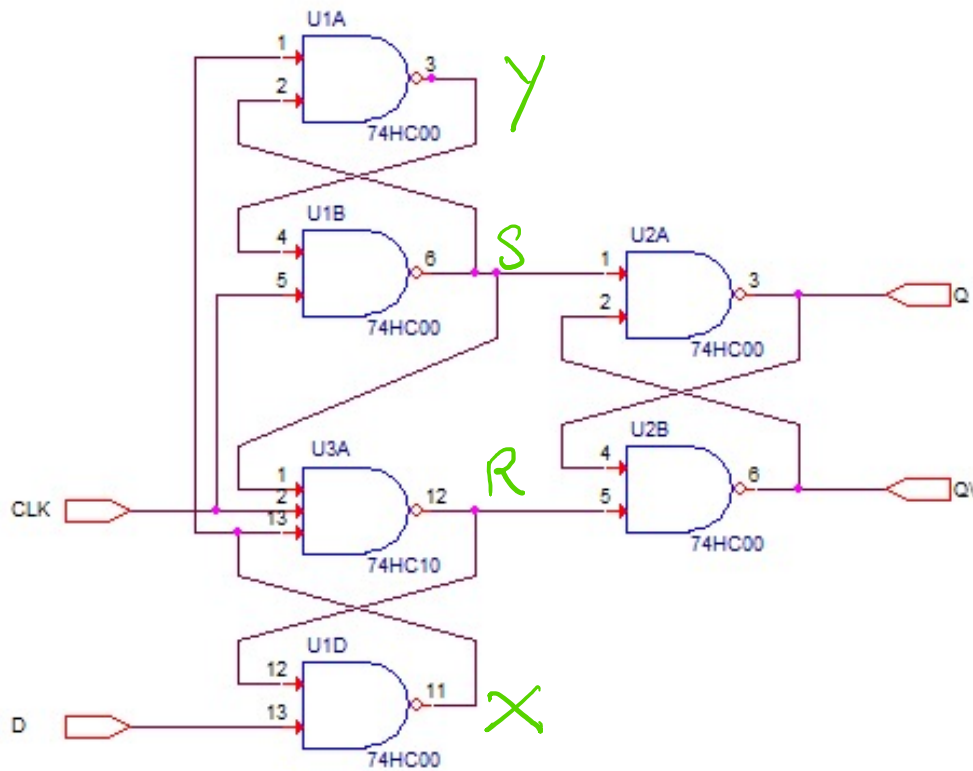

CLK = 0

$\Rightarrow R = 1$



$S = 1$

OUTPUTS HOLD

$X = \overline{D}$

$Y = D$

D FLIP FLOP

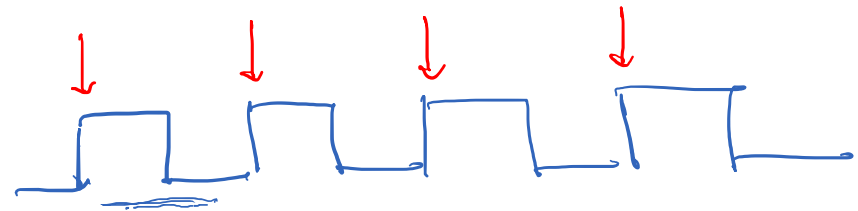
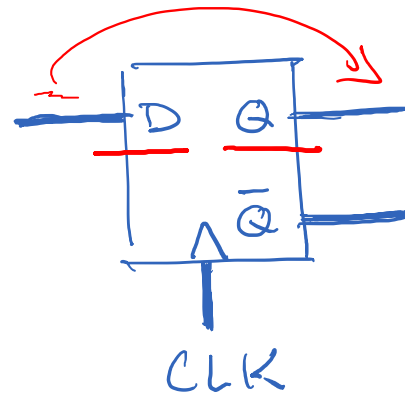


| CLK | D | Q |
|--------------------|---|-----|
| <u>RISING EDGE</u> | 0 | 0 ← |
| <u>RISING EDGE</u> | 1 | 1 → |
| <u>NON RISING</u> | X | Q |

$$Q_{next} = D$$


$$Q_{n+1} = D_n$$

DIVIDE-BY-TWO

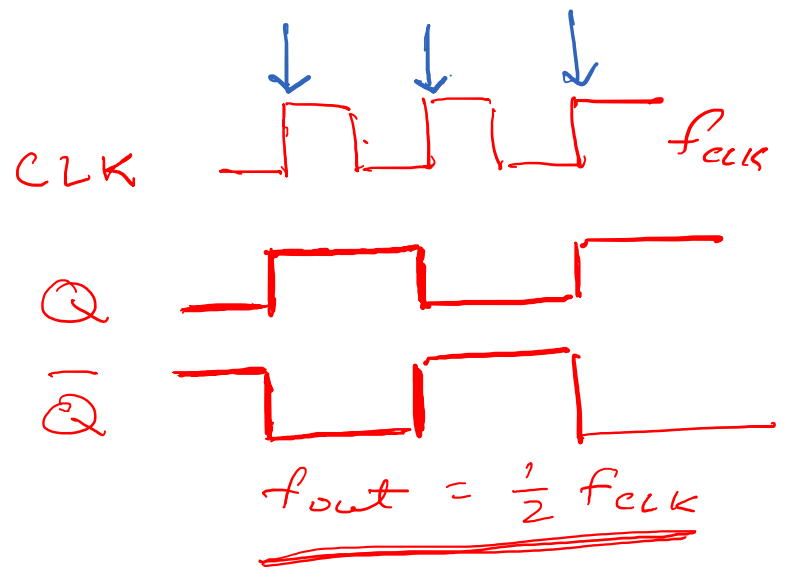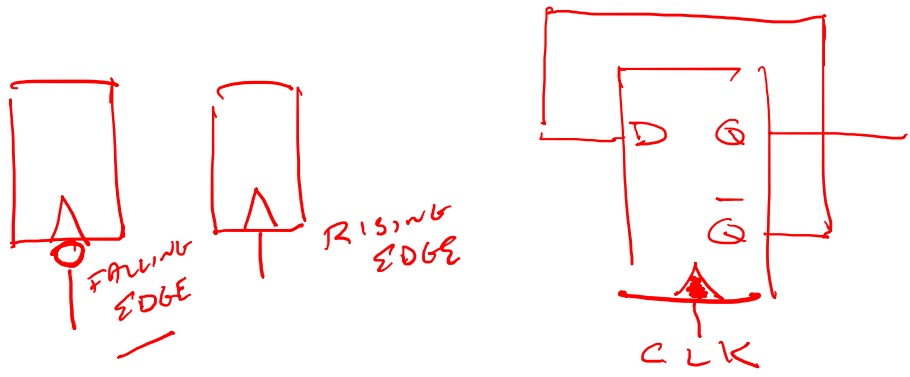


ASYNCHRONOUS COUNTER

"RIPPLE" COUNTER

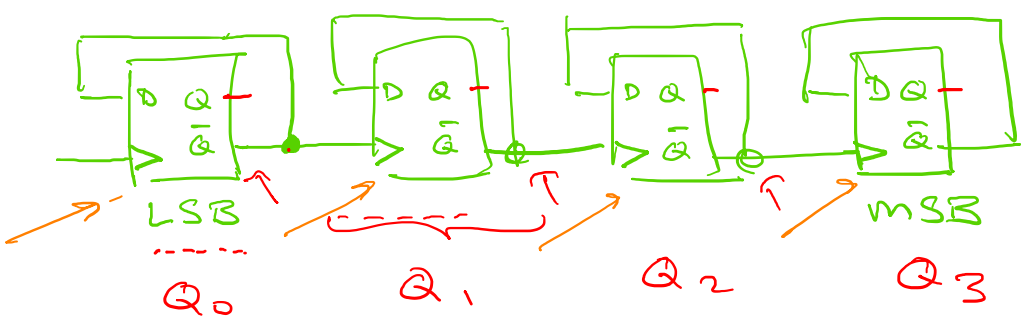

| MSB | Q_3 | Q_2 | Q_1 | Q_0 | LSB |
|-----|-------|-------|-------|-------|-----|
| | 0 | 0 | 0 | 0 | |
| | 0 | 0 | 0 | 1 | |
| | 0 | 0 | 1 | 0 | |
| | 0 | 1 | 0 | 0 | |

SYNCHRONOUS COUNTER

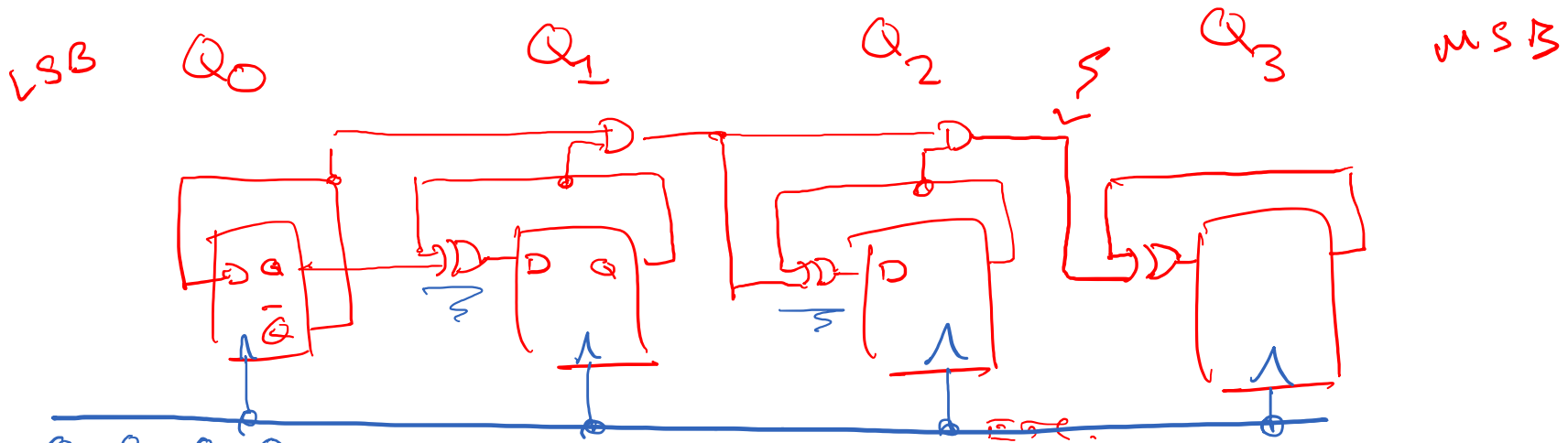


| Q ₃ | Q ₂ | Q ₁ | Q ₀ |
|----------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 |

$$Q_{1, \text{next}} = Q_{0, \text{prev}} \oplus Q_{1, \text{prev}}$$


$$Q_{2, \text{next}} = (Q_{0, \text{prev}} \cdot Q_{1, \text{prev}}) \oplus Q_{2, \text{prev}}$$

SHIFT REGISTER

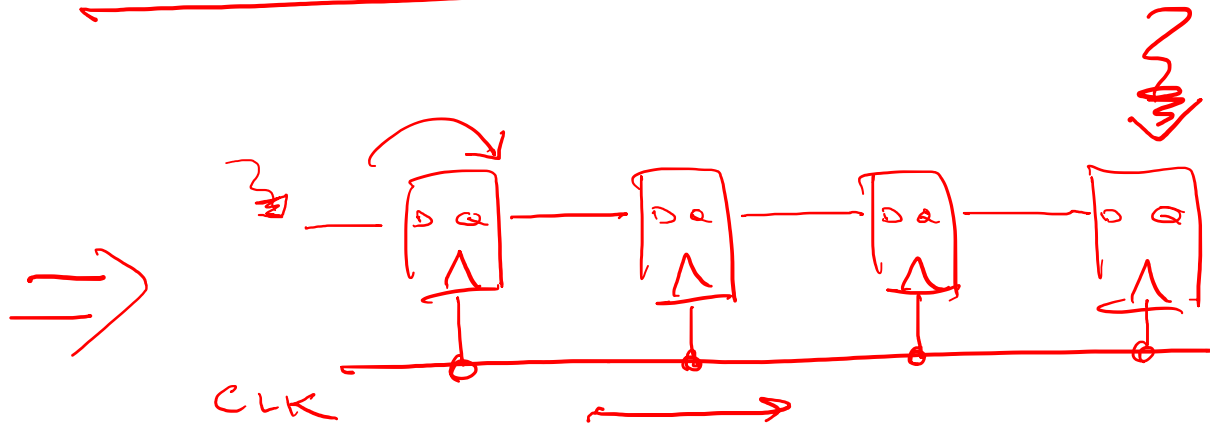

| | Q_3 | Q_2 | Q_1 | Q_0 | D |
|---|-------|-------|-------|-------|-----|
| | 0 | 0 | 0 | 0 | 1 |
| → | 0 | 0 | 0 | 1 | 0 |
| → | 0 | 0 | 1 | 0 | 1 |
| → | 0 | 1 | 0 | 1 | 1 |
| → | 1 | 0 | 1 | 1 | 1 |


JK FLIP FLOP

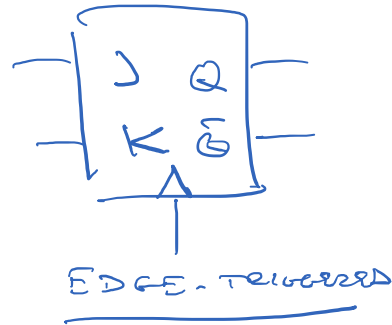

| J | K | Q _{next} |
|---|---|-------------------|
| 0 | 0 | Q |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | Q̄ |

@ RISING EDGE

SYNCHRONOUS
COUNTER

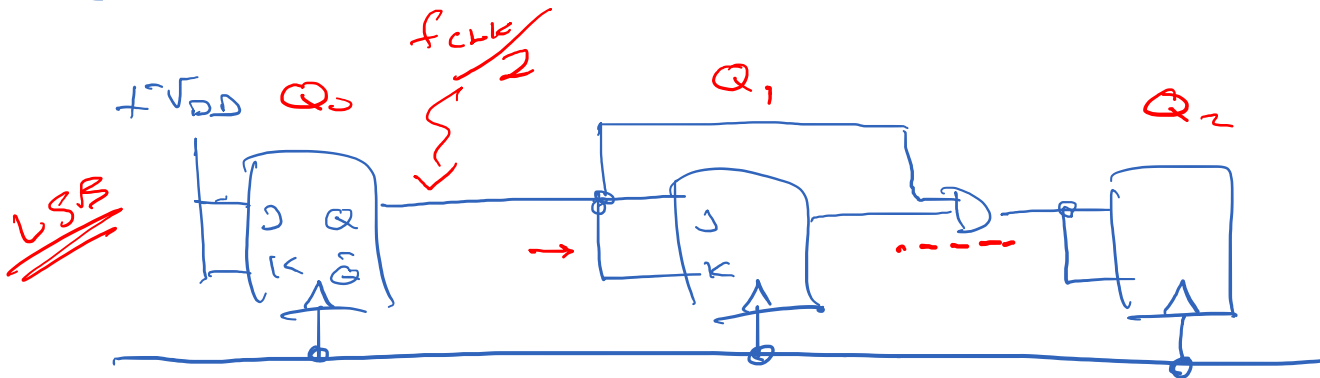

SHIFT REGISTER.

| J | K | Q_{n+1} |
|---|---|-----------|
| 0 | 0 | Q_n |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | Q_n |

← COUNTING
} SHIFT REGISTERS
←

