

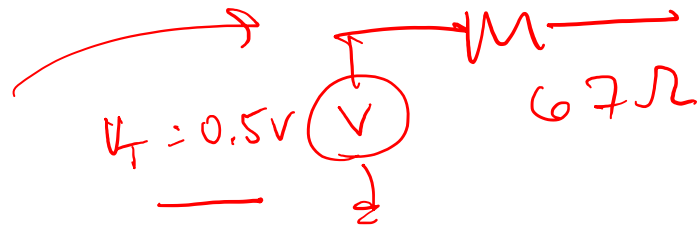


QUESTIONS?

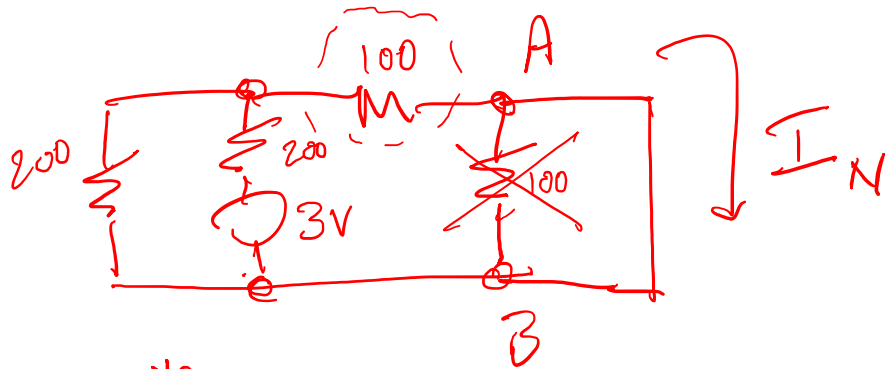

$$I_N = \frac{V_T}{R_T}$$
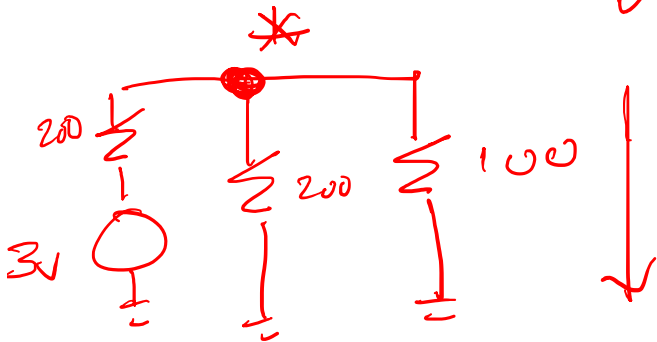
$$3 = \frac{I}{\frac{2}{3} \cdot 100} \quad 7.5 \text{ mA} ?$$




$$V_* = 3V \cdot \frac{\frac{2}{3}}{2 + \frac{2}{3}} = \frac{3}{4} V$$

$$I_N = 7.5 \text{ mA}$$

IMPEDANCE

CAPACITOR: CIRCUIT ELEMENT THAT
STORES CHARGE / ELECTRIC FIELD ENERGY

PROTOTYPICAL:

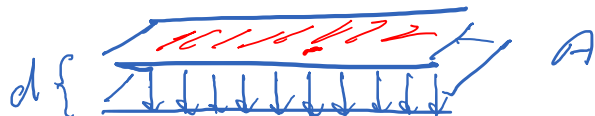


MAYWELL $\nabla \cdot \vec{E} = \frac{1}{\epsilon} \rho$ $\int \vec{E} \cdot d\vec{A} = \frac{1}{\epsilon} \int \rho dV$

$$E \cdot A = \frac{1}{\epsilon} Q \quad \Rightarrow \quad \frac{V}{d} \cdot A = \frac{1}{\epsilon} Q$$

$$Q = \frac{\epsilon A}{d} V \quad \Rightarrow \quad Q = CV, \quad \text{WITH } C = \frac{\epsilon A}{d}$$

UNITS: FARAD

DIFFERENTIATE $\Rightarrow \underline{I = C \frac{dV}{dt}}$ [DISPLACEMENT CURRENT]

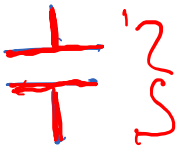SYMBOL 

OPEN @ DC
SHORT @ HIGH. FREQ.

PRACTICAL CAPS :

μF [MICROFARADS]

\rightarrow μPF FOR RF

\rightarrow mF FOR FILTERING / POWER APPLICATIONS

$\epsilon_0 \sim 8 \cdot 10^{-12} \text{ F/m}$

STORED ENERGY

$$\int (I V) dt = C \int V \frac{dV}{dt} dt = \underline{\underline{\frac{1}{2} C V^2}} = \underline{\underline{\frac{Q^2}{2C}}}$$

INDUCTOR : ELEMENT FOR STORING MAGNETIC ENERGY
[FLUX, FIELD]

PROTOTYPICAL :  LENGTH l ,
 n TURNS



MAXWELL $\nabla \times \vec{B} = \mu_0 \vec{J}$

$$\int_A \rightarrow \oint \vec{B} \cdot d\vec{l} = \mu_0 I \cdot n$$

$$B \cdot l = \mu_0 I n$$

$$B = \mu_0 \frac{n}{l} I$$

$$\Phi = n B A = \mu_0 n^2 \frac{A}{l} I$$

DEFINING INDUCTANCE

$$L = \frac{\Phi}{I}$$

$$\Rightarrow L = \mu_0 n^2 \frac{A}{l}$$

$$\mu_0 = \frac{4\pi \times 10^{-7} \text{ H/m}}{\sim 10^{-6} \text{ H/m}}$$

INDUCTANCE GOES AS n^2 ←

• PROPORTIONAL TO LENGTH ←

• UNIT: HENRY


PRACTICAL INDUCTORS:
pH [MICROFAB. DEVICES]
nH [RF APPLICATIONS]
mH [FILTERS]

$$\mu_0 \sim 10^{-6} \text{ H/m}$$

$$1 \text{ pH} / \mu\text{m}$$

$$1 \text{ nH} / \text{mm}$$

USEFUL:

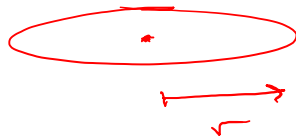


$$L \sim \int \mu_0 r$$

STORES ENERGY

SINCE $\Phi = LI$, $V = L \frac{dI}{dt}$
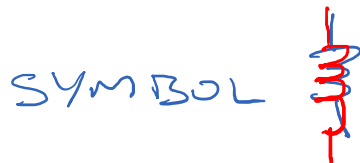
$$\int (IV) dt = 2 \int I dI = \frac{1}{2} LI^2 = \frac{\Phi^2}{2L}$$



SHORT @ DC
OPEN CIRCUIT @ HIGH FREQ.


Duality

$$\left. \begin{array}{l} Q \leftrightarrow \phi \\ C \leftrightarrow L \\ V \leftrightarrow I \\ E \leftrightarrow B \end{array} \right\} \mathcal{N}$$

Quantum mechanics, $\hat{\phi}$ and \hat{Q}
ARE CONJUGATE VARIABLES ~~AND~~


$$[\hat{\phi}, \hat{Q}] = i\hbar$$

~~AND~~

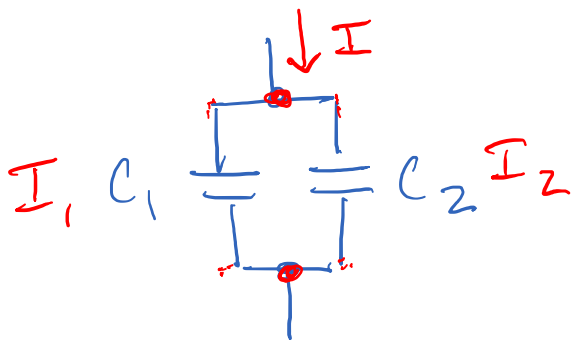

$$I_1 = C_1 \frac{dV}{dt} \quad ; \quad I_2 = C_2 \frac{dV}{dt} \quad \dots$$
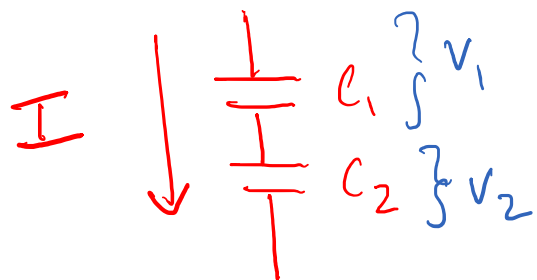
$$I = (C_1 + C_2) \frac{dV}{dt} \quad \Rightarrow \quad \underline{\underline{C_{eff} = C_1 + C_2}}$$



$$I = C_1 \frac{dV_1}{dt} = C_2 \frac{dV_2}{dt} \quad \dots$$

$$\dot{V} = \dot{V}_1 + \dot{V}_2$$

$$\dot{V} = \frac{I}{C_1} + \frac{I}{C_2} = \frac{1}{C_{eff}} \cdot I$$

$$\rightarrow C_{eff} = \left[\frac{1}{C_1} + \frac{1}{C_2} \right]^{-1}$$

FREQ. - DEPENDENT CIRCUITS, IMPEDANCE


CONSIDER $V = V_0 \cos(\omega t + \phi)$ ←

WRITE AS

$$V = V_0 e^{j(\omega t + \phi)}$$

PHASOR

$$j \equiv \sqrt{-1}$$

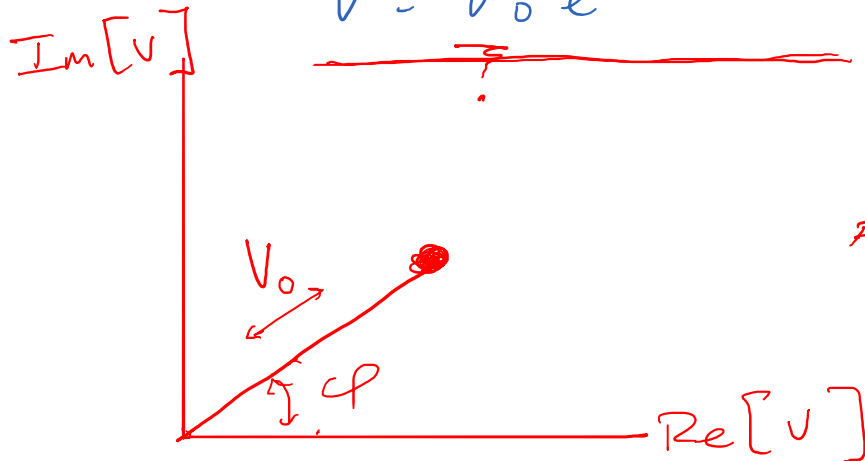


FRAME ROTATES @
ANG. FREQ. ω

@ END OF DAY, TAKE REAL PART TO DETERMINE
PHYSICAL VOLTAGES, CURRENTS

$$\text{Re} \left[\underbrace{V_0 e^{j(\omega t + \phi)}} \right] = V_0 \cos(\omega t + \phi)$$

TAKE $V = V_0 e^{j\omega t}$

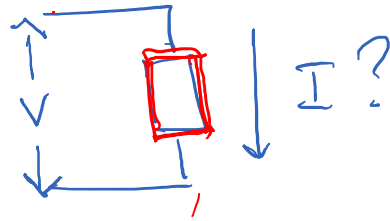

WHAT CURRENT
IN LOAD?

$$R: I = \frac{V}{R} = \frac{V_0}{R} e^{j\omega t}$$

$$C: I = C \frac{dV}{dt} = j\omega C V_0 e^{j\omega t}$$

$$L: I = \frac{1}{L} \int V dt = \frac{1}{j\omega L} V_0 e^{j\omega t}$$

DEFINE IMPEDANCE

$$Z \equiv \frac{V}{I}$$

GEN'ERIALIZED OHM'S LAW.

$$\rightarrow R: Z_R(\omega) = R$$

$$\rightarrow C: Z_C(\omega) = \frac{1}{j\omega C}$$


$$\rightarrow L: Z_L(\omega) = j\omega L$$

$$= -\frac{j}{\omega C}$$

VOLTAGE LAGS CURRENT


VOLTAGE LEAD CURRENT

COMPLEX IMPEDANCE PLANE

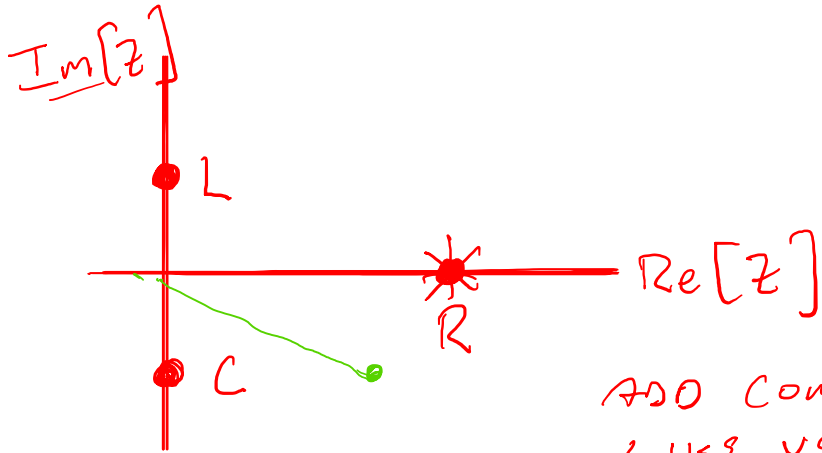


$$Z = R - \frac{j}{\omega C}$$



ADD COMPLEX IMPEDANCES
LIKE VECTORS

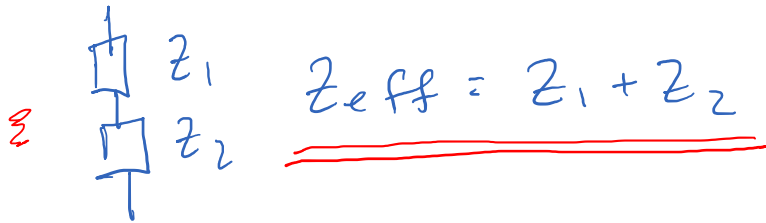

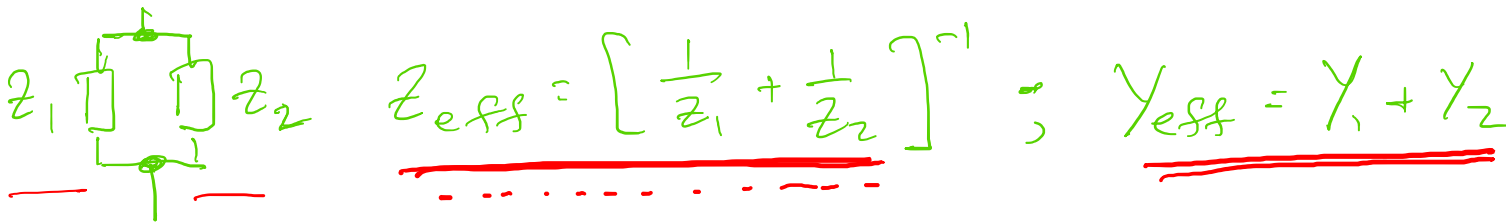SOMETIMES CONVENIENT TO WORK w/ ADMITTANCE $Y \equiv \frac{1}{Z}$



PHASOR EXAMPLE

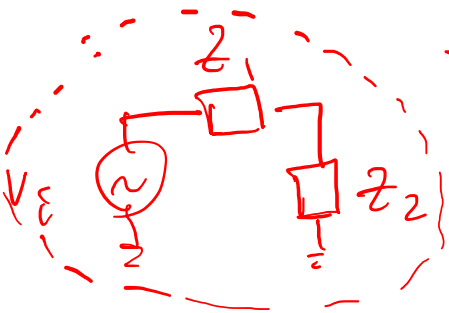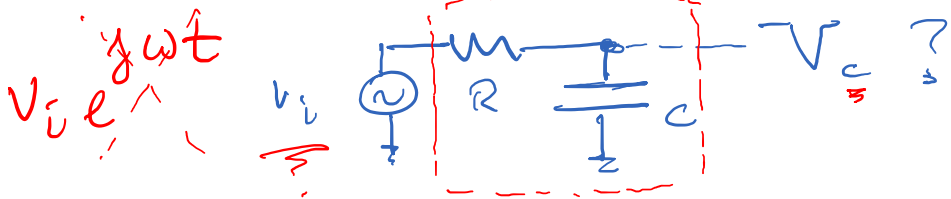


$\tau = RC$

$V_o = v_i \frac{z_1}{z_1 + z_2}$

LOW FREQ. :





HIGH FREQ. :

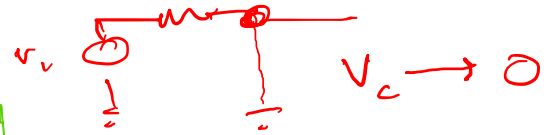


$\tau = L/R$

$V_c = \frac{-j\omega C}{R - j\omega C} \quad V_c = \frac{1}{1 + j\omega RC} v_i = \frac{1}{1 + j\omega \tau} v_i$

$\left| \frac{V_c}{v_i} \right|^2 = \frac{1}{1 + \omega^2 \tau^2}$

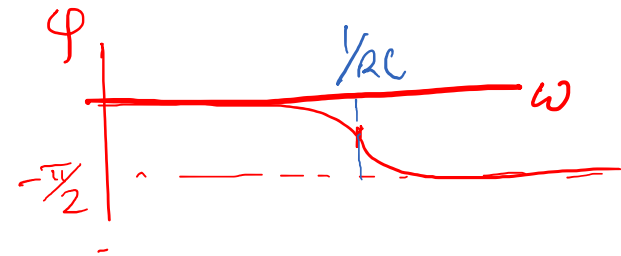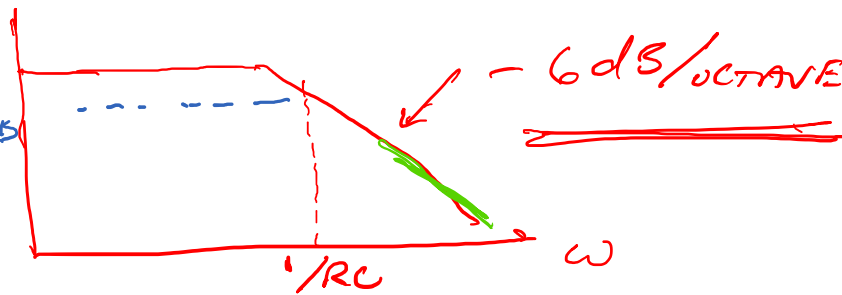

SERIES RLC circuit

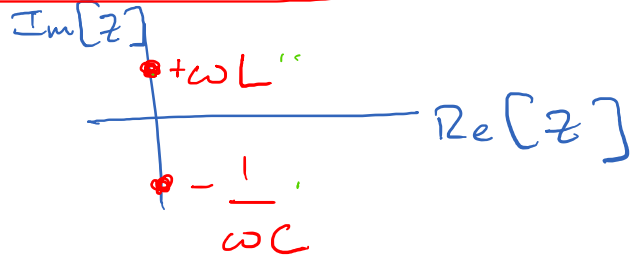

$$X \equiv \omega L - \frac{1}{\omega C}$$

$$I = \frac{V}{R + jX} = \frac{R - jX}{R^2 + X^2} V$$

$$Z_{TOT} = j \left(\omega L - \frac{1}{\omega C} \right)$$


@ $\omega_0 \equiv \frac{1}{\sqrt{LC}} \Rightarrow Z = 0$

CONSIDER

$$\omega_0 L = \frac{1}{\omega_0 C}$$

$$\equiv Z_0$$

$$Z_0 \gg R$$

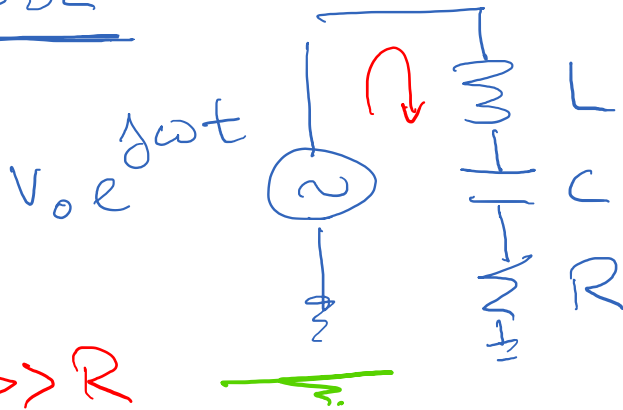

$$|I|^2 = \frac{V_0^2}{R^2 + X^2}$$

$$Z_0; Q \equiv \frac{Z_0}{R} \gg 1$$

$$X = \frac{Z_0}{\omega_0 \omega} \underbrace{(\omega + \omega_0)}_{2\omega_0} \underbrace{(\omega - \omega_0)}_{\Delta}$$

$$X \approx 2 Z_0 \frac{\Delta}{\omega_0}$$




$$|I|^2 = \frac{V_0^2}{\left[\frac{Z_0}{Q}\right]^2 + 4\left[\frac{Z_0}{\omega_0}\right]^2 \Delta^2}$$

$$|I|^2 = \frac{V_0^2}{Z_0^2} Q^2 \frac{\omega_0^2}{\omega_0^2 + 4Q^2 \Delta^2}$$

$$\Delta = 0 \rightarrow I_{\text{PEAK}} = \frac{V_0}{Z_0} Q$$

CURRENT ENHANCEMENT
BY FACTOR Q

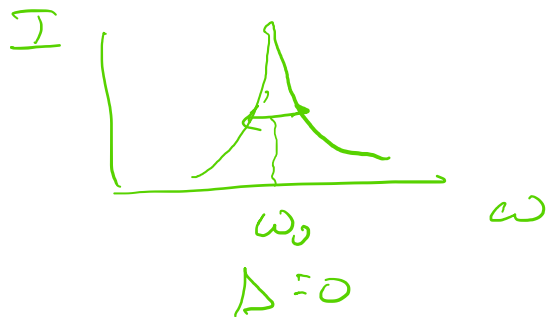

$$\text{FWHM} \rightarrow 2\Delta = \frac{\omega_0}{Q}$$