

```
module addbit(
```

```
  a,  
  b,  
  ci,  
  sum,  
  co  
);
```

DECLARE PORTS

```
input a;  
input b;  
input ci;
```

```
output sum;  
output co;
```


```
wire a;  
wire b;  
wire ci;  
wire sum;  
wire co;
```

```
assign {co,sum} = a + b + ci;
```

```
endmodule
```

HDL
H
E
D
L
S
U
M
A
D
D
I
T
I
O
N
S


FULL ADDER

 

→ VHDL (EUROPE)
→ VERILOG (US)

~

MODULE
INSTANCE

 

```

module adder(
  result,
  carry,
  r1,
  r2,
  ci
);

```

```

input [3:0] r1;
input [3:0] r2;
input ci;

```

```

output [3:0] result;
output carry;

```

```

wire [3:0] r1;
wire [3:0] r2;
wire ci;
wire [3:0] result;
wire carry;

```

```

wire c1;
wire c2;
wire c3;

```

INTERNAL VARIABLES

```

addbit u0(r1[0],r2[0],ci,result[0],c1);
addbit u1(r1[1],r2[1],c1,result[1],c2);
addbit u2(r1[2],r2[2],c2,result[2],c3);
addbit u3(r1[3],r2[3],c3,result[3],carry);



```

IMPLICIT INSTANTIATION

```

endmodule

```

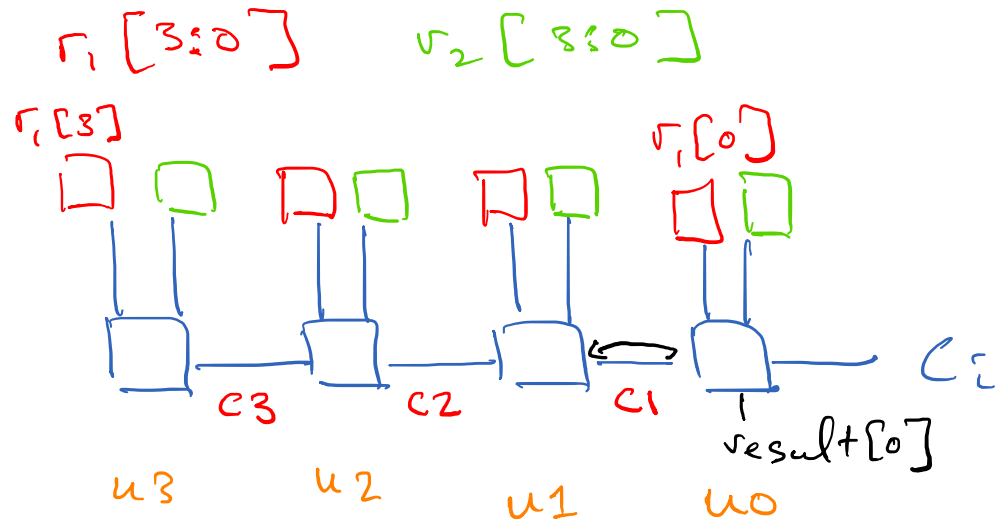 

```
module tb();  
reg [3:0] r1, r2;  
reg ci;  
wire [3:0] result;  
wire carry;
```

initial begin

```
// Dump waves  
$dumpfile("dump.vcd");  
$dumpvars(1);  
$display("time\t r1 r2 ci result carry");  
$monitor("%g %b %b %b %b %b",  
$time, r1, r2, ci, result, carry);
```

```
r1 = 0;  
r2 = 0;  
ci = 0;  
#10 r1 = 10;  
#10 r2 = 2;  
#10 ci = 1;  
#10  
$finish;  
end
```

```
adder U(result,carry,r1,r2,ci);
```

endmodule

TESTBENCH

edaplayground.com

r1 = 4'b0000


#10

1010

0010

r1 = 4'b1010

r2 = 4'b0010

 

time	r1	r2	ci	result	carry
0	0000	0000	0	0000	0
10	1010	0000	0	1010	0
20	1010	0010	0	1100	0
30	1010	0010	1	1101	0

$r_1 \rightarrow 10$ "a"
 $r_2 = 0$
 $r_1 + r_2 = a$

$r_1 = a$
 $r_2 = 2$
 $a + 2 = c$

$a + 2 + 1 = d$

time r1 r2 ci result carry

0	0000	0000	0	0000	0
10	1010	0000	0	1010	0
20	1010	0110	0	0000	1
30	1010	0110	1	0001	1



```
module mux_4_to_1(
```

```
out,
i0,
i1,
i2,
i3,
s0,
s1
);
```

$(out, i, s);$

4 TO 1 MULTIPLEXER



```
output out;
input i0, i1, i2, i3;
input s0, s1;
```

input [3:0] i;
input [1:0] s;

```
wire out;
wire i0, i1, i2, i3;
wire s0, s1;
```

```
assign out = s1 ? (s0 ? i3 : i2) : (s0 ? i1 : i0);
```

```
endmodule
```

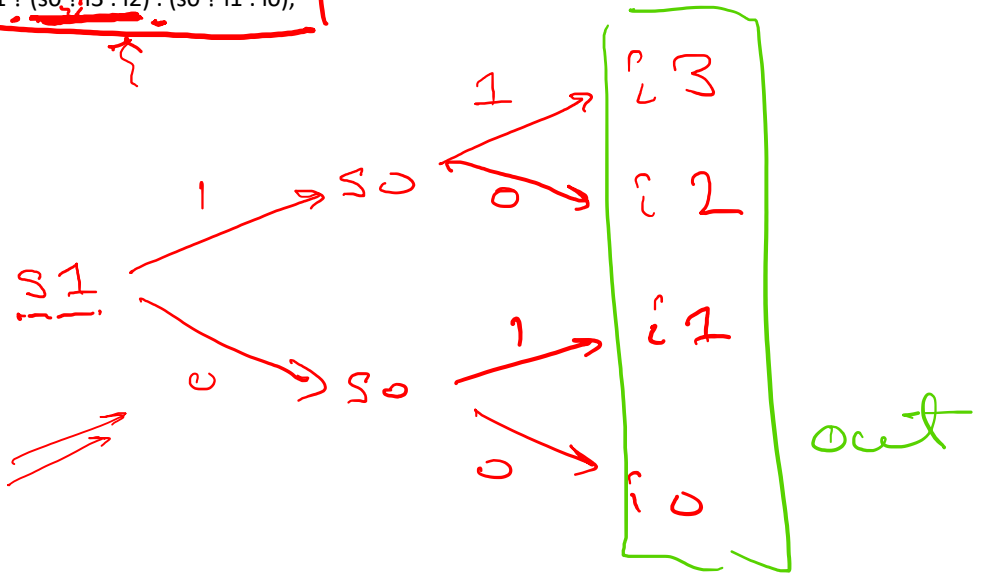 

NESTED CONDITIONAL

$$s = 2'b11 \quad out \leftarrow i3$$
$$s = 2'b10 \quad out \leftarrow i2$$
$$\vdots$$

```
module tb_mux();
```

```
reg [3:0] i;  
reg [1:0] s;  
wire out;
```

```
initial begin
```

```
    // Dump waves  
    $dumpfile("dump.vcd");  
    $dumpvars(1);  
  
    $display("time\t i s result");  
  
    $monitor("%g %b %b %b",  
            $time, i, s, out);
```

```
    i = 4'b0000;  
    s = 2'b00;  
    #10 i = 4'b0001;  
    #10 s = 2'b01;  
    #10 i = 4'b0011;  
    #10 s = 2'b10;  
    #10 i = 4'b0111;  
    #10 s = 2'b11;  
    #10 i = 4'b1111;
```

```
    #10  
    $finish;
```

```
end
```

```
mux_4_to_1 U(out,i[0],i[1],i[2],i[3],s[0],s[1]);
```

```
endmodule
```


$i[3:0]$


→ 0000

0001

0011

0111

1111

 

$s[1:0]$

00

01

10

11

```
module FJKRSE(J,K,Clk,R,S,CE,Qout);
```

```
input J,K; //inputs
input Clk; //Clock
input R; //synchronous reset (R)
input S; //synchronous set (S)
input CE; //clock enable (CE)
output Qout; //data output (Q)
```

```
//Internal variable
reg Qout;
```

```
always@ (posedge(Clk)) //Everything is synchronous to positive edge of clock
```

```
begin
  if(R == 1) //reset has highest priority.
```

SYNCHRONOUS RESET

```
    Qout = 0;
  else
    if(S == 1) //set has next priority
```

```
      Qout = 1;
```

```
  else
    if(CE == 1) //J,K values are considered only when CE is ON.
```

```
      if(J == 0 && K == 0)
        Qout = Qout; //no change
```

```
      else if(J == 0 && K == 1)
        Qout = 0; //reset
```

```
      else if(J == 1 && K == 0)
        Qout = 1; //set
```

```
      else
        Qout = ~Qout; //toggle
```

```
      else
        Qout = Qout; //no change
```

```
end
```

```
endmodule
```

J	K	Q _{n+1}
1	1	$\sim Q_n$
1	0	1
0	1	0
0	0	Q_n

```
module tb_jkff;
```

```
// Inputs
```

```
reg J;
```

```
reg K;
```

```
reg Clk;
```

```
reg R;
```

```
reg S;
```

```
reg CE;
```

```
// Outputs
```

```
wire Qout;
```

```
// Instantiate the Unit Under Test (UUT)
```

```
FJKRSE uut (
```

```
.J(J),
```

```
.K(K),
```

```
.Clk(Clk),
```

```
.R(R),
```

```
.S(S),
```

```
.CE(CE),
```

```
.Qout(Qout)
```

```
);
```

```
initial begin
```

```
...  
$dumpfile("jkff.vcd");
```

```
$dumpvars(1);
```

```
// Initialize Inputs
```

```
Clk = 0;
```

```
J = 0;
```

```
K = 0;
```

```
R = 0;
```

```
S = 0;
```

```
CE = 0;
```

```
#3;
```

```
//Apply inputs
```

```
R = 1; #5;
```

```
R = 0;
```

```
S = 1; #5;
```

```
S = 0;
```

```
J = 1; K = 1; #5;
```

```
CE = 1; #5;
```

```
J = 0; K = 0; #5;
```

```
J = 0; K = 1; #5;
```

```
J = 1; K = 0; #5;
```

```
J = 1; K = 1; #5;
```

```
CE = 0;
```

```
$finish;
```

```
end
```

```
always begin
```

```
#2 Clk = ~Clk;
```


```
end
```

```
endmodule
```

CLOCK PERIOD


4 UNITS

→ eda_playground.com.

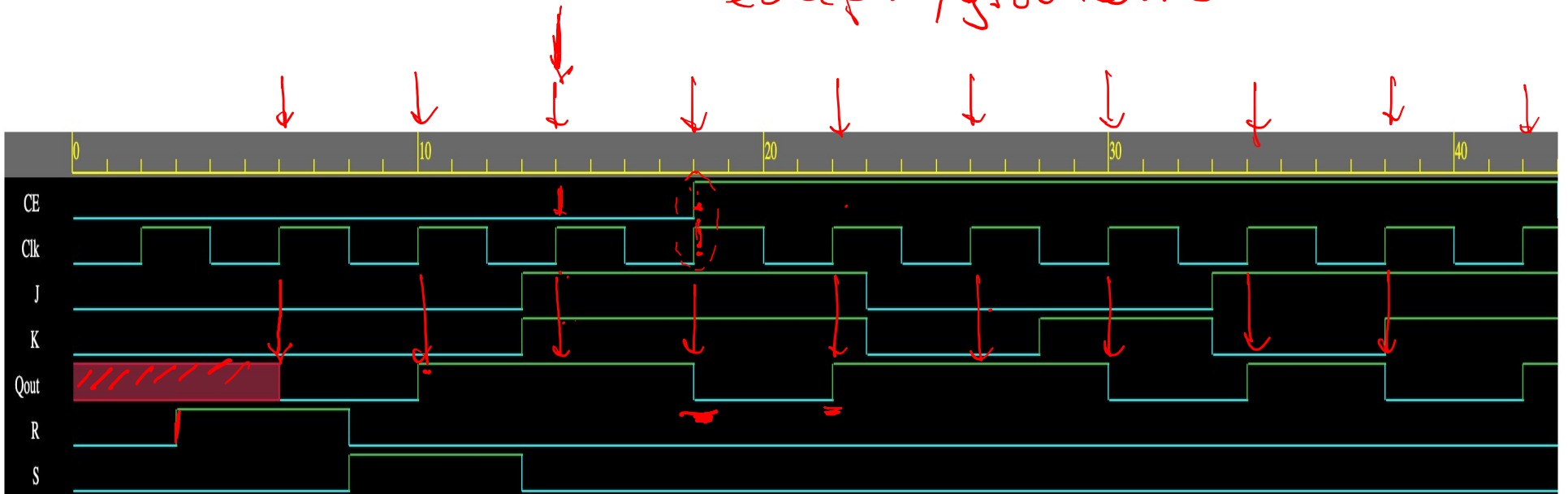

RESET

```
module first_counter (  
  clock,  
  reset,  
  enable,  
  counter_out  
);  
  
input clock;  
input reset;  
input enable;  
  
output [3:0] counter_out;  
  
wire clock;  
wire reset;  
wire enable;  
reg [3:0] counter_out;  
  
always @ (posedge clock)  
begin: COUNTER  
  if (reset == 1'b1) begin  
    counter_out <= #1 4'b0000;  
  end  
  
  else if (enable == 1'b1) begin  
    counter_out <= #1 counter_out+1;  
  end  
  
end  
  
endmodule
```



```
module first_counter_tb();
```

```
reg clock, reset, enable;  
wire [3:0] counter_out;
```

```
initial begin
```

```
// Dump waves  
$dumpfile("dump.vcd");  
$dumpvars(1);
```

```
$display("time\t clk reset enable counter");
```

```
$monitor("%g %b %b %b %b",  
         $time, clock, reset, enable, counter_out);
```

```
clock = 1;  
reset = 0;  
enable = 0;  
#5 reset = 1;  
#10 reset = 0;  
#5 enable = 1;  
#200 enable = 0;  
#10 $finish;
```



```
end
```


```
always begin
```

```
#5 clock = ~clock;
```

```
end
```

```
first_counter U_counter(  
clock,  
reset,  
enable,  
counter_out  
);
```

```
endmodule
```

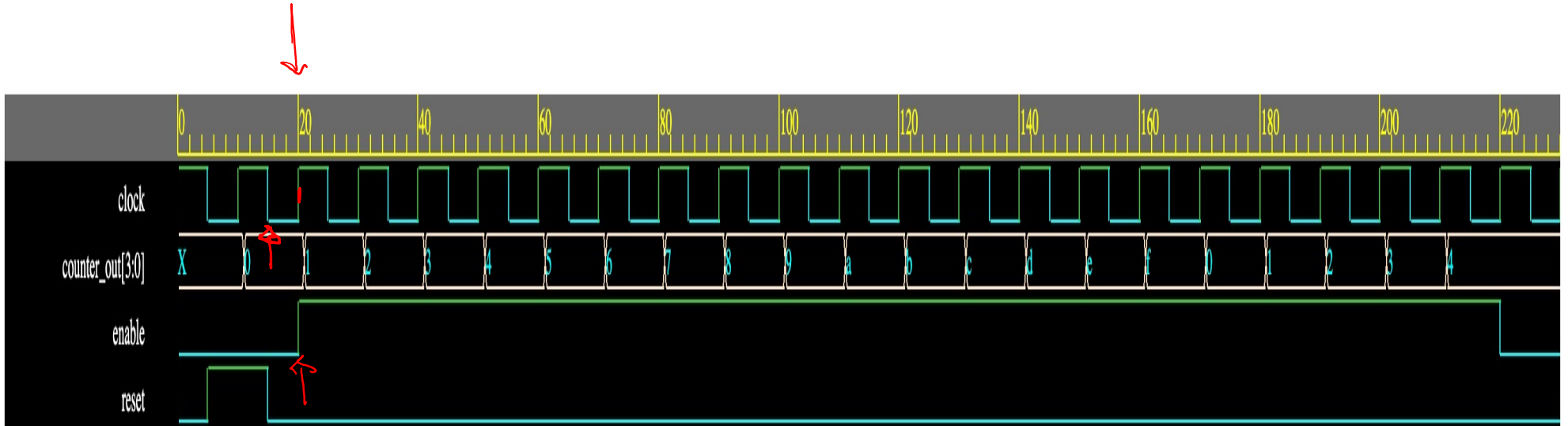


FINITE STATE MACHINE

KARNAUGH
MAP

FINITE SET OF STATES
INPUTS INDUCE TRANSITIONS BASED
ON CURRENT STATE & INPUT VALUES

STORE UP TO 2^N STATES IN OUTPUTS OF N FLIP FLOPS

STATE DIAGRAM

 


VENDING MACHINE

TYPE II P.D.

PULL CHIP

ACCEPT 5¢, 10¢
@ 15¢, DISPENSE NEWSPAPER

 

Output
0 → "BLUE"
1 → "RED"
Give
N. PAPER.

```
module vend(coin, clock, reset, newspaper);
```

```
// port declarations
```

```
input [1:0] coin;
```

```
input clock;
```

```
input reset;
```

```
output newspaper;
```

```
wire newspaper;
```

```
// internal FSM declarations
```

```
wire [1:0] NEXT_STATE;
```

```
reg [1:0] PRES_STATE;
```

```
// state encodings
```

```
parameter s0 = 2'b00;
```

```
parameter s5 = 2'b01;
```

```
parameter s10 = 2'b10;
```

```
parameter s15 = 2'b11;
```

```
function [2:0] fsm;  
input [1:0] fsm_coin;  
input [1:0] fsm_PRES_STATE;
```

```
reg fsm_newspaper;
```

```
reg [1:0] fsm_NEXT_STATE;
```

```
begin  
case (fsm_PRES_STATE)
```

```
  s0:  
  begin  
    if (fsm_coin == 2'b10)  
      begin  
        fsm_newspaper = 1'b0;  
        fsm_NEXT_STATE = s10;  
      end  
    else if (fsm_coin == 2'b01)  
      begin  
        fsm_newspaper = 1'b0;  
        fsm_NEXT_STATE = s5;  
      end  
    else  
      begin  
        fsm_newspaper = 1'b0;  
        fsm_NEXT_STATE = s0;  
      end  
  end  
end
```

```
s5:
```

```
begin  
if (fsm_coin == 2'b10)  
begin  
fsm_newspaper = 1'b0;  
fsm_NEXT_STATE = s15;  
end  
else if (fsm_coin == 2'b01)  
begin  
fsm_newspaper = 1'b0;  
fsm_NEXT_STATE = s10;  
end  
else  
begin  
fsm_newspaper = 1'b0;  
fsm_NEXT_STATE = s5;  
end  
end
```

```
s10:
```

```
begin  
if (fsm_coin == 2'b10)  
begin  
fsm_newspaper = 1'b0;  
fsm_NEXT_STATE = s15;  
end  
else if (fsm_coin == 2'b01)  
begin  
fsm_newspaper = 1'b0;  
fsm_NEXT_STATE = s15;  
end  
else  
begin  
fsm_newspaper = 1'b0;  
fsm_NEXT_STATE = s10;  
end  
end
```

```
s15:
```

```
begin  
fsm_newspaper = 1'b1;  
fsm_NEXT_STATE = s0;  
end
```

```
endcase
```

```
fsm = {fsm_newspaper, fsm_NEXT_STATE};
```

```
end
```

```
endfunction
```

```
assign (newspaper, NEXT_STATE) = fsm(coin, PRES_STATE);
```

```
always @(posedge clock)
```

```
begin
```

```
if (reset == 1'b1)  
PRES_STATE <= s0;
```

```
else
```

```
PRES_STATE <= NEXT_STATE;
```

```
end
```

```
endmodule
```

{ output, NEXT STATE }

```

module tb_vend;

reg clock;
reg [1:0] coin;
reg reset;
wire newspaper;

vend U(coin, clock, reset, newspaper);

initial
begin
    $dumpfile("dump.vcd");
    $dumpvars(1);
    $display("\t\tTime Reset Newspaper\n");
    $monitor("%d %d %d", $time, reset, newspaper);
end

```

```

initial
begin
    clock = 0;
    coin = 0;
    reset = 1;
    #50 reset = 0;

```

```

@(negedge clock);

```

```

//put in 2 dimes
#180 coin = 2; #40 coin = 0;
#80 coin = 2; #40 coin = 0;

```

```

//put in 1 dime then 1 nickel
#180 coin = 2; #40 coin = 0;
#80 coin = 1; #40 coin = 0;

```

```

#80 $finish;
end

```

```

always
begin
    #20 clock = ~clock;
end
endmodule

```

```

//put in 3 nickels to get newspaper

```

```

#80 coin = 1; #40 coin = 0;
#80 coin = 1; #40 coin = 0;
#80 coin = 1; #40 coin = 0;

```

```


//put in 1 nickel then 1 dime

```

```

#180 coin = 1; #40 coin = 0;
#80 coin = 2; #40 coin = 0;

```

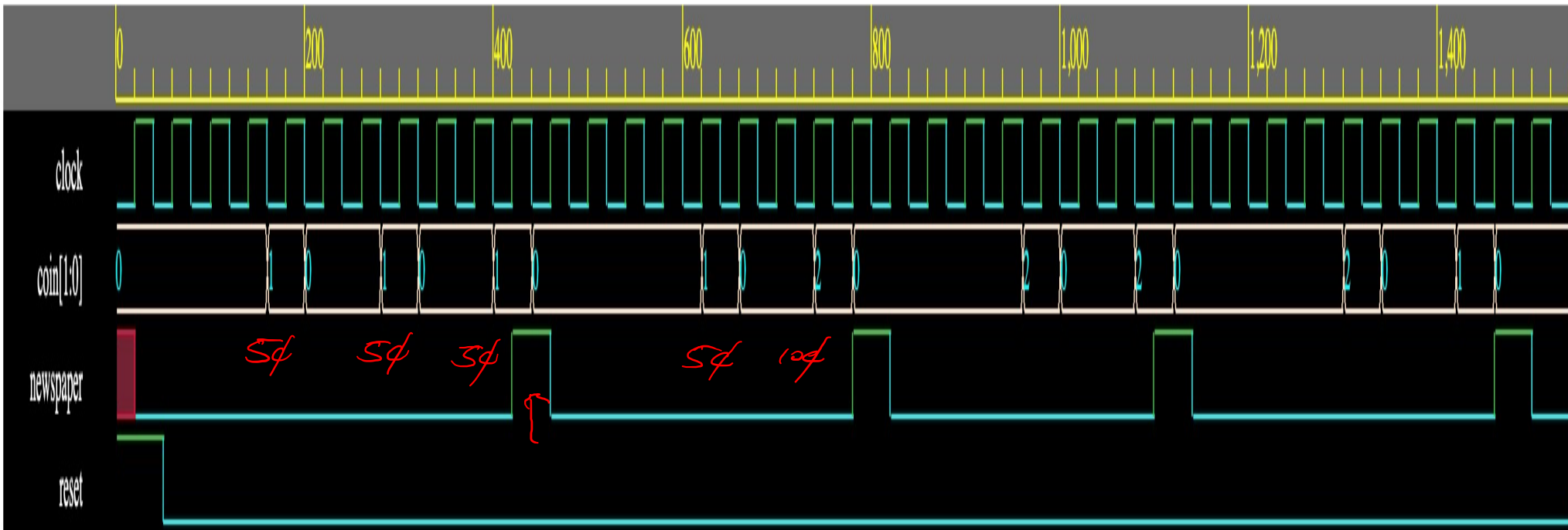

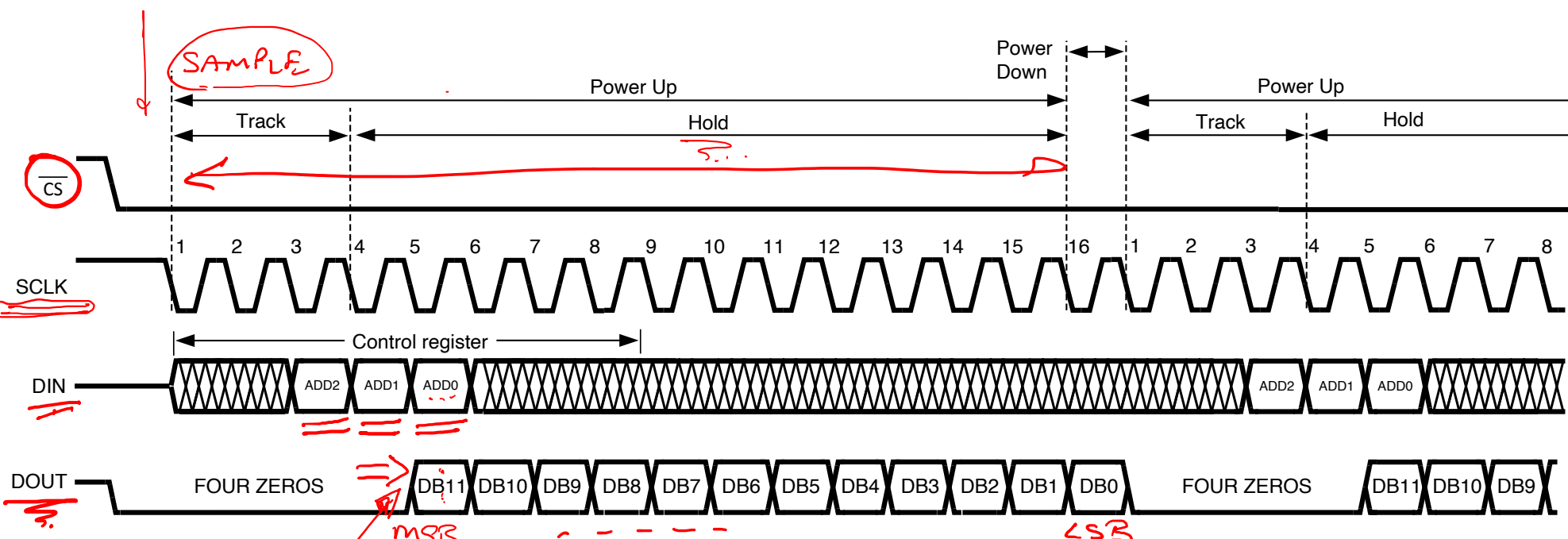


Figure 1. ADC128S022 Operational Timing Diagram

```

module ADC_CTRL(iRST,iCLK,iCLK_n,iGO,iCH,oLED,oDIN,oCS_n,oSCLK,iDOUT);
  input iRST;
  input iCLK;
  input iCLK_n;
  input iGO;
  input [2:0] iCH;
  input iDOUT;



  output [7:0] oLED;
  output oDIN;
  output oCS_n;
  output oSCLK;

  reg data;
  reg go_en;
  wire [2:0] ch_sel;
  reg sclk;
  reg [3:0] cont;
  reg [3:0] m_cont;
  reg [11:0] adc_data;
  reg [7:0] led;

  assign oCS_n = ~go_en;
  assign oSCLK = (go_en) ? iCLK:1;
  assign oDIN = data;
  assign ch_sel = iCH;
  assign oLED = adc_data[11:4];
  //assign oLED = led;

  always @(posedge iGO or negedge iRST)
  begin
    if(!iRST)
      go_en <= 0;
    else
      begin
        if(iGO)
          go_en <= 1;
        end
      end
  end
end

```

  

```

always @(posedge iCLK or negedge go_en)
begin
  if(!go_en)
    cont <= 0;
  else
    begin
      if(iCLK)
        cont <= cont+1;
      end
    end
end

always @(posedge iCLK_n)
begin
  if(iCLK_n)
    m_cont <= cont;
  end
end

always @(posedge iCLK_n or negedge go_en)
begin
  if(!go_en)
    begin
      data <= 0;
    end
  else
    begin
      if(iCLK_n)
        begin
          if(cont == 2)
            data <= ch_sel[2];
          else if(cont == 3)
            data <= ch_sel[1];
          else if(cont == 4)
            data <= ch_sel[0];
          else
            data <= 0;
          end
        end
      end
    end
end

```

iCLK_n
 is used
 to send
 "data"
 [ADC ADDRESS]
 WHICH OF
 8
 ADC UNITS
 TO
 TALK TO

iCLK → USED TO CAPTURE!


```

always @(posedge iCLK or negedge go_en)
begin
  if(!go_en)
    begin
      adc_data <= 0;
    end
  else
    begin
      if(iCLK)
        begin
          if(m_cont == 4)
            adc_data[11] <= iDOUT;
          else if(m_cont == 5)
            adc_data[10] <= iDOUT;
          else if(m_cont == 6)
            adc_data[9] <= iDOUT;
          else if(m_cont == 7)
            adc_data[8] <= iDOUT;
          else if(m_cont == 8)
            adc_data[7] <= iDOUT;
          else if(m_cont == 9)
            adc_data[6] <= iDOUT;
          else if(m_cont == 10)
            adc_data[5] <= iDOUT;
          else if(m_cont == 11)
            adc_data[4] <= iDOUT;
          else if(m_cont == 12)
            adc_data[3] <= iDOUT;
          else if(m_cont == 13)
            adc_data[2] <= iDOUT;
          else if(m_cont == 14)
            adc_data[1] <= iDOUT;
          else if(m_cont == 15)
            adc_data[0] <= iDOUT;
          //led <= adc_data[11:4];
          //else if(m_cont == 1);
          //led <= adc_data[11:4];
        end
      end
    end
end
endmodule

```

Dout

```
module ADC_tb();  
    reg iRST;  
    reg iCLK;  
    reg iCLK_n;  
    reg iGO;  
    reg [2:0] iCH;  
    reg iDOUT;  
  
    wire [7:0] oLED;  
    wire oDIN;  
    wire oCS_n;  
    wire oSCLK;  
  
    ADC_CTRL U(iRST,iCLK,iCLK_n,iGO,iCH,oLED,oDIN,oCS_n,oSCLK,iDOUT);  
  
    initial  
    begin  
        $dumpfile("dump.vcd");  
        $dumpvars(1);  
    end  
  
    initial  
    begin  
        iCLK = 0;  
        iCLK_n = 1;  
        iRST = 1;  
        iGO = 0;  
        iCH = 3'b101;  
        iDOUT = 1;  
        #10 iRST = 0;  
        #10 iRST = 1;  
        #10 iGO = 1;  
        #350  
        iDOUT = 0;  
        #350 $finish;  
    end  
  
    always  
    begin  
        #10 iCLK = ~iCLK;  
        iCLK_n = ~iCLK_n;  
    end  
endmodule
```

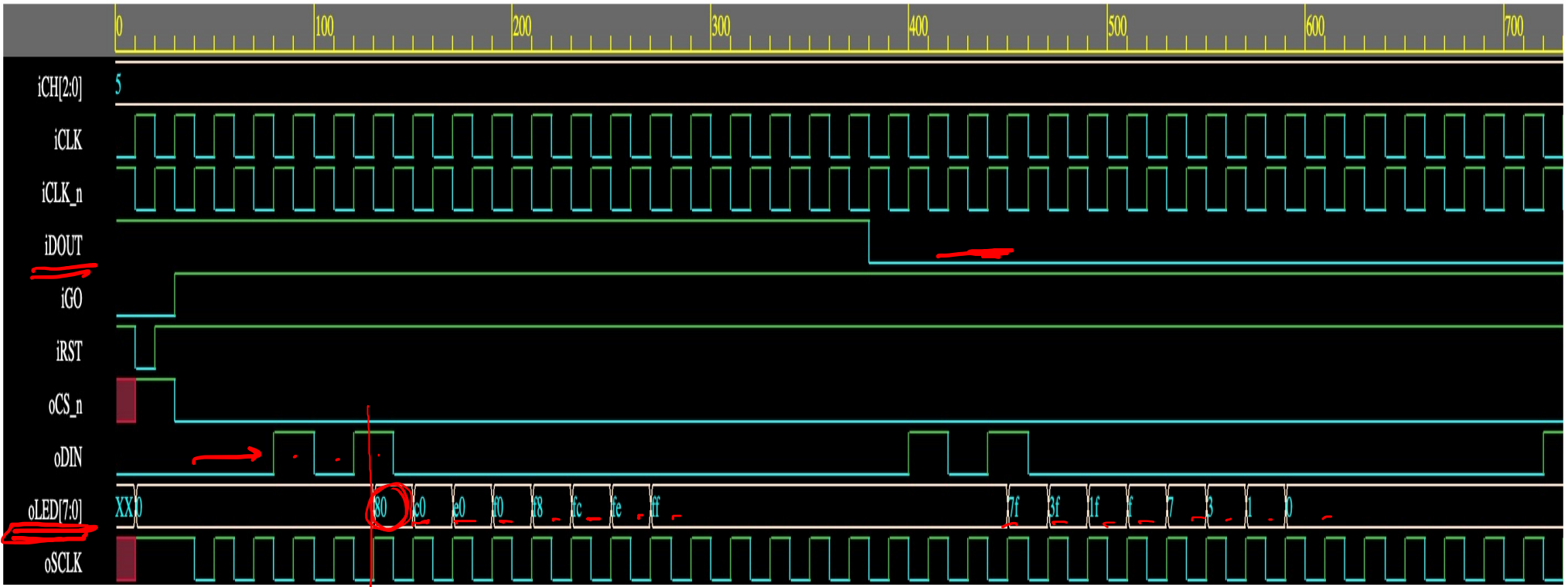

8'h xx

"VERILOG MULTIPLY ACCUMULATE"

```

module unsig_altmult_accum(
    input [7:0] dataa,
    input [7:0] datab,
    input clk, aclr, clken, sload,
    output reg [15:0] adder_out
);

// Declare registers and wires
reg [15:0] dataa_reg, datab_reg;
reg sload_reg;
reg [15:0] old_result;
wire [15:0] multa;

// Store the results of the operations on the current data
assign multa = dataa_reg * datab_reg;

// Store the value of the accumulation (or clear it)
always @ (adder_out, sload_reg)
begin
    if (sload_reg)
        old_result <= 0;
    else
        old_result <= adder_out;
end

// Clear or update data, as appropriate
always @ (posedge clk or posedge aclr)
begin
    if (aclr)
        begin
            dataa_reg <= 0;
            datab_reg <= 0;
            sload_reg <= 0;
            adder_out <= 0;
        end
    else if (clken)
        begin
            dataa_reg <= dataa;
            datab_reg <= datab;
            sload_reg <= sload;
            adder_out <= old_result + multa;
        end
    end
endmodule

```

