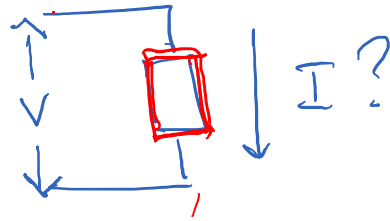


TAKE $V = V_0 e^{j\omega t}$



WHAT CURRENT IN LOAD?

$$R: I = \frac{V}{R} = \frac{V_0}{R} e^{j\omega t}$$

$$C: I = C \frac{dV}{dt} = j\omega C V_0 e^{j\omega t}$$

$$L: I = \frac{1}{L} \int V dt = \frac{1}{j\omega L} V_0 e^{j\omega t}$$

DEFINE IMPEDANCE

$$Z \equiv \frac{V}{I}$$

GEN'ERIALIZED OHM'S LAW.

$$\rightarrow R: Z_R(\omega) = R$$


$$\rightarrow C: Z_C(\omega) = \frac{1}{j\omega C} = -\frac{j}{\omega C}$$

VOLTAGE LAGS CURRENT

$$\rightarrow L: Z_L(\omega) = j\omega L$$

VOLTAGE LEAD CURRENT

SERIES RLC circuit

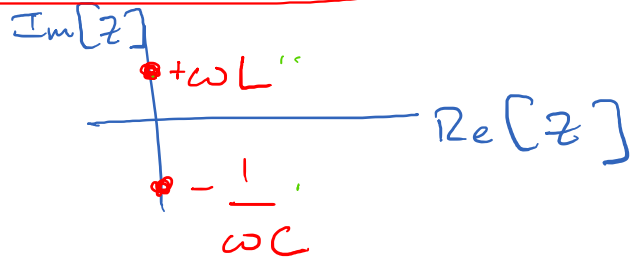

$$Z_{TOT} = j \left(\omega L - \frac{1}{\omega C} \right)$$

→ @ $\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow Z = 0$

CONSIDER



$$X = \omega L - \frac{1}{\omega C}$$


$$I = \frac{V}{R + jX} \quad |I|^2 = \frac{V_0^2}{R^2 + X^2}$$

INTRODUCE $Z_0 = \omega_0 L = \frac{1}{\omega_0 C} = \sqrt{\frac{L}{C}}$

WORK IN LIMIT $Q = \frac{Z_0}{R} \gg 1$


$$X = \frac{Z_0}{\omega_0 \omega} (\omega + \omega_0) (\omega - \omega_0)$$
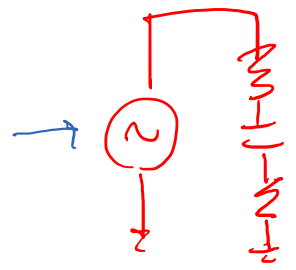
$$X \approx 2 Z_0 \frac{\Delta}{\omega_0}$$




$\omega < \omega_0$

$|I| \sim \frac{V_0}{Z_0}$

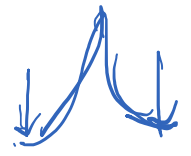


$$|I|^2 = \frac{V_0^2}{\left[\frac{Z_0}{Q}\right]^2 + 4\left[\frac{Z_0}{\omega_0}\right]^2 \Delta^2}$$

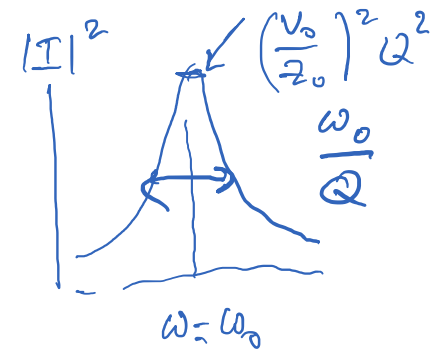


$$|I|^2 = \frac{V_0^2}{Z_0^2} Q^2 \frac{\omega_0^2}{\omega_0^2 + 4Q^2 \Delta^2}$$

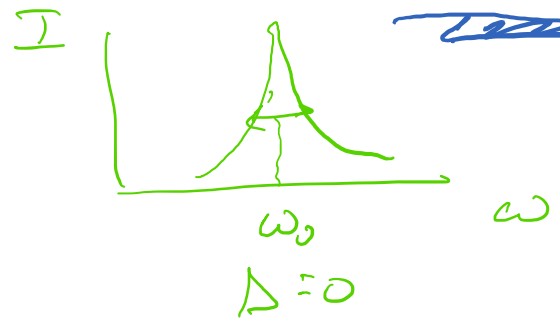$\Delta = 0 \rightarrow I_{PEAK} = \frac{V_0}{Z_0} Q = \frac{R}{\omega L} \frac{V_0}{Z_0}$ CURRENT ENHANCEMENT BY FACTOR Q



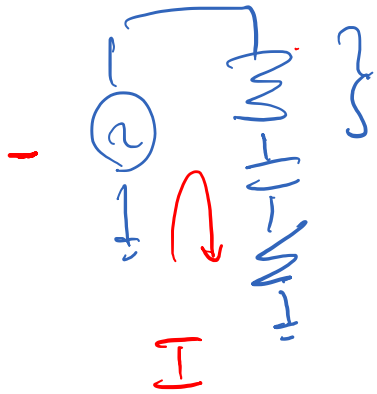FWHM $\rightarrow 2\Delta = \frac{\omega_0}{Q}$




$$V_L = \frac{V_0}{Z_0} \cdot Q \times j Z_0 = j Q V_0$$

$$V_C = \frac{V_0}{Z_0} \cdot Q \cdot (-j Z_0) = -j Q V_0$$




VOLTAGE
ENHANCEMENT

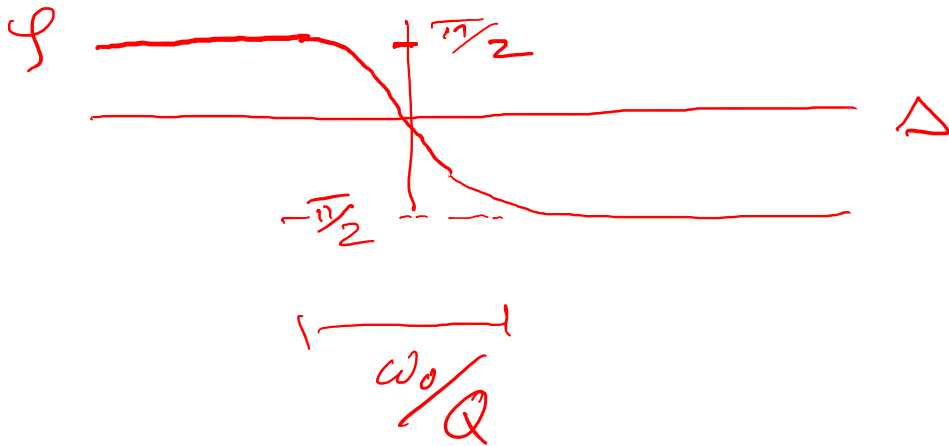

NOT AMPLIFICATION!

PARALLEL LC RESONANCE

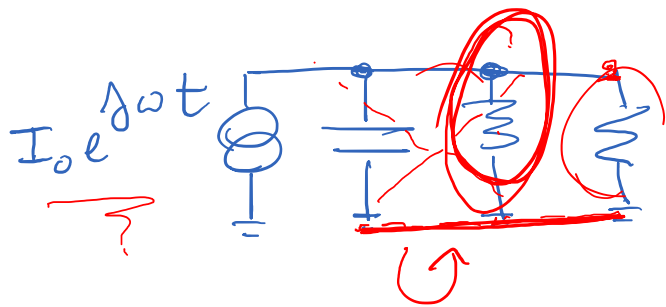

$$Y(LC) = \frac{1}{j\omega L} + j\omega C$$

$$Y=0 \text{ @ } \omega_0 = \frac{1}{\sqrt{LC}}$$

At ω_0 , introduces


$$\rightarrow Z_0 \equiv \sqrt{\frac{L}{C}} = \omega_0 L = \frac{1}{\omega_0 C}$$

$$\rightarrow Q \equiv \frac{R}{\omega_0 L} = \omega_0 R C = \frac{R}{Z_0}$$

$$\rightarrow \Delta \equiv \omega - \omega_0$$

...


$$|V|^2 = I_0^2 Z_0^2 Q^2 \frac{\omega_0^2}{\omega_0^2 + 4Q^2 \Delta^2}$$

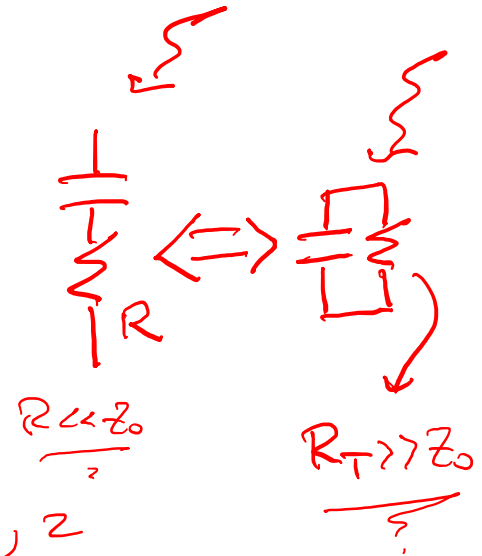

ANOTHER DEFINITION OF Q

$$Q = \frac{\omega_0 \times \text{MAX STORED ENERGY}}{\text{POWER DISSIPATION}}$$
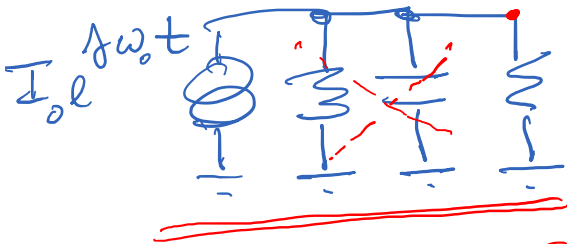
$$H = \frac{Q^2}{2C} + \frac{\phi^2}{2L}$$




$$V_{\text{max}} = I_0 R$$

$$Q = \frac{\omega_0 \cdot \frac{1}{2} C I_0^2 R^2}{\frac{1}{2} I_0^2 R}$$

$$= \omega_0 R C$$


AS EXPECTED

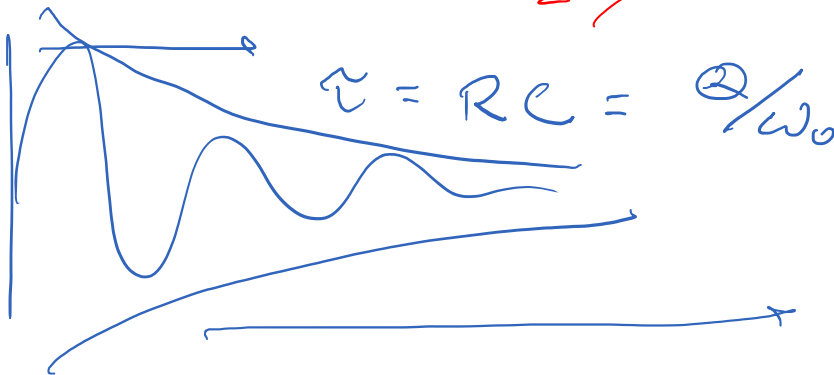

$$\tau = RC = Q/\omega_0$$

IMPEDANCE TRANSFORMATION

$$X \equiv \frac{1}{\omega C}$$

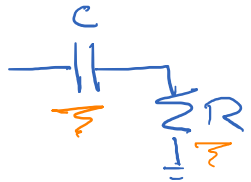

$$Z = R + \frac{1}{j\omega C} = R - jX$$

j TAKE $X \gg R$

WHAT IS Y TO GROUND?

$$Y = \frac{1}{R - jX} = \frac{R + jX}{R^2 + X^2} \approx \frac{R}{X^2} + \frac{j}{X}$$



$$\Rightarrow R_T = \frac{(\frac{1}{\omega C})^2}{R}$$



$$C_c \approx 1 \text{ pF}$$


$$\tau = 5 \cdot 10^{-11} \rightarrow 50 \text{ ps}$$

RESONANT IMPEDANCE TRANSFORMATION

$$Z_C \equiv \frac{1}{\omega C}$$

$$Z_L \equiv \omega L$$

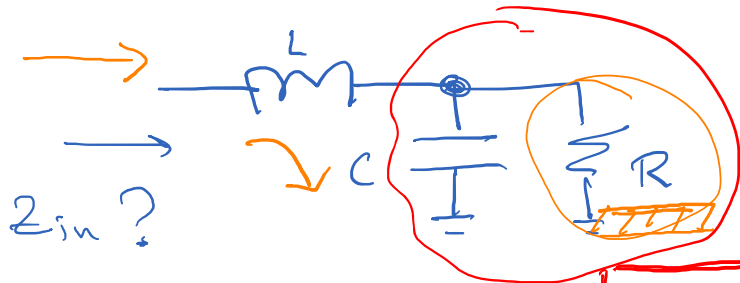TRANSFORM HIGH RESISTANCE TO LOW RESISTANCE




DEFINE $\omega_0 \equiv \frac{1}{\sqrt{LC}}$

$$Z_0 = \omega_0 L = \frac{1}{\omega_0 C} = \sqrt{\frac{L}{C}}$$

CONSIDER $Z_0 \ll R$


$$Y = \frac{1}{R} + j \frac{1}{Z_C}$$
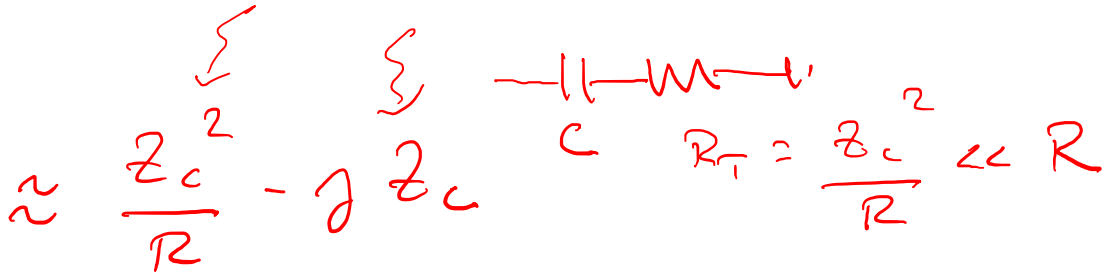
$$Z(RC) = \frac{\frac{1}{R} - j/Z_C}{\frac{1}{R^2} + \frac{1}{Z_C^2}} \approx \frac{Z_C^2}{R} - j Z_C$$





$R \xrightarrow{\text{TRANSFORMS TO}} R_T = \frac{Z_0^2}{R} \ll R$

"RF SET"

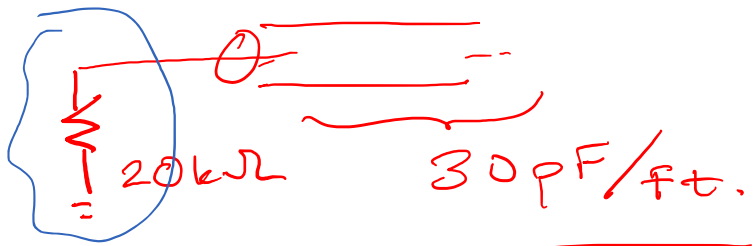

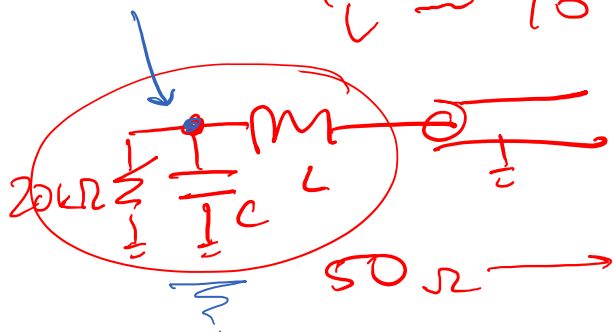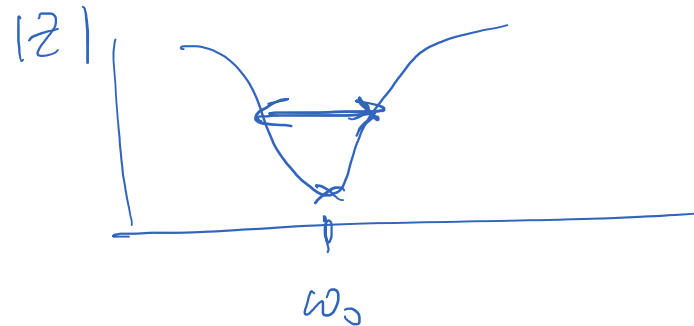
$$Z \sim 10^4 \cdot 10^{-10} \sim 10^{-6} \Omega'$$




$$Q = \frac{R}{Z_0}$$
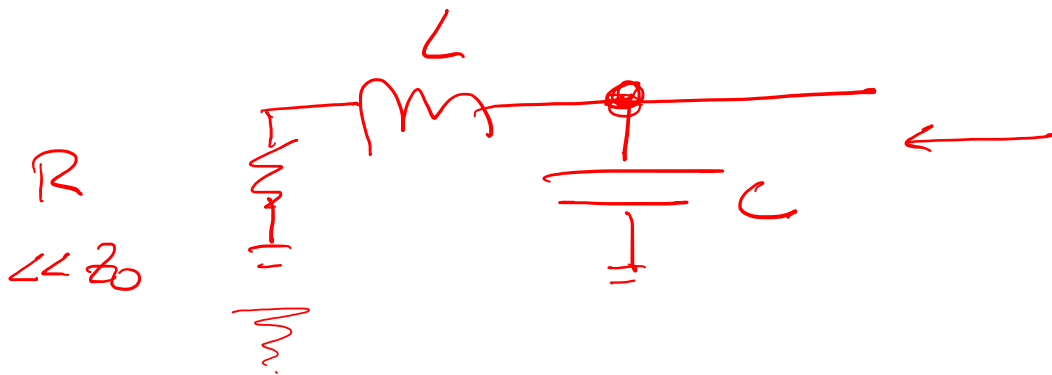
$$R_{\text{HIGH}} \rightarrow \frac{R_{\text{HIGH}}}{Q^2}$$



TRANSMISSION LINES

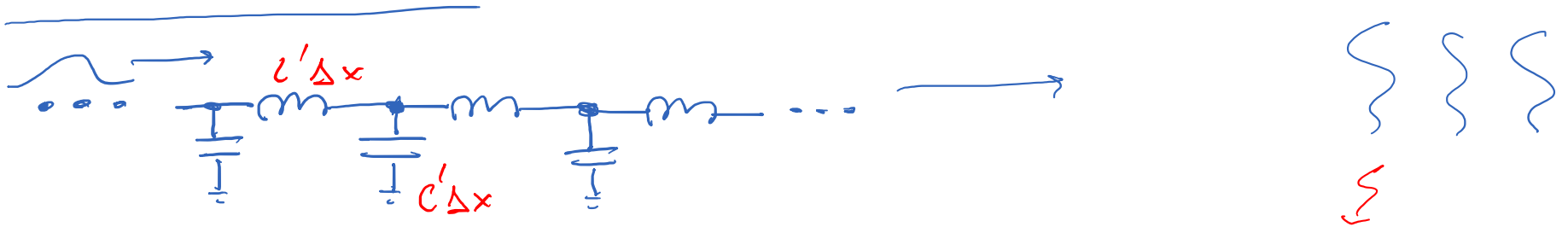

KIRCHHOFF VOLTAGE LAW: $V(x) - V(x + \Delta x) = L' \Delta x \frac{dI}{dt}$

$$\Rightarrow \frac{\partial V}{\partial x} = -L' \frac{\partial I}{\partial t} \leftarrow$$

KIRCHHOFF CURRENT LAW: $I(x + \Delta x) = I(x) - C' \Delta x \frac{dV}{dt}$

$$\Rightarrow \frac{\partial I}{\partial x} = -C' \frac{\partial V}{\partial t} \leftarrow$$

$$\frac{\partial^2 V}{\partial x^2} = -L' \frac{\partial^2 I}{\partial x \partial t} ; \quad \frac{\partial^2 V}{\partial t^2} = -\frac{1}{C'} \frac{\partial^2 I}{\partial x \partial t}$$

$$\Rightarrow \frac{\partial^2 V}{\partial x^2} = L' C' \frac{\partial^2 V}{\partial t^2}, \quad \text{Similarly for } I$$

WAVE EQUATION

$$\frac{\partial^2 \psi}{\partial x^2} - \frac{1}{v^2} \frac{\partial^2 \psi}{\partial t^2} = 0$$

TRAVELING WAVE
SOLUTIONS OF FORM

$$e^{j(\pm kx - \omega t)} = e^{j \frac{2\pi}{\lambda} (\pm x - vt)}$$

WAVELENGTH λ , PHASE VELOCITY v

$$\underline{k = \frac{2\pi}{\lambda}} ; \quad \underline{v = \lambda f = \frac{\omega}{k}}$$

FOR OUR TRANSMISSION LINE,

$$\frac{\partial^2 V}{\partial x^2} - L' C' \frac{\partial^2 V}{\partial t^2} = 0$$


$$\underline{\text{PHASE VELOCITY } v = \frac{1}{\sqrt{L' C'}}$$

EXAMPLES



$$C' = \frac{2\pi\epsilon}{\ln(b/a)}$$

$$L' = \frac{\mu}{2\pi} \ln(b/a)$$

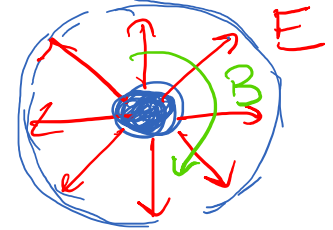

BNC \rightarrow 30 pF/ft.

μUT


$$v = \frac{1}{\sqrt{\epsilon\mu}}$$

$\mu \rightarrow \mu_0$

$\epsilon \sim \epsilon_r \epsilon_0$

$$v = \frac{c}{\sqrt{\epsilon_r}}$$

COPLANAR WAVEGUIDE

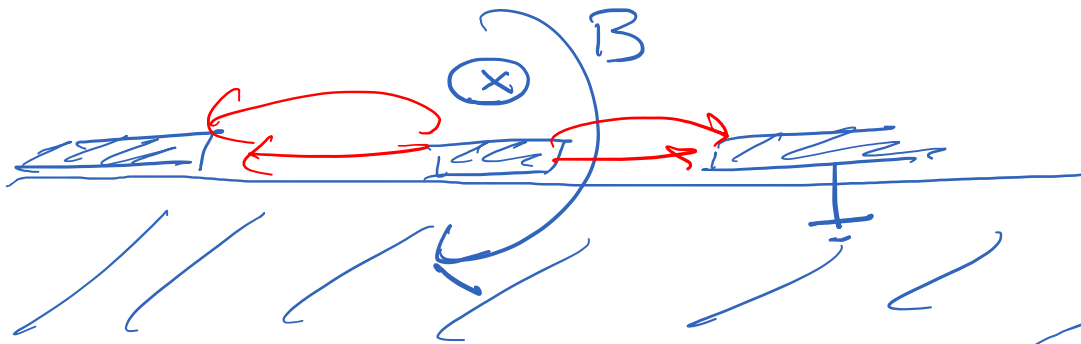

$$C = \frac{1}{\sqrt{\epsilon_0 \mu_0}}$$

FOR COAX
 $v \sim 2 \cdot 10^8 \text{ m/s}$

[SWS FOR (m)]

$$\boxed{V(x,t) = V_0 e^{j(kx - \omega t)}}$$

WHAT IS $I(x,t)$?

$$\frac{\partial I}{\partial t} = -\frac{1}{L'} \frac{\partial V}{\partial x} = -\frac{1}{L'} jk V_0 e^{j(kx - \omega t)}$$

$$I = -\frac{1}{L'} jk V_0 \int e^{j(kx - \omega t)} dt$$

$$= +\frac{1}{L'} \frac{jk}{j\omega} V_0 e^{j(kx - \omega t)}$$

RECALL $\frac{\omega}{k} = \frac{1}{\sqrt{LC}}$

$$= \sqrt{\frac{C}{L}} V_0 e^{j(kx - \omega t)}$$

DEFINE

$$\underline{Z_0 = \sqrt{\frac{L}{C}}}$$

CHARACTERISTIC IMPEDANCE OF TRANSMISSION LINE



TRANSMISSION LINE w/ MATCHED TERMINATION

