


# OPERATIONAL AMPLIFIERS

HIGH-GAIN MULTISTAGE TRANSISTOR AMPS

BJT OR FET


INTEGRATED CIRCUIT:

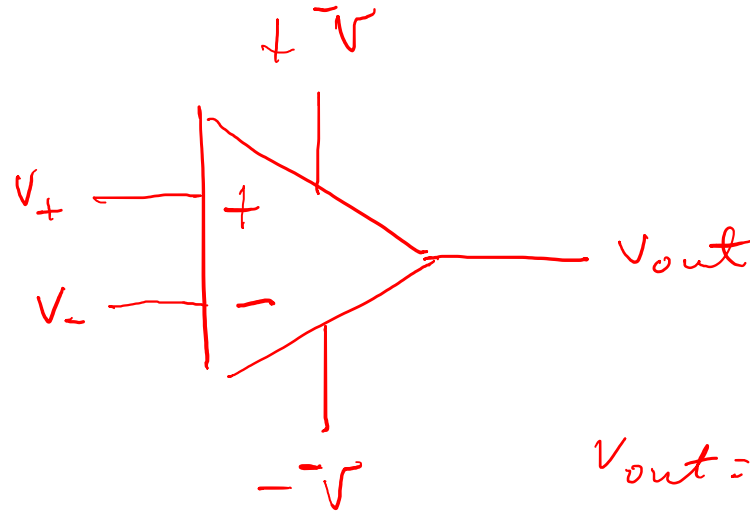HUNDREDS OF TRANSISTORS, THIN-FILM R & C  
MULTILAYER MICRO/NANOFAB




$A_0 \gg 1$


$V_{out} = A_0 [V_+ - V_-]$

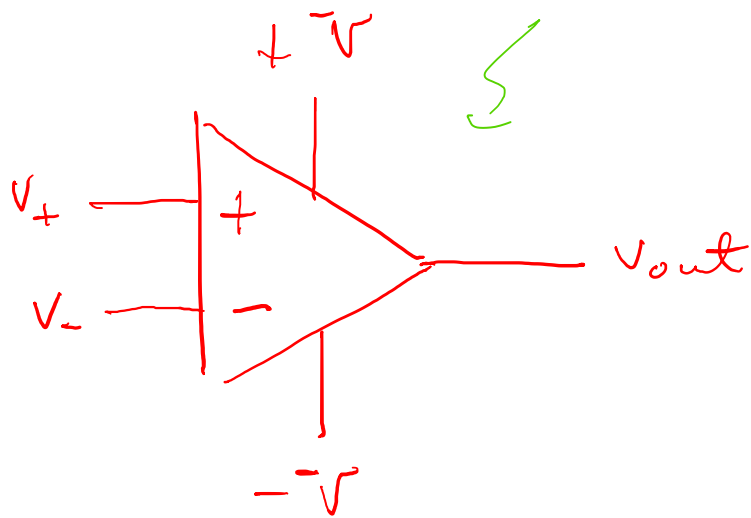
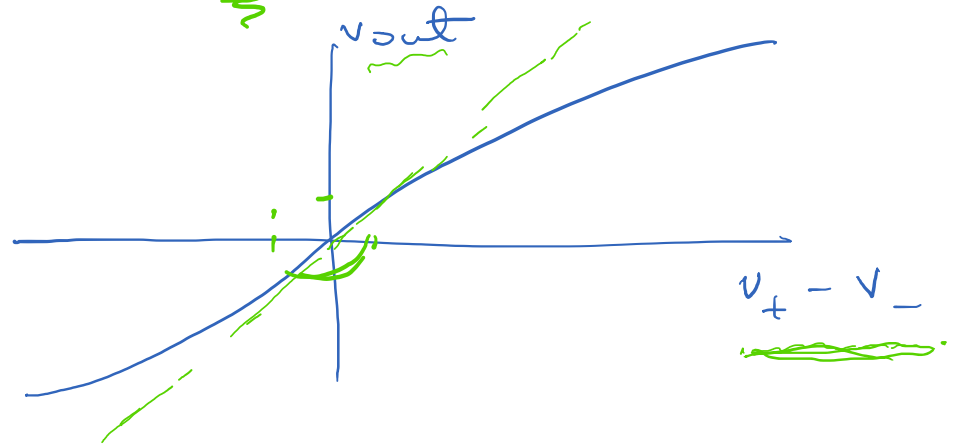
$$v_{out} = \underbrace{A_0}_{\text{green}} [V_+ - V_-]$$



EQUIVALENT CIRCUIT

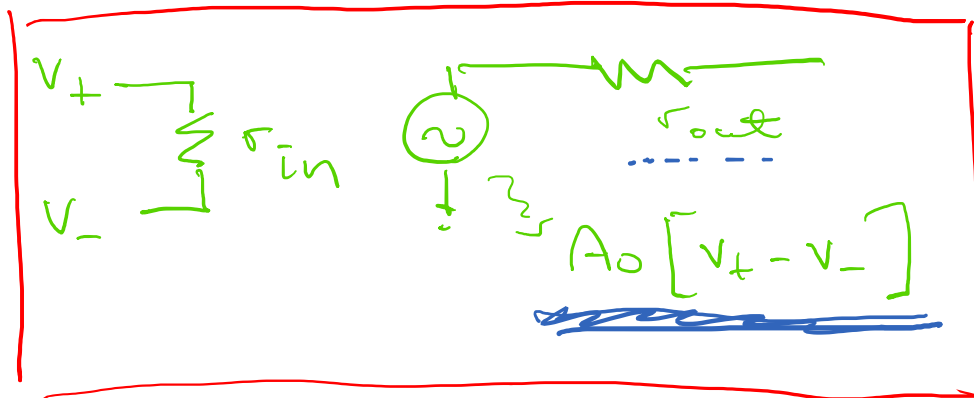

$$r_{in} \sim 10^5 \Omega \text{ [BJT]} \rightarrow 10^9 \Omega \text{ [FET]}$$

$$r_{out} \sim 10 - 10^3 \Omega$$



IDEAL OP AMP:

$$r_{in} = \infty ; r_{out} = 0$$

$$A_0 \rightarrow \infty$$

OP AMPS ARE ALMOST ALWAYS USED WITH NEGATIVE FEEDBACK  
 → EXCHANGE GAIN FOR LINEARITY.

CONSIDER

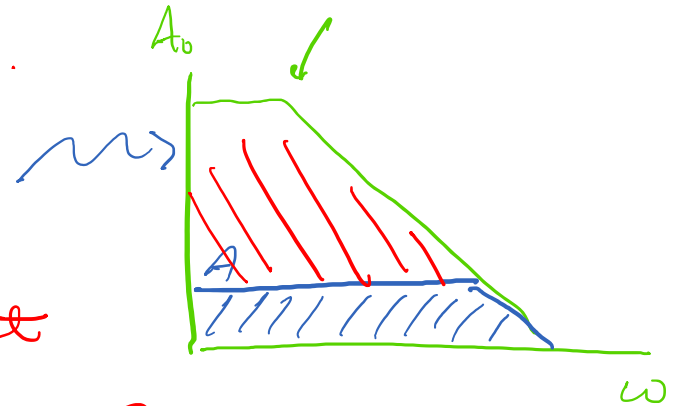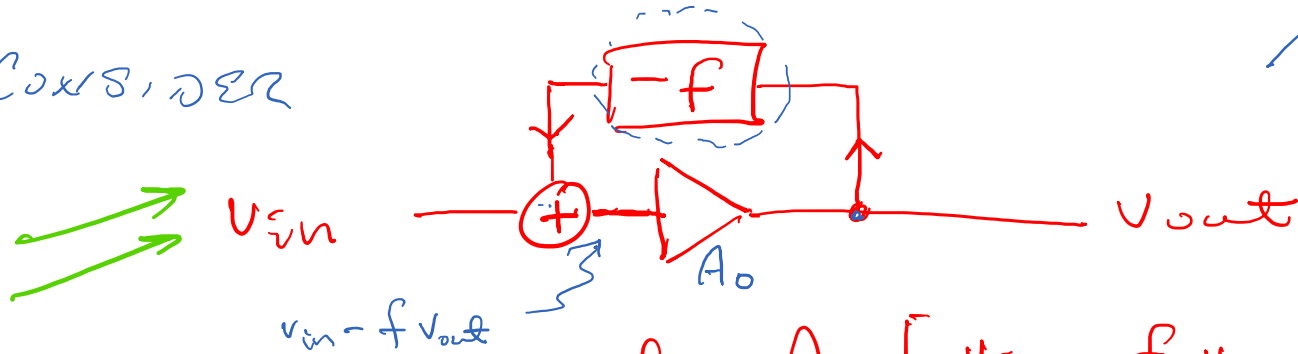

$$v_{out} = A_0 [v_{in} - f v_{out}] \dots$$


$$v_{out} (1 + A_0 f) = A_0 v_{in}$$

$$\frac{v_{out}}{v_{in}} = \frac{A_0}{1 + A_0 f} v_{in} ; \text{ IF } A_0 \gg 1$$

CLOSED LOOP GAIN  $A \equiv \frac{v_{out}}{v_{in}} \approx \frac{1}{f}$

INDEPENDENT  
 OF  
 DETAILS OF  $A_0$

# SOME JARGON

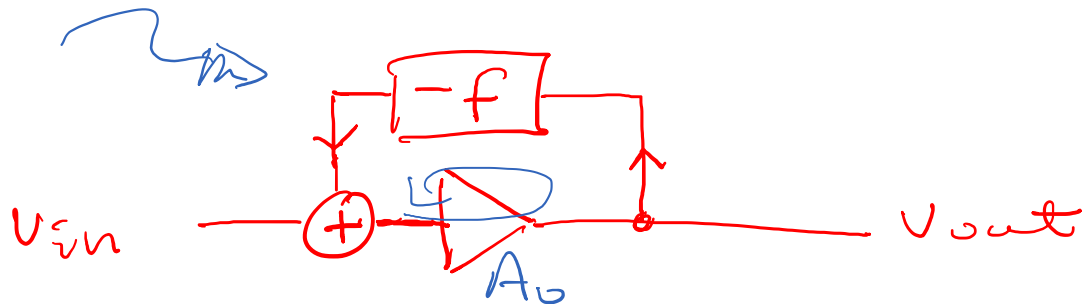

OPEN LOOP GAIN :  $A_0$

$$V_{out} = A_0 [V_+ - V_-]$$


IN ABSENCE OF FEEDBACK.

CLOSED LOOP GAIN :  $\frac{V_{out}}{V_{in}}$  IN CONFIGURATION W/ NEGATIVE F.B.

$$A = \frac{V_{out}}{V_{in}} \approx \frac{1}{f}$$

LOOP GAIN :  $A_0 f$

# "GOLDEN RULES"

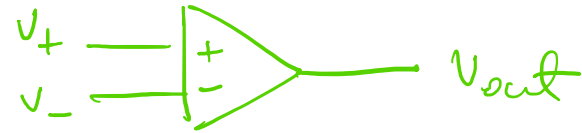

①

$$V_+ = V_-$$

ANY NONZERO  $V_+ - V_- \rightarrow$  GENERATE  
A HUGE  $v_{out}$ , THAT GETS SAMPLED &  
FEED BACK IN SUCH A WAY THAT  
 $V_+ - V_-$  GETS PUSHED TO ZERO.

②

INPUTS DRAW NO CURRENT

# NONINVERTING OP AMP STAGE

"VOLTAGE FEEDBACK"


Rule 1

$$V_+ = V_-$$

$$V_- = V_{in}$$




Rule 2: INV. INPUT DRAWS NO CURRENT

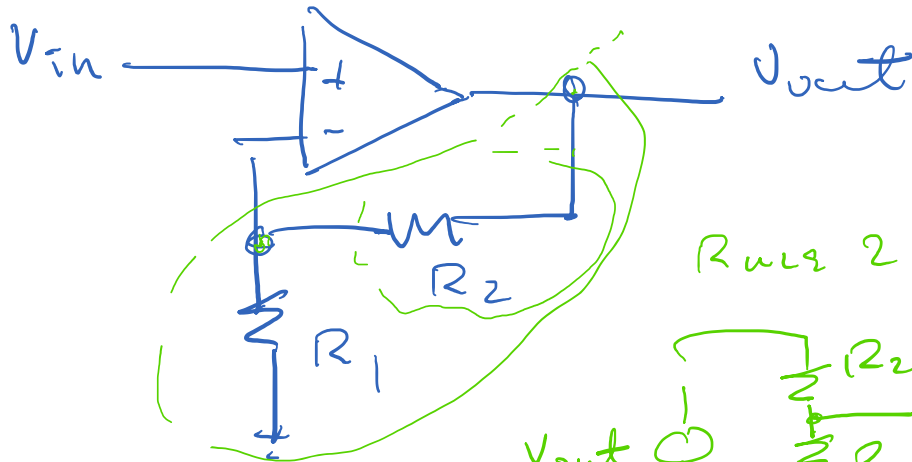

$$V_{in} = \frac{R_1}{R_1 + R_2} V_{out}$$


$$A = \frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$$

FOLLOWER

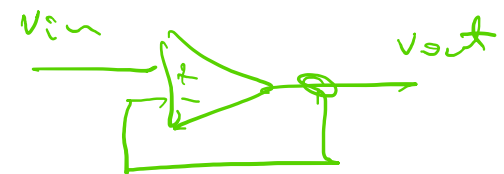

$$A = 1$$

# INVERTING OP AMP STAGE

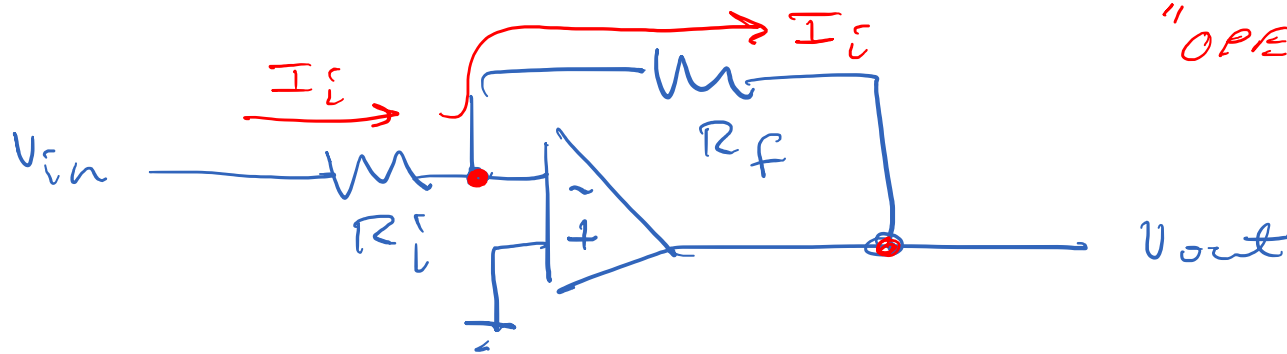

"OPERATIONAL  
FEEDBACK"

RULE 1:  $V_- = V_+ = 0$  "VIRTUAL GROUND"


$$I_i = \frac{V_{in}}{R_i}$$

RULE 2: INVERTING INPUT DRAWS NO CURRENT

$$V_{out} = V_- - R_f I_i = -\frac{R_f}{R_i} V_{in}$$

$$A = -\frac{R_f}{R_i}$$

## EXAMPLES

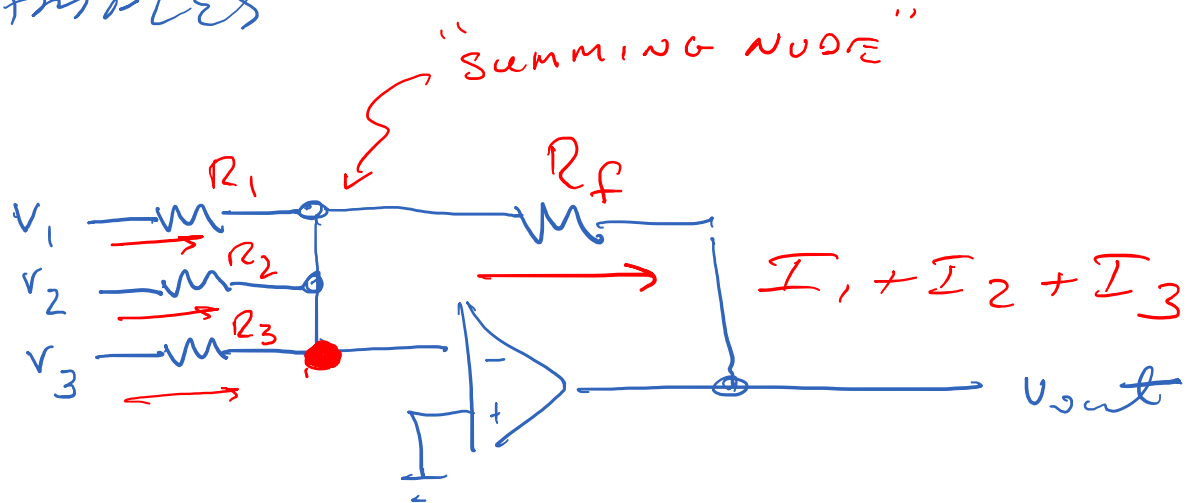


RULE 1:  $V_- = V_+ = 0$  VIRTUAL GROUND

$$I_1 = \frac{V_1}{R_1} ; I_2 = \frac{V_2}{R_2} ; I_3 = \frac{V_3}{R_3}$$

RULE 2: ALL CURRENTS SUM @ INV. INPUT &  
FLOW ACROSS  $R_f$
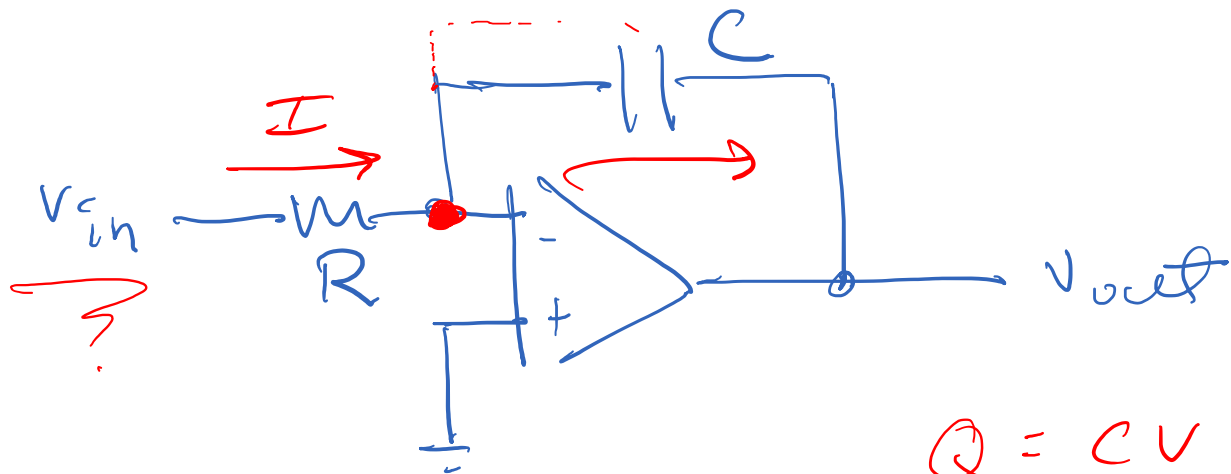
$$V_{out} = -R_f \left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$





TIME-DOMAIN ANALYSIS


$$I = \frac{V_{in}}{R}$$

$$Q = CV$$


$$I = C \frac{dV}{dt}$$

$$V_{out} = - \frac{1}{C} \int I dt$$
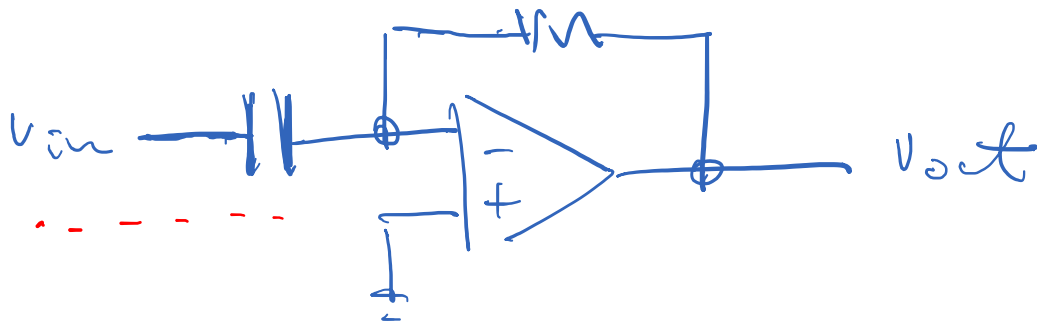
$$V_{out} = - \frac{1}{RC} \int V_{in} dt$$




say,  $v_{in} = v_0 e^{j\omega t}$

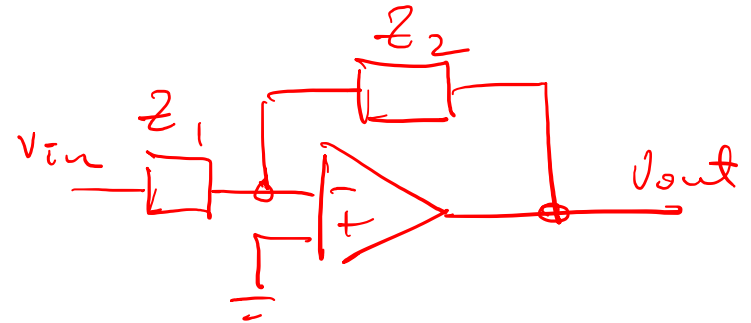


$$A = \frac{v_{out}}{v_{in}} = -\frac{Z_2}{Z_1}$$

$$A = \frac{-R}{\left(\frac{1}{j\omega C}\right)} = -j\omega RC$$


HIGH-PASS  
FILTER.

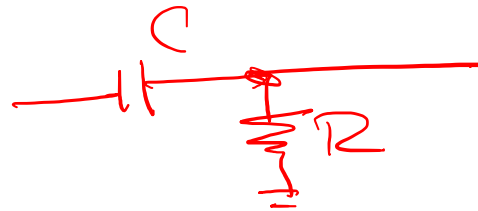

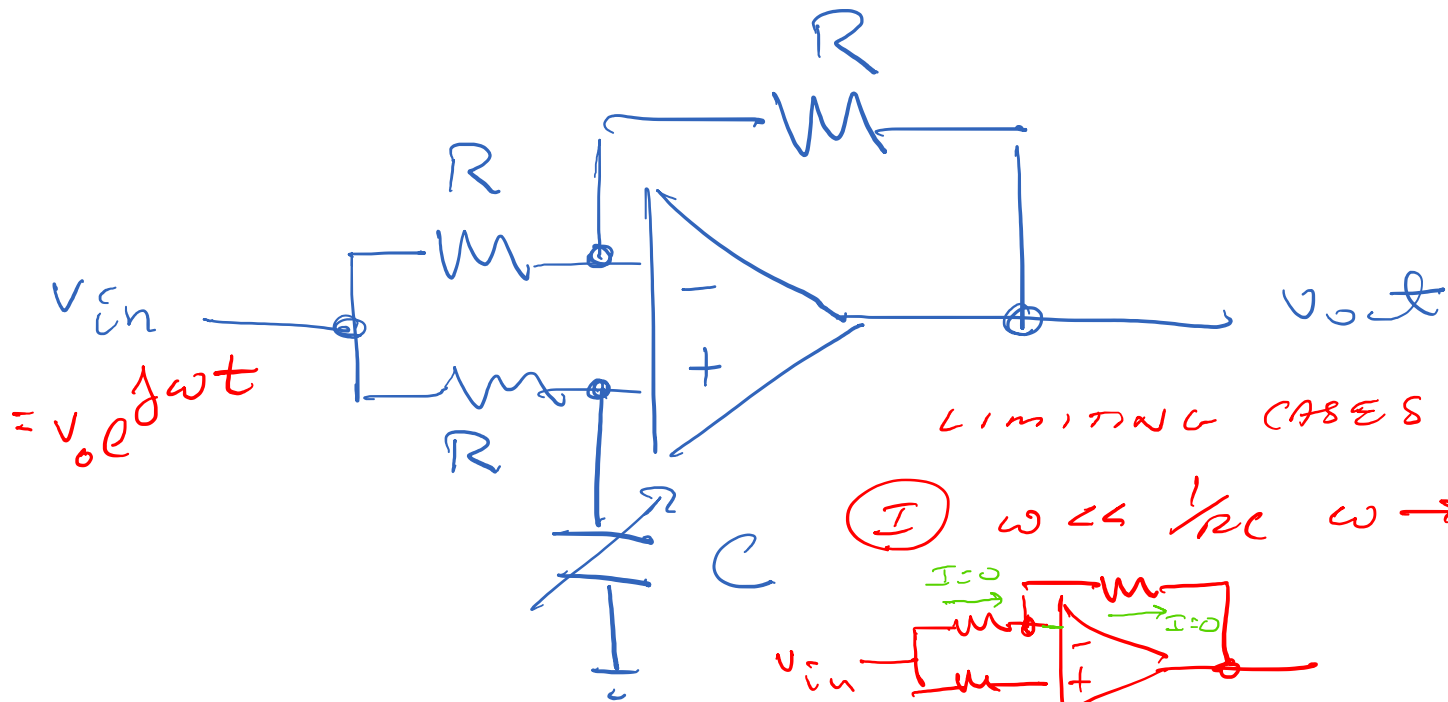

LIMITING CASES:

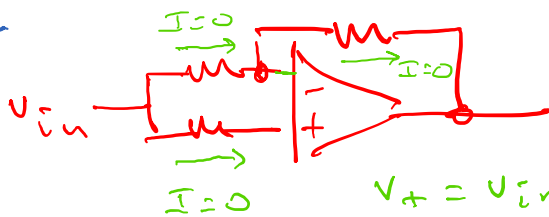(I)  $\omega \ll 1/RC \quad \omega \rightarrow 0$



$V_+ = V_{in} = V_-$

$V_{out} = V_{in}$


$\rightarrow A = +1$   
@  $\omega = 0$

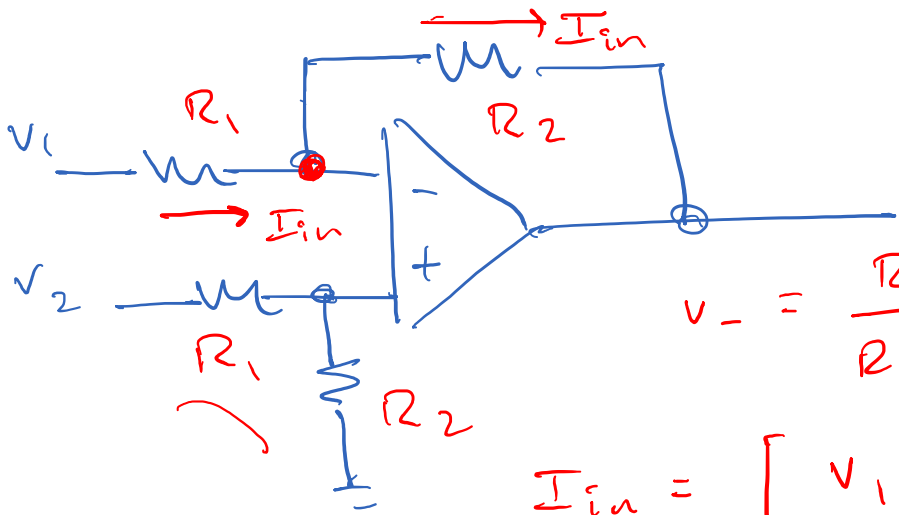(II)  $\omega \gg 1/RC \quad \omega \rightarrow \infty$



$\frac{V_{out}}{V_{in}} = -\frac{R}{R} = -1$

$A = -1$   
@  $\omega \rightarrow \infty$



$$V_+ = \frac{R_2}{R_1 + R_2} V_2$$


$$V_- = \frac{R_2}{R_1 + R_2} V_1$$

$$I_{in} = \left[ V_1 - \frac{R_2}{R_1 + R_2} V_2 \right] \frac{1}{R_1}$$

$$V_{out} = \underbrace{\frac{R_2}{R_1 + R_2} V_2}_{V_-} - \underbrace{\left[ V_1 - \frac{R_2}{R_1 + R_2} V_2 \right] \frac{1}{R_1} \cdot R_2}_{I_{in}}$$

$$V_{out} = \frac{R_2}{R_1} [V_2 - V_1]$$


DIFFERENTIAL  
GAIN

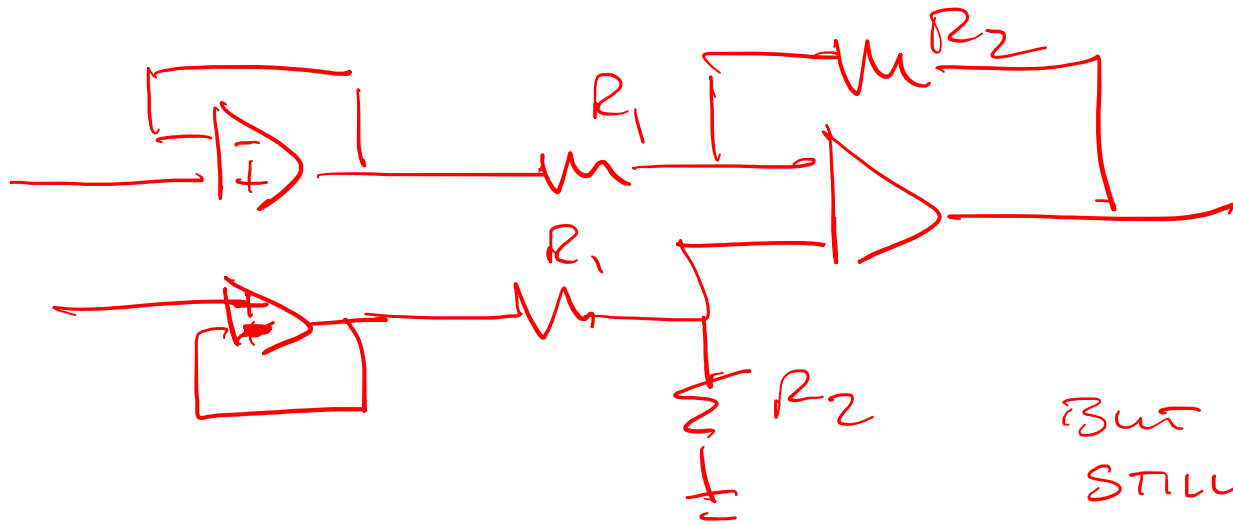


But  
STILL NEEDED

GOOD MATCH  
OF  
 $R_1$ 'S

# INSTRUMENTATION AMPLIFIER

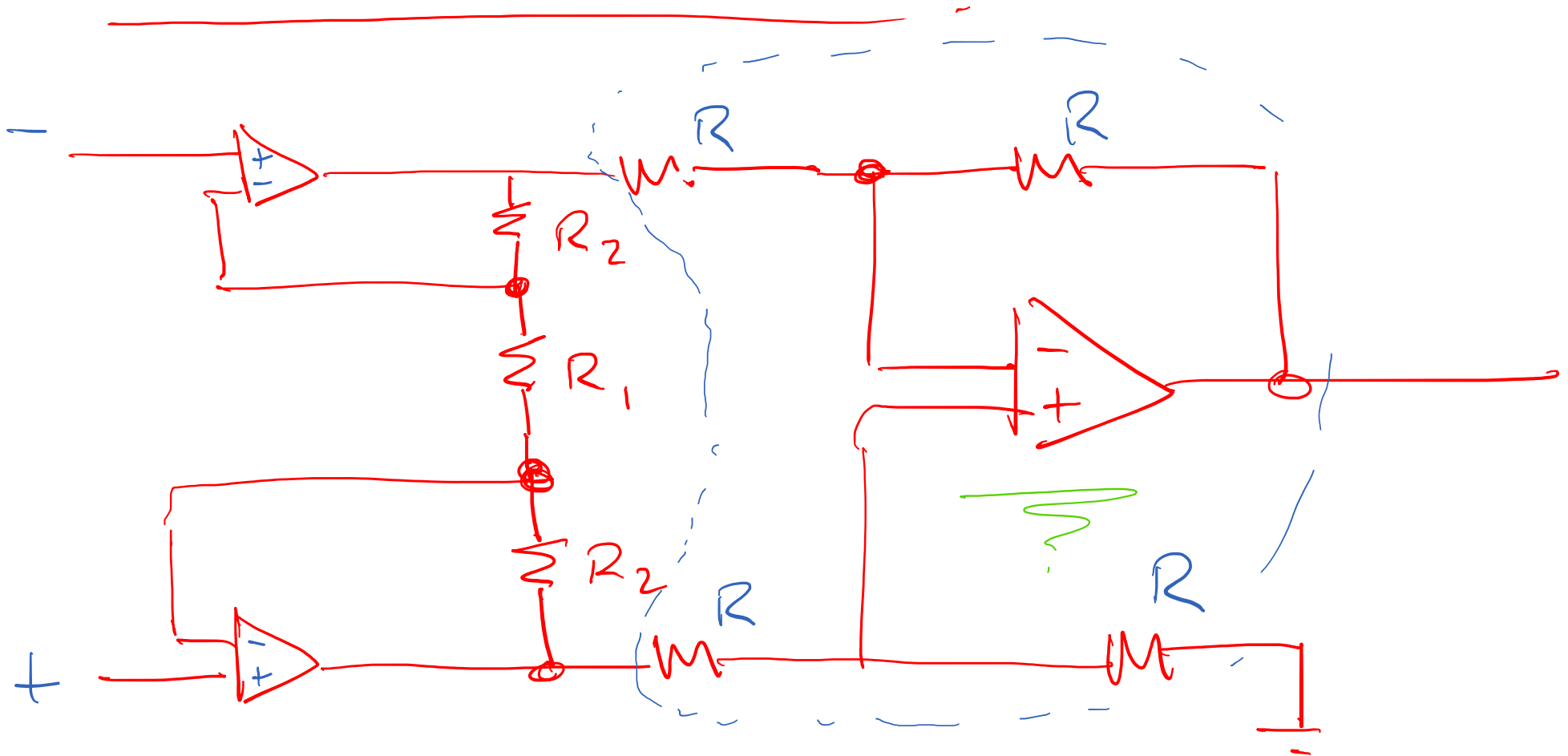

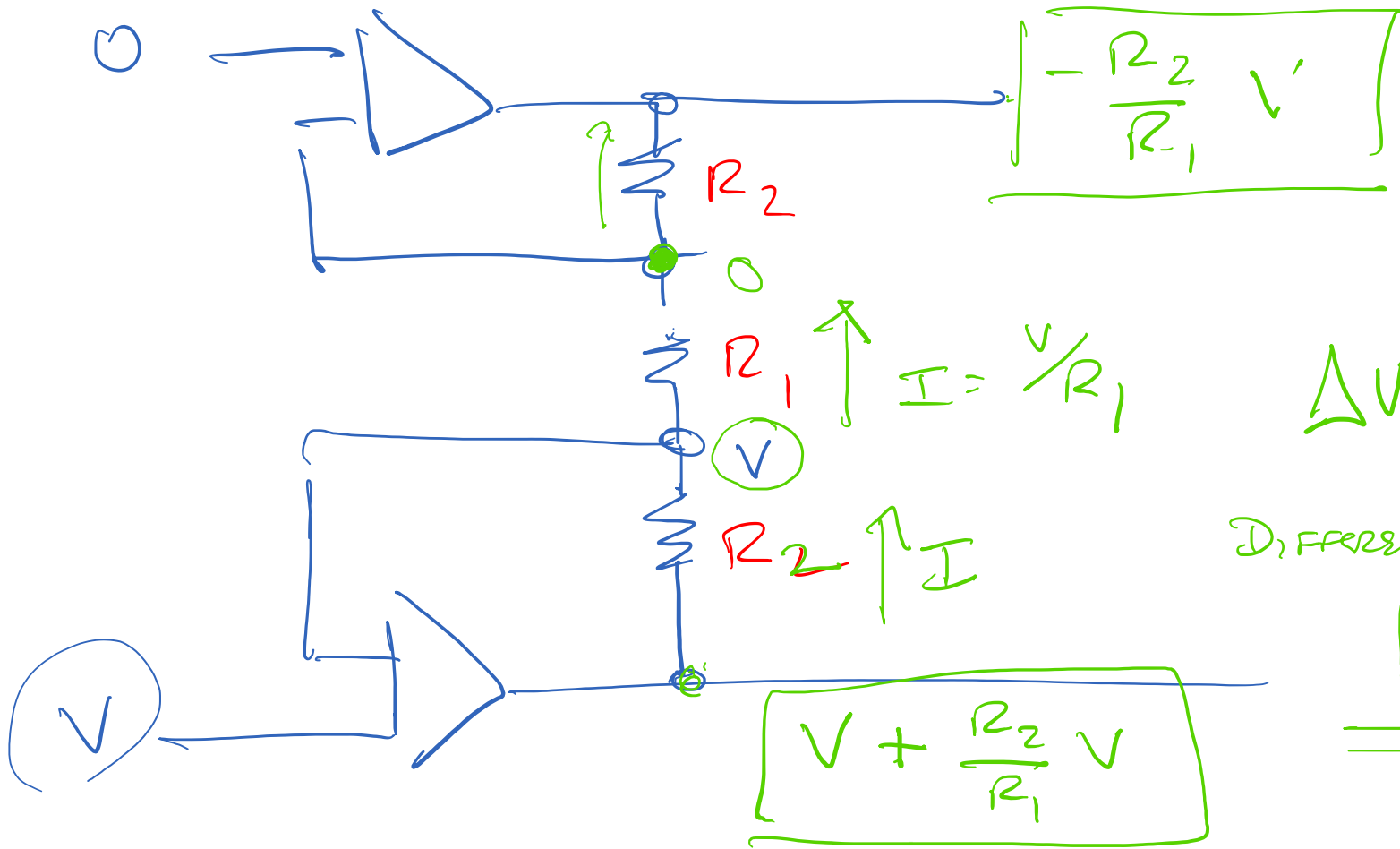

$$\Delta V = V + \frac{2R_2}{R_1} V$$

DIFFERENTIAL GAIN

$$\underline{\underline{1 + \frac{2R_2}{R_1}}}$$