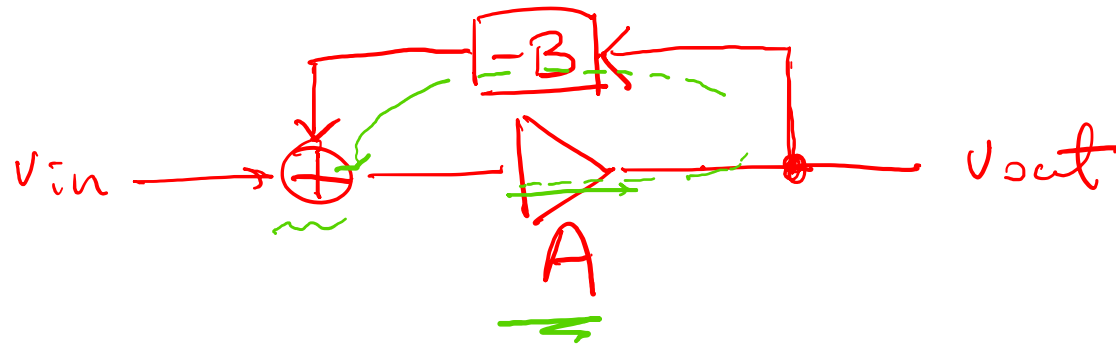


NEGATIVE FEEDBACK



$$v_{out} = \frac{A}{1 + AB} v_{in} \approx \underline{\underline{\frac{1}{B}}}$$

A : OPEN LOOP GAIN

$$v_{out} = A [v_{+} - v_{-}]$$


B : FEEDBACK FRACTION PROGRAMMED BY EXTERNAL R'S

$\rightarrow G \approx \frac{1}{B}$: CLOSED LOOP GAIN

AB : LOOP GAIN

*
$$\underline{\underline{A}} = \underbrace{(AB)}_{\text{LOOP GAIN}} \underbrace{\frac{1}{B}}_{\text{CLOSED LOOP GAIN}} = (AB)G$$


$$\log A = \log (AB) + \log G$$

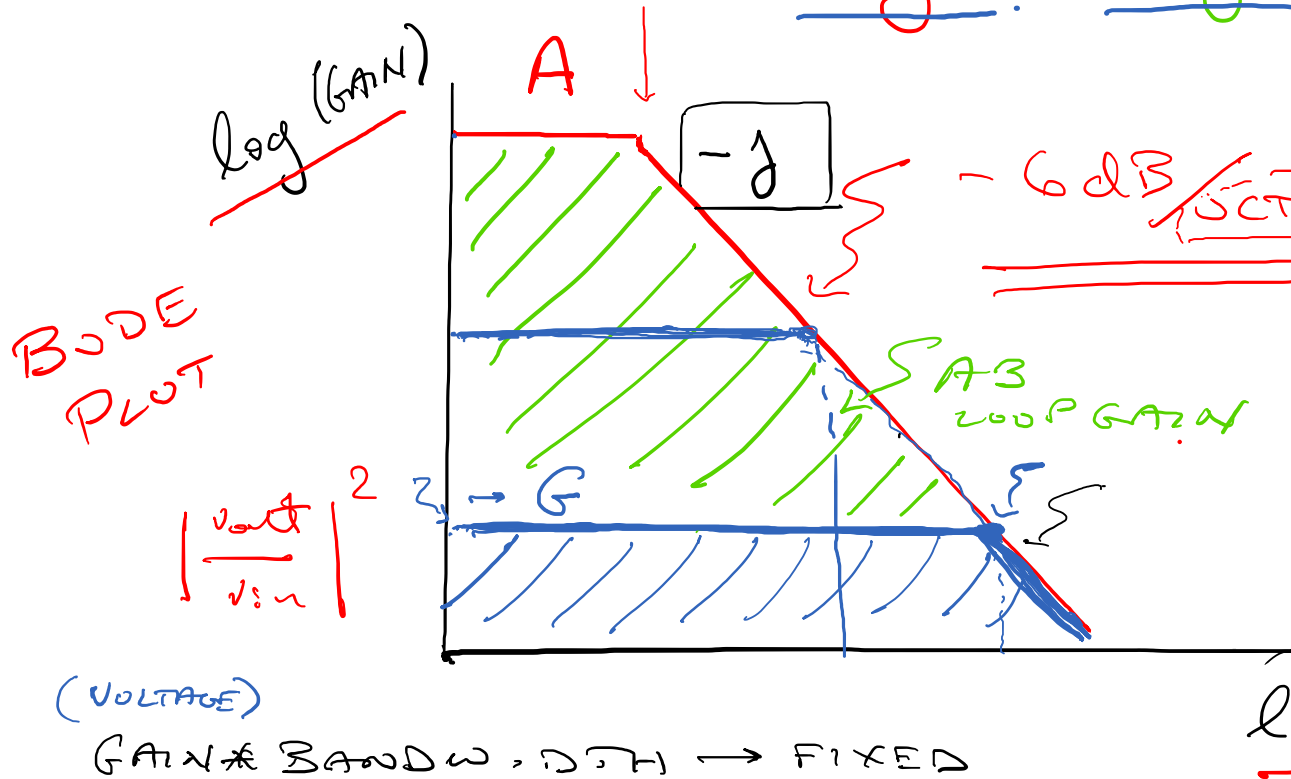

FACTOR 2



3 dB -> FACTOR 2

6 dB FACTOR 4

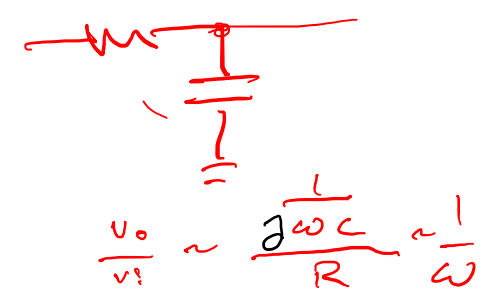


MORE DETAILED LOOK

NON INVERTING STAGE

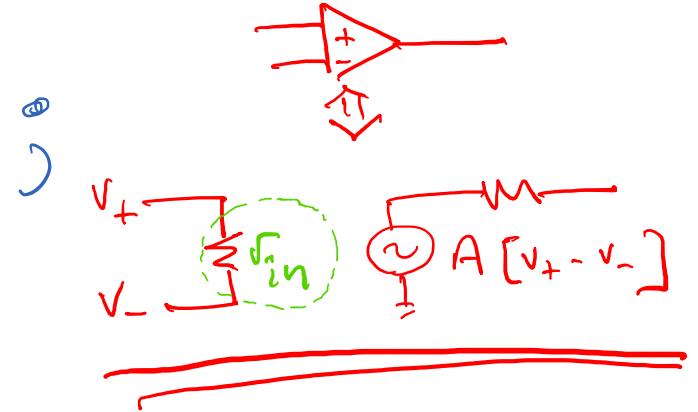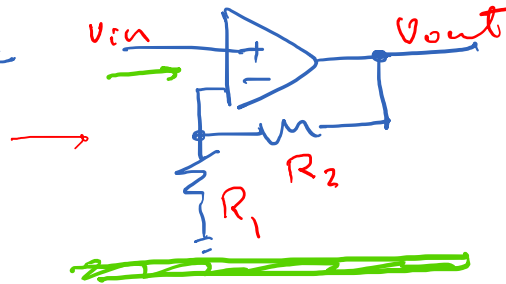

EQUIVALENT:

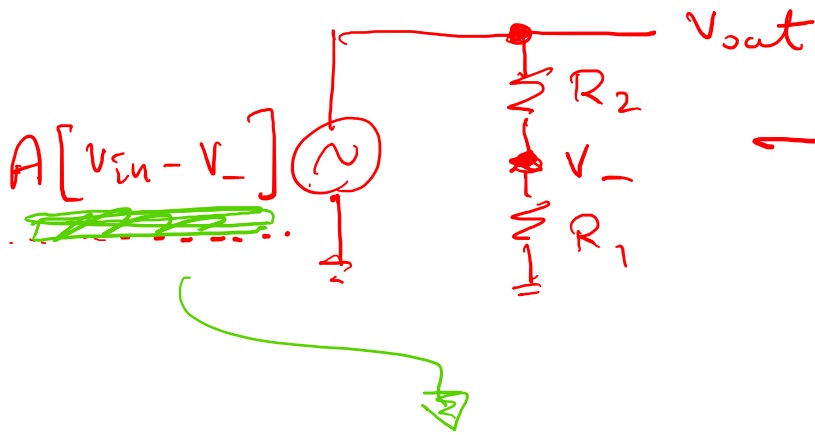

$$v_- = \frac{R_1}{R_1 + R_2} A [v_{in} - v_-]$$


$$= \frac{A R_1}{(A+1)R_1 + R_2} v_{in}$$

$$G = \frac{v_{out}}{v_{in}} = A \frac{R_1 + R_2}{(A+1)R_1 + R_2}$$

As $A \rightarrow \infty$,

$$G \rightarrow 1 + \frac{R_2}{R_1}$$

NON INVERTING STAGE: INPUT IMPEDANCE

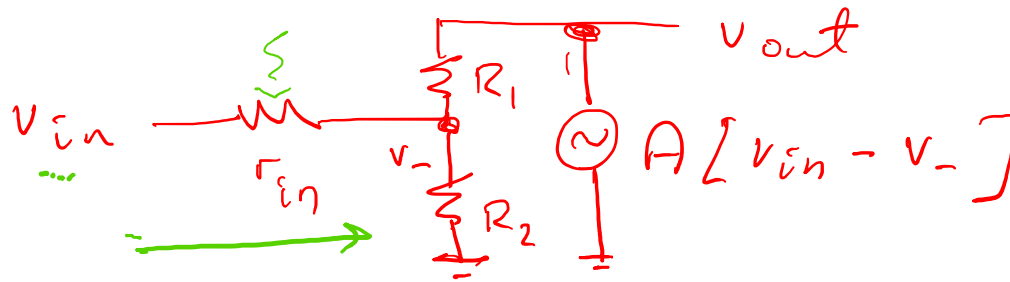

$$v_{out} = G v_{in}$$

$$I_{in} = \frac{v_{in} - v_-}{r_{in}} = \frac{v_{out}}{A} \frac{1}{r_{in}} = \frac{G}{A} \frac{1}{r_{in}} v_{in}$$


$$R_{in} = \frac{A}{G} r_{in}$$

ENHANCED BY



FACTOR $\frac{A}{G}$ (LOOP GAIN)

RELATIVE TO NO FEEDBACK!


TRANSRESISTANCE AMPLIFIER

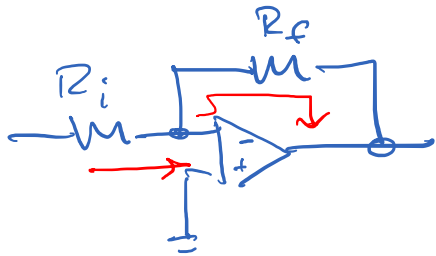

eg

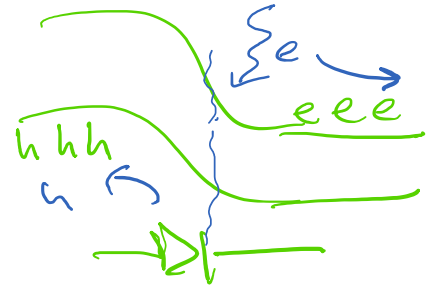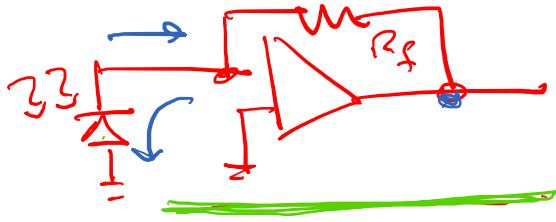

$$G = -R_f / R_i$$

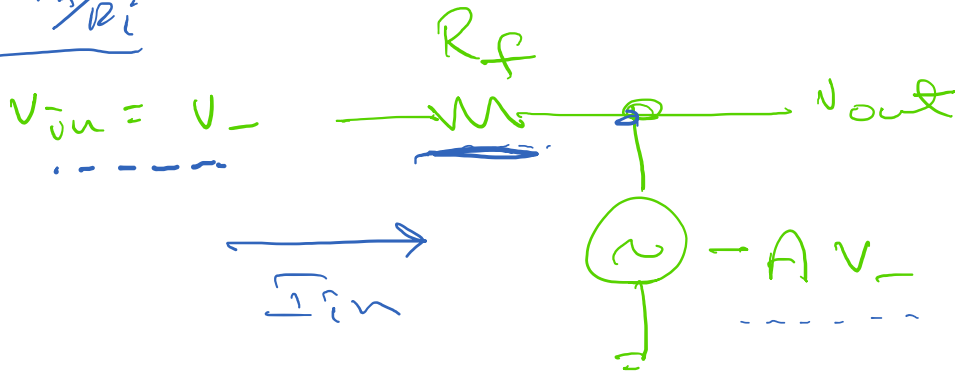


$$I_{in} = \frac{[1 + A]}{R_f} V_{in}$$


$$\Rightarrow R_{in} = \frac{R_f}{1 + A}$$

SUPPRESSION OF INPUT RESISTANCE


NON INVERTING AMP: OUTPUT IMPEDANCE

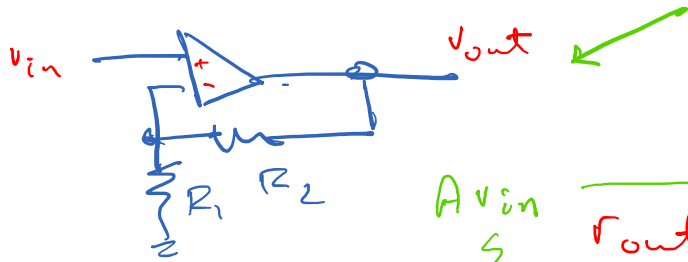

$$A [v_{in} - v_-]$$

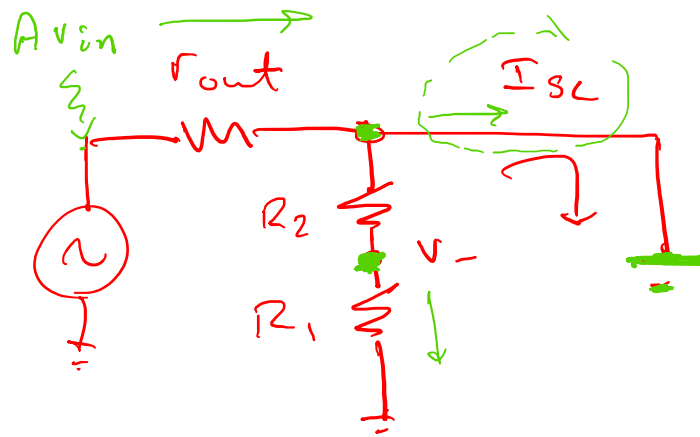

$$R_{out} = \frac{V_{oc}}{I_{sc}}$$

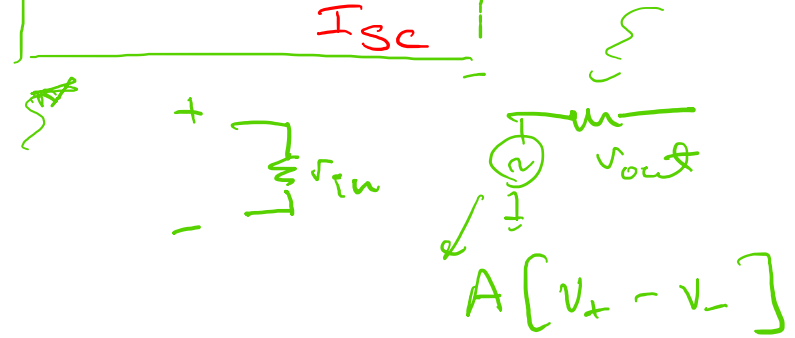


$$v_- = 0$$

$$I_{sc} = \frac{A v_{in}}{v_{out}} \quad ; \quad V_{oc} = G v_{in}$$

$$R_{out} = \frac{G}{A} v_{out} = \frac{v_{out}}{1 + AB}$$


R_{out} is suppressed
 BY FACTOR AB [LOOP GAIN]
 RELATIVE TO
 NO F. FBK.
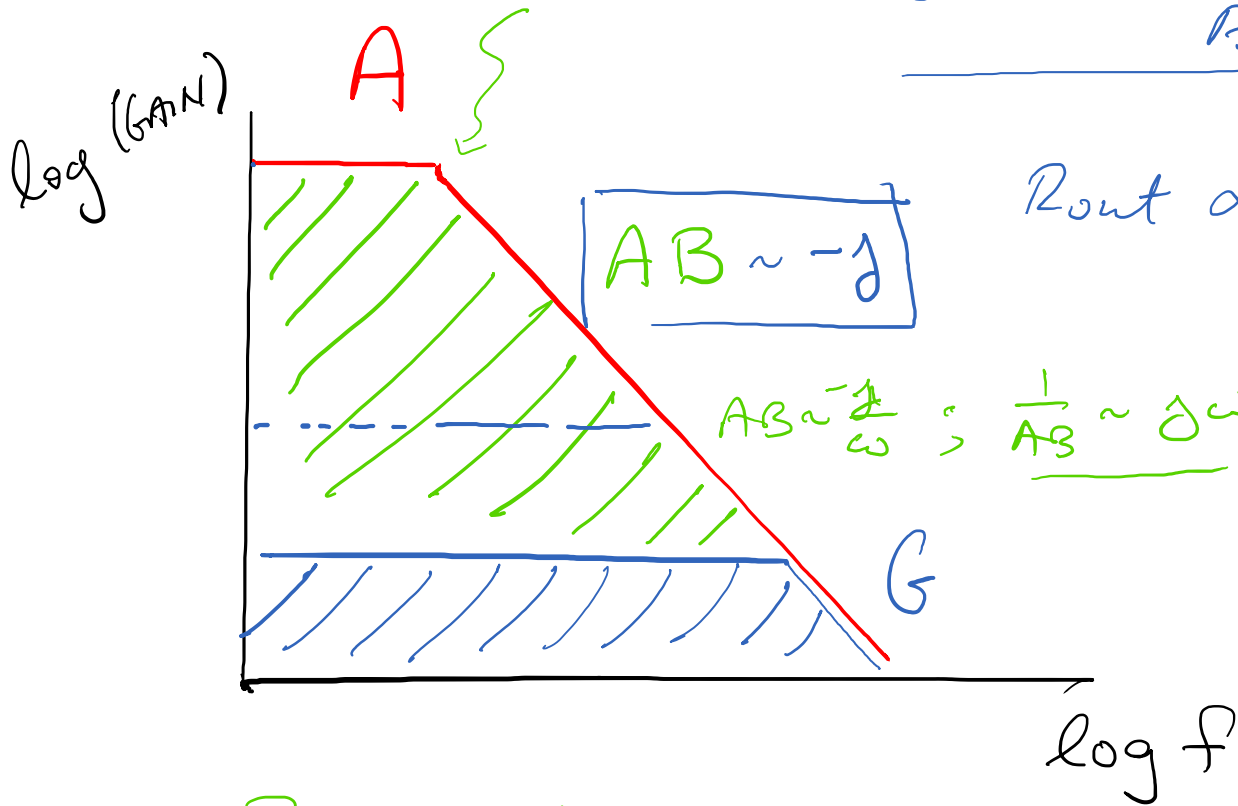
$$R_{out} \approx \frac{r_{out} \epsilon}{AB} \rightarrow \times f \quad \underline{90^\circ \text{ PHASE SHIFT.}}$$




$R_{out} \propto f \Rightarrow$ INDUCTIVE !!

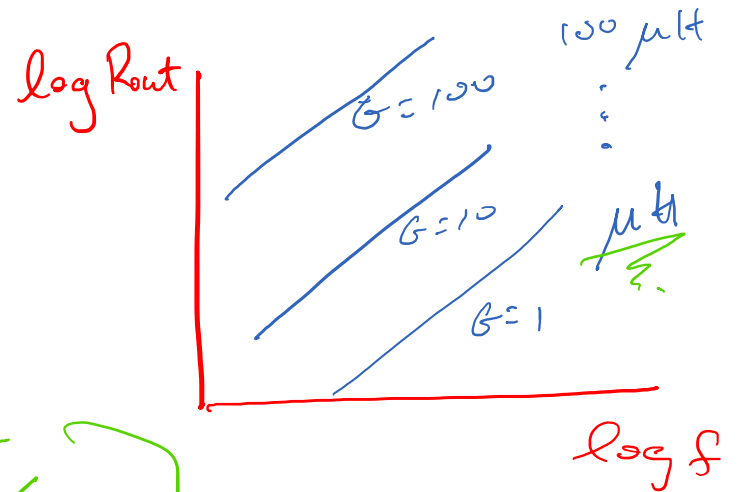
$\Xi \Xi \Xi$
 \rightarrow H.H., FIG 4.53



$$R_{out} \sim \omega$$
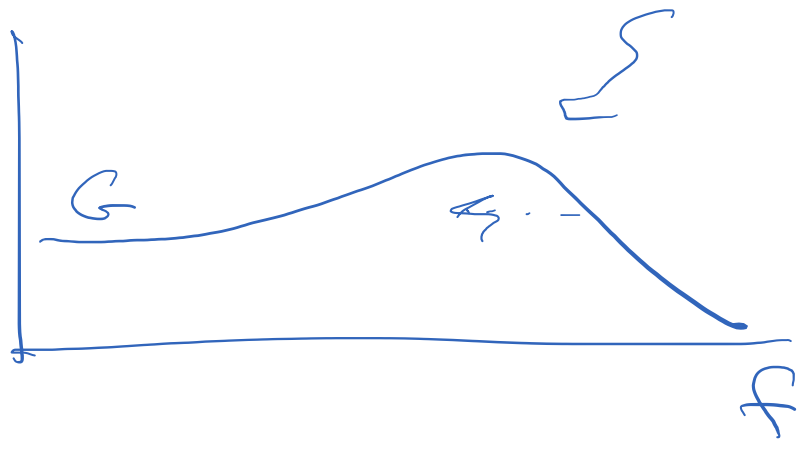
$$\rightarrow BNC \approx 30 \text{ pF/ft.}$$



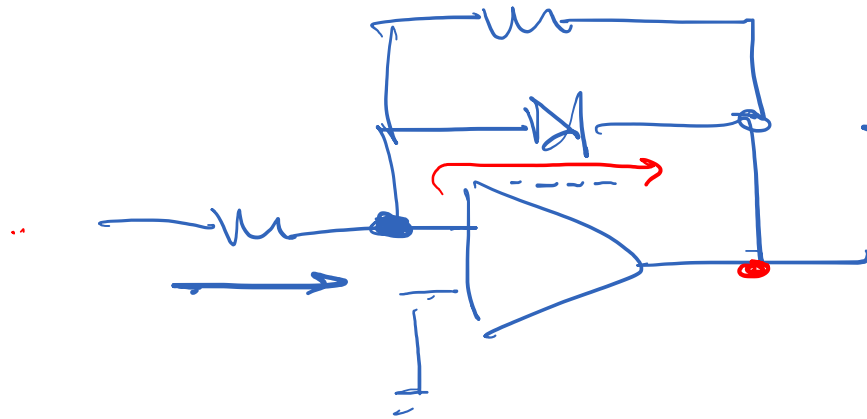

$$I = I_0 e^{\frac{eV}{kT}}$$

$$V \sim \ln I$$