

## Physics 623: HW 7

1) For the below positive feedback circuit, let's assume that the open loop amplifier gain  $A$  saturates as the input voltage is increased with the following functional dependence:  $A = -A_{SS} \left(1 - |V|/V_{SAT}\right)$ .

Here  $A_{SS}$  is the small signal gain,  $V$  is the *output* voltage, and  $V_{SAT}$  is called the saturation voltage (for a real op-amp, the open-loop gain will decrease somewhat at large output amplitudes, although not necessarily with this functional form).

Note that  $A$  is negative. That is, the feedback goes to the inverting input of the amplifier. Assume  $\beta = \left(1 / \left(1 + i \frac{f}{f_c}\right)\right)^4$  (this is a four-pole low-pass filter, where each pole has a corner frequency  $f_c$ ).

- a) What is the minimum value of  $A_{SS}$  such that oscillation will occur?
- b) What will be the amplitude of the steady-state output voltage?
- c) Assume  $A_{SS} = 100$  and  $V_{SAT} = 10$  V, and  $f_c = 100$  Hz.
  - i. Will the circuit oscillate?
  - ii. At what frequency will oscillation occur?
  - iii. Will it be an undistorted sine wave? Why or why not? (No calculations expected – this would be a job for a computer, or someone willing to do a lot of complex algebra.)

