

Analog and Digital Simulation Lab

MultiSim Hints & Kinks

Note: This is a brief summary of how to use a small part of a powerful and flexible tool. Hopefully, it will explain most of what you need for this lab. For further guidance on specific points, or to see what the program can do, you can consult the *MultiSim Getting Started Guide*, *User's Guide*, and *Appendices* found under Software Documentation: MultiSim on the Ph 623 home page. There is also very good online help within the program under the Help menu: Multisim Help. This has a search facility, table of contents, and detailed index.

0. Create a folder on the desktop with your name.

1. Start multisim. There is an icon at Desktop\Lab Software\623\multisim. "File" → "New" if you don't start up with a blank schematic sheet.

2. "File" → "Save As" : find the folder with your name, save the circuit with a reasonable name (such as "diffamp". Don't put any ". " extension on it).

3. Click on any of the small "place component" icons (at left end of 2nd row under menus) to bring up the "Select a Component" window. "Database:" should be "Master Database". Select a "Group" with the component you want. This is not always obvious. But ground points, power supplies, and adjustable DC voltage sources and AC signal generators are all under "Sources". Resistors, Capacitors, and Inductors are under the "Basic" group. Simple voltmeters and ammeters are under "Indicators". There are fancier instruments under the "Simulate" menu: Instruments. After placing one of these, you have to double-click on it to adjust the settings. There is even a Tektronix oscilloscope similar, but not identical, to the ones in the lab (but the generic oscilloscope and 4-channel oscilloscope are much easier to use). You can get rid of any unwanted components in your schematic area by selecting them and hitting the "Delete" key (not "Backspace"). Right click ! "Horizontal flip" to get mirror image for one. But note item 7 below: when you run simulations, you can get plots of the voltage on any net or the current through any component in the "grapher" without attaching any instruments at all.

4. For resistors and capacitors, you don't need to select the particular values you want to use – it's very easy to change the values later for any component (right-click on the component and chose "properties", then edit whatever you need to. Watch the units!). Save often! (This is Windows, remember?)

5. Place a couple of resistors, a couple of unpolarized capacitors, a ground, a Vcc source or "battery", and an AC voltage source (for input). You can copy any object (or collection of objects) on your schematic and paste it as many times as you want. If you've altered properties first, you'll get the same thing in the copies.

6. Wiring is easy: just click on a component lead and then move to where you want to connect it and click there. It will usually auto-route pretty intelligently through one bend, but to make it go where you want you can click at any intermediate point to force it to turn there. You can terminate the wire on another wire just by clicking a point somewhere along the existing wire. So you should generally try to go from a component lead to a wire. If you have to start on a wire, you will need to use ctrl-j and click on the wire to put an almost invisible "junction dot" on it. You can then click on this to start the wire. The escape key will terminate wire routing if you don't want to finish it. Right click on any wire segment and choose "Delete" to delete just that segment. Briefly look through the tabs of "Global preferences" under the "Options" menu. This will give you some idea of what is going on (and the opportunity to change defaults if you wish).

7. "Nets" are a group of components lead and other items that are all interconnected by wires. You should give important nets (such as inputs and outputs) unique names and colors. (Nets are just numbered in order created and colored red by default.) To do this, double click the net, and in the properties box that comes up, select a unique color, type in a name (such as "in-1") and check the box that says "show net name". This will do several good things for you. When you start doing simulations, net names show up on DC bias point lists and as labels on plots. The plots will also color code the lines the same as the net color by default. You will be able to plot the voltage on any net, or the current through any component, without having any meters or instruments in your schematic.

Analog simulation:

8. Attach an AC voltage generator to each input. Set voltage, frequency, and phase to values appropriate for measuring differential or common-mode gain. Note that voltages and phases have to be set in two places: one for transient analyses (turning on the switch in the upper right corner is the same as starting a transient analysis) and one for AC frequency (small signal) analysis.

9. Get the Q-point bias values by "Analysis" → "DC Operating Point". In the window that comes up, select all the net names that you want to appear in the output. You can print out the resulting table for your notebook.

10. "Analysis" → "Transient" to run a time-integrated nonlinear simulation. Choose start and end times and output items you want plotted, then click on "simulate". Default time steps are usually OK, but you can set a smaller minimum step if the output isn't as smooth as you'd like.

11. "Analysis" → "AC Frequency" to make Bode Plot (gain and phase vs frequency). Use log-log scales. This takes over the frequency settings of any AC voltage sources you have in the circuit. It also uses the alternate "Phase for AC analysis" you have set for signal sources on your schematic. Since this is a linear small signal analysis around the Q point, the ac analysis magnitude isn't used. It does use the magnitude you give it to scale the input and output values, so it is convenient to set the input to 1 V pk. Then the output volts will just be the gain. (You can set the input to 100 V if you want. If the small signal gain is 10, it will show the output as 1000 V.)

12. The Grapher window will come up by itself after a simulation, but if you've closed it, "View" → "Grapher" (or click tiny graph icon near center) to see results. DC bias point is still on first tab (old results are kept even if you close the window – you can press "delete" key twice to delete them). **Try the icons from the little grid through the third magnifying glass to see what they do. You will want to leave the grids on – need to put on both graphs. You also need to switch background to white if it is black.** You can resize graph by edges or corner, and move the legend around and reshape it. Right click on graph → "Properties" lets you change scales, colors, etc. Or just double-click on almost anything you want to change. Traces with small amplitudes can be moved to the right axis, then "Enable" that and autoscale it. On "file" → "print preview" (from top bar of the grapher window) select pages you want to print. Don't forget to Save! (Graphs are saved separately from the schematic.)

16. You can print out your schematic from bar above main menu. First choose "File" → "Print options" → "Print sheet setup...". You'll want landscape. 100% will fill page. 70% is probably about right. If you are using measuring instruments, you can print their faces exactly as they appear by choosing "File" → "Print options" → "Print instruments". (Use "single" sweep on scope to get full trace when it stops, "Reverse" to get white background.) But the screen outputs of the instruments also appear on pages in the Grapher window, and you have a lot more flexibility here for fixing the display before you print them, so this is usually recommended.

Digital simulation:

"File" → "New" to get rid of (hopefully saved) analog circuit and get new blank sheet. "Save as" with appropriate name. (You will probably have to navigate back to your folder again.)

Right click on schematic sheet → "Place component". Use TTL → 74LS series flip flops and gates. For the DAC use "Mixed" → "ADC_DAC" → "VDAC". For the comparator, use "Analog" → "Comparator" → LM311N. This is the same part you used in the lab and needs all the same connections, including power supplies – go back and look at the data sheet or your notebook if necessary. If you want to be clever, you can notice that there is a large unit of the circuit that is repeated four times. So draw just this part once, copy, and paste it three times. You can then interconnect.

The "Word generator" can generate an arbitrary timing diagram on up to 32 outputs. Double-click on the word generator to bring up the programming window. Set the display to "Hex". Each 8-hex-digit "word" in the list drives the 32 output lines (four bits per octal digit), and the generator advances through the list of words at the clock rate that is set in the generator. Set rate to 1 kHz. Eight clock pulses are enough for a conversion, so you can use just the first sixteen words. Right-click on the 16th word and "set final position" to stop it at this point. You can use one bit for the clock, one to make the "reset" pulse (so you don't need a switch—put this at the beginning), and one to make the "start" pulse. If you use just the lsb of the first three hex digits, it will be easier to "read" your table (or set the format to binary and use the three lowest bits). Try 1000 Hz for an initial clock speed.

The logic analyzer will produce a timing diagram plotting all the inputs. Double-click the logic analyzer to open its display, then click on the "set" box under "clock" to set the rate to about 100x word generator clock rate to give good time resolution. Also set pretrigger samples to 200 and post trigger to 10,000. Then set "clocks per division" to 200 for a reasonable display. You can monitor the clock, start and reset pulses as well as the four D flip-flop outputs and the comparator out (and the four J-K f/f outputs if you want). If you "color code" the wires going into the logic analyzer, the corresponding traces on the analysis plot will come out in the same color. This can be handy. Use a two-channel oscilloscope to look at the comparator inputs. **Push 'reverse' button to set white background. Time/div should be two word generator clock periods.**

For "Vin" source, try "Sources" → "Signal Voltage sources" → DC_Interactive_Voltage. Slider will set the voltage to any value in the range set in "Properties". Cycling the power (0-1) rocker switch in the upper right corner resets all the plots to start at the left edge. You can print everything from the grapher for maximum flexibility.

If you are running out of time for making the second circuit, you can ask the instructor for a pre-drawn one.